
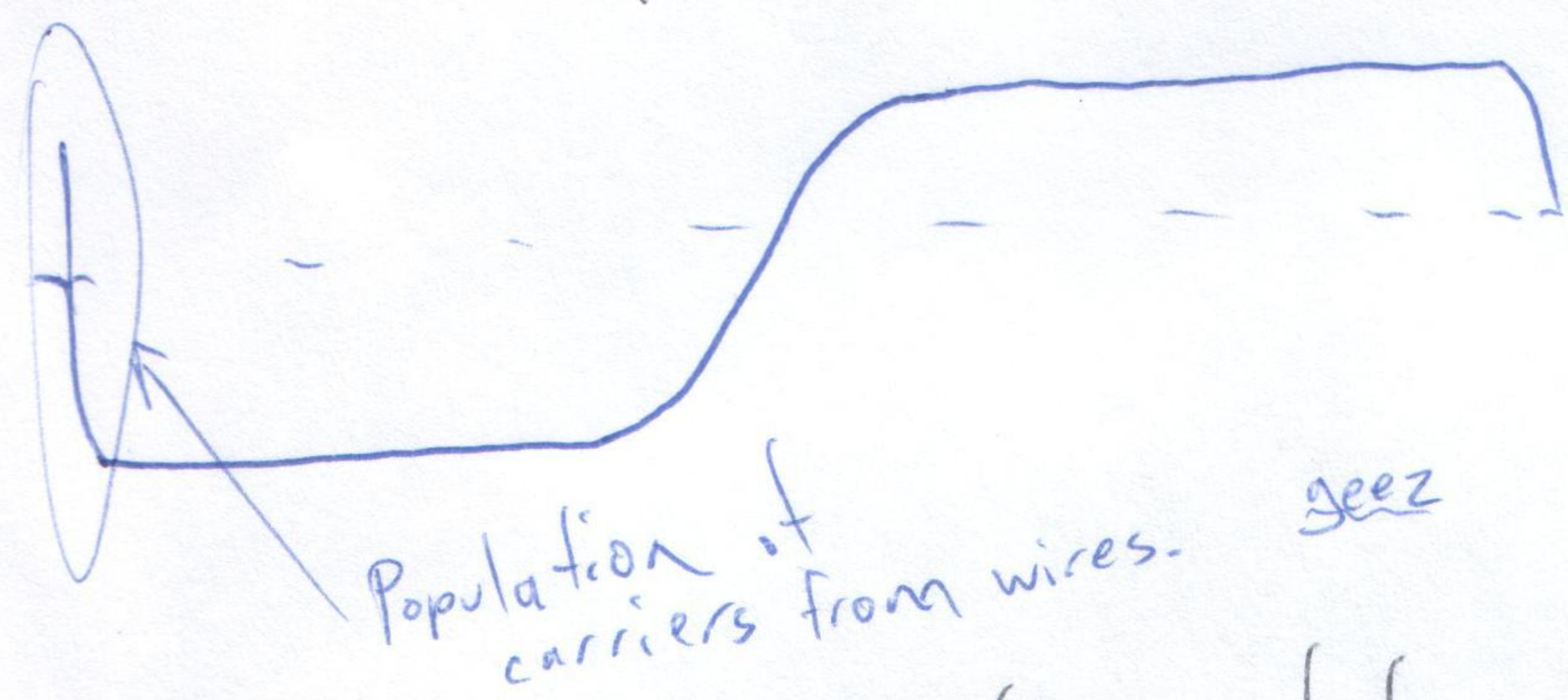


Loose Ends:

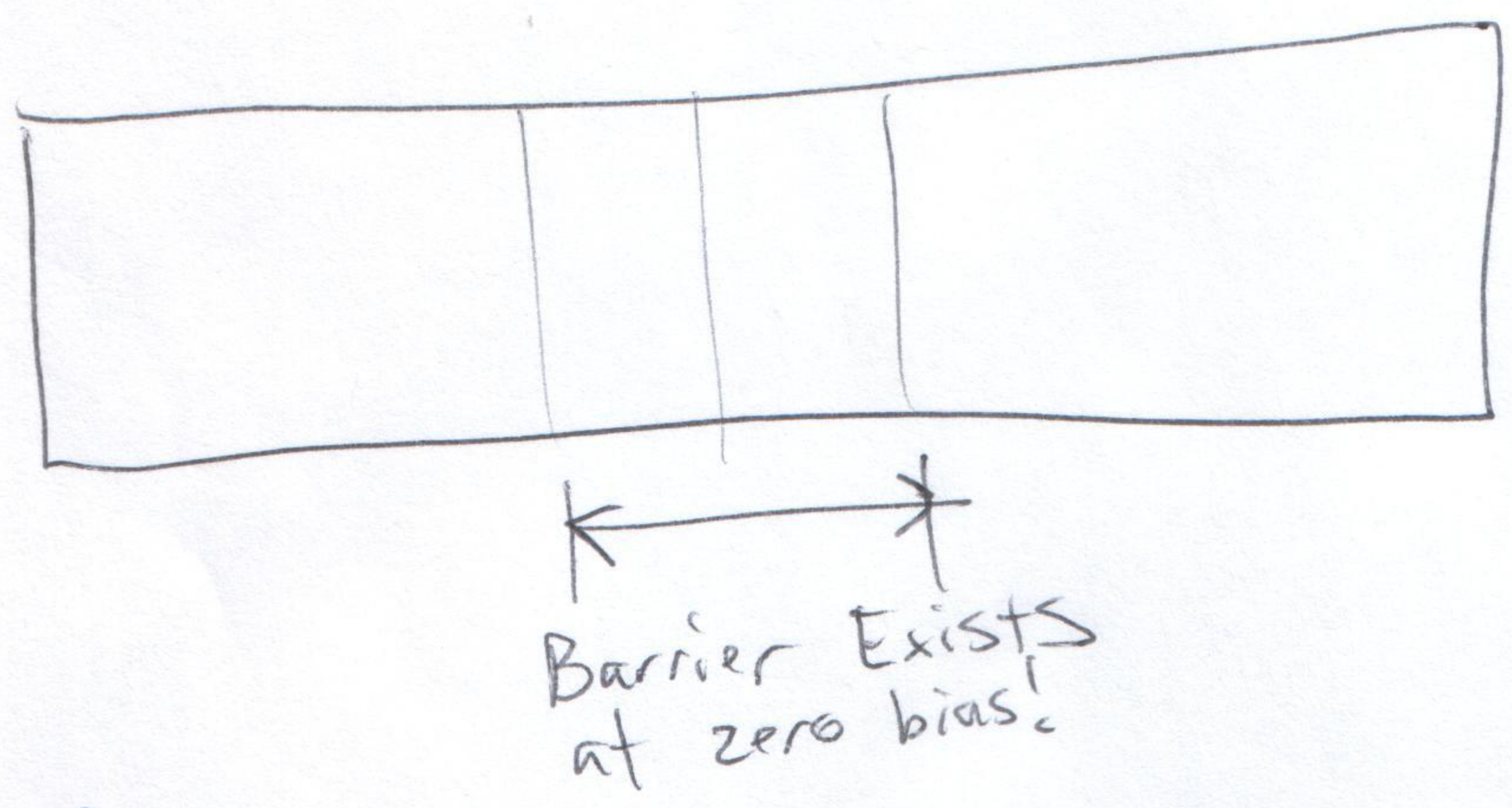

In answer to the bloody awful maths at the end of 3.1. $E_{MAX} = \frac{qN_A X_P}{\epsilon}$ or $\frac{-qN_D X_n}{\epsilon}$

$$\phi_j = -\int E = \frac{|E_{MAX}(X_P + X_n)|}{2}$$

← area of a rectangle
← area of a triangle

or: $\frac{E_{max} X_P}{2} + \frac{E_{max} X_n}{2}$ nice because:

$$\phi = \frac{qN_A X_P^2}{2\epsilon} + \frac{qN_D X_n^2}{2\epsilon}$$

$$Ax^2 + By^2 \stackrel{?}{=} (x+y)^2 \frac{AB}{A+B}$$

*True for $A \neq B$, $Ax^2 = By^2$

$$\phi = \frac{q}{2\epsilon} (N_A X_P^2 + N_D X_n^2)$$

$$\phi = \frac{q}{2\epsilon} \cdot W^2 \frac{N_A N_D}{N_A + N_D}$$

solve for W

$$W = \sqrt{\phi \frac{2\epsilon}{q} \frac{N_A + N_D}{N_A N_D}}$$

$$= V_T \ln \left(\frac{N_A N_D}{n_i^2} \right)$$

← STILL WEIRD


Actually Computing the N Curve:

$$N_c \cdot q \cdot \mu \cdot E - \mu V_T \cdot \frac{dN_c}{dx} = j$$

Solutions to this relationship are $E = \frac{dV}{dx}$ mostly terrible, so, SHORTHAND:

If the ~~field~~ ^{dep. region} exists, current must flow across it.
as V -applied ^{goes more negative} ~~increases~~, ~~so does~~ the effective R
gets larger by \sqrt{V} .


Not I_s !

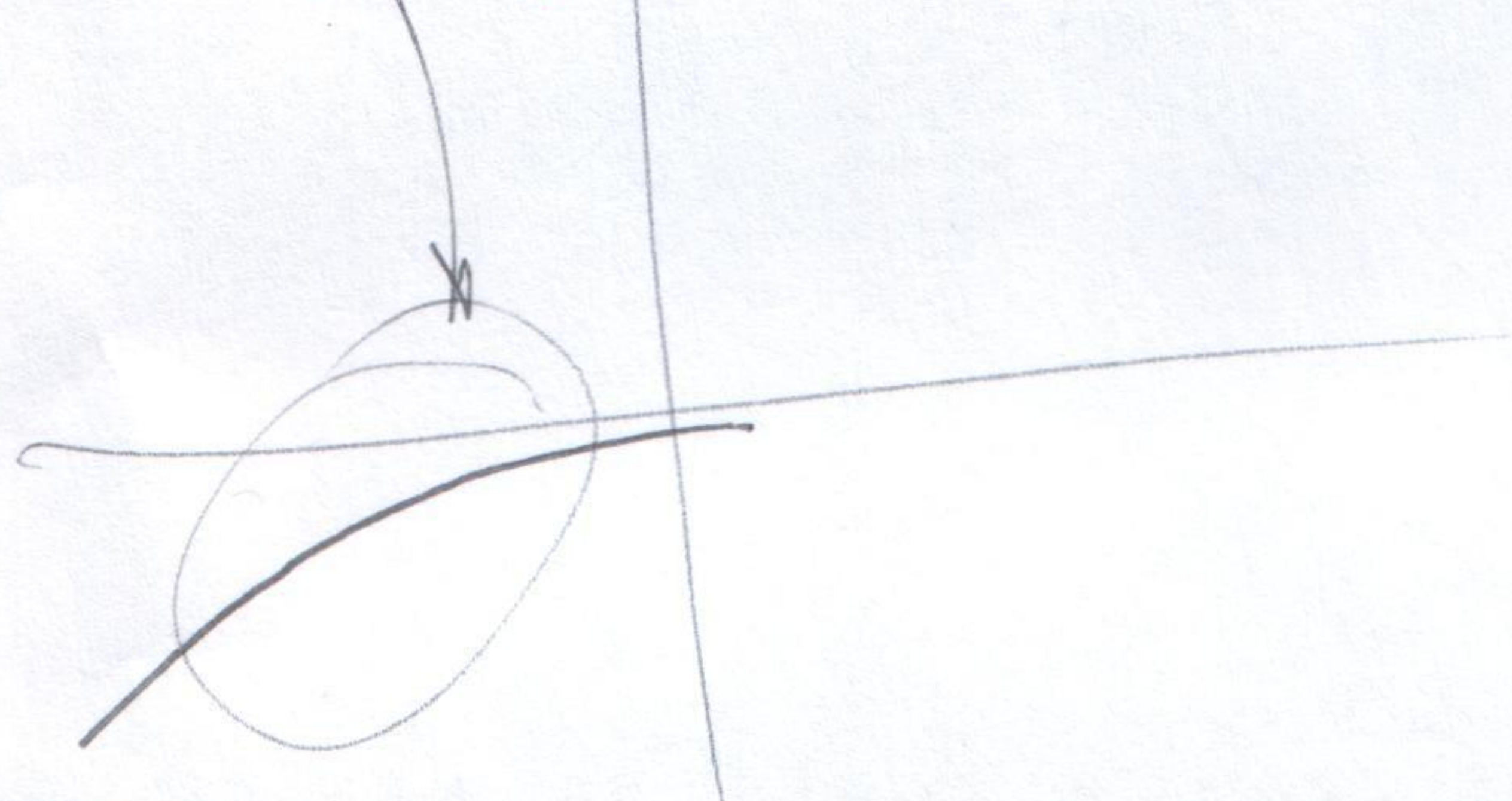


OR: Diffusion and Drift are now actually pointing in the same direction and increasing the field increases both. It is this approach that gives the exp. relationship.

Note: none of this directly gives you exactly the model $I = I_s e^{V/V_T}$.


Structure of Diode Theory:

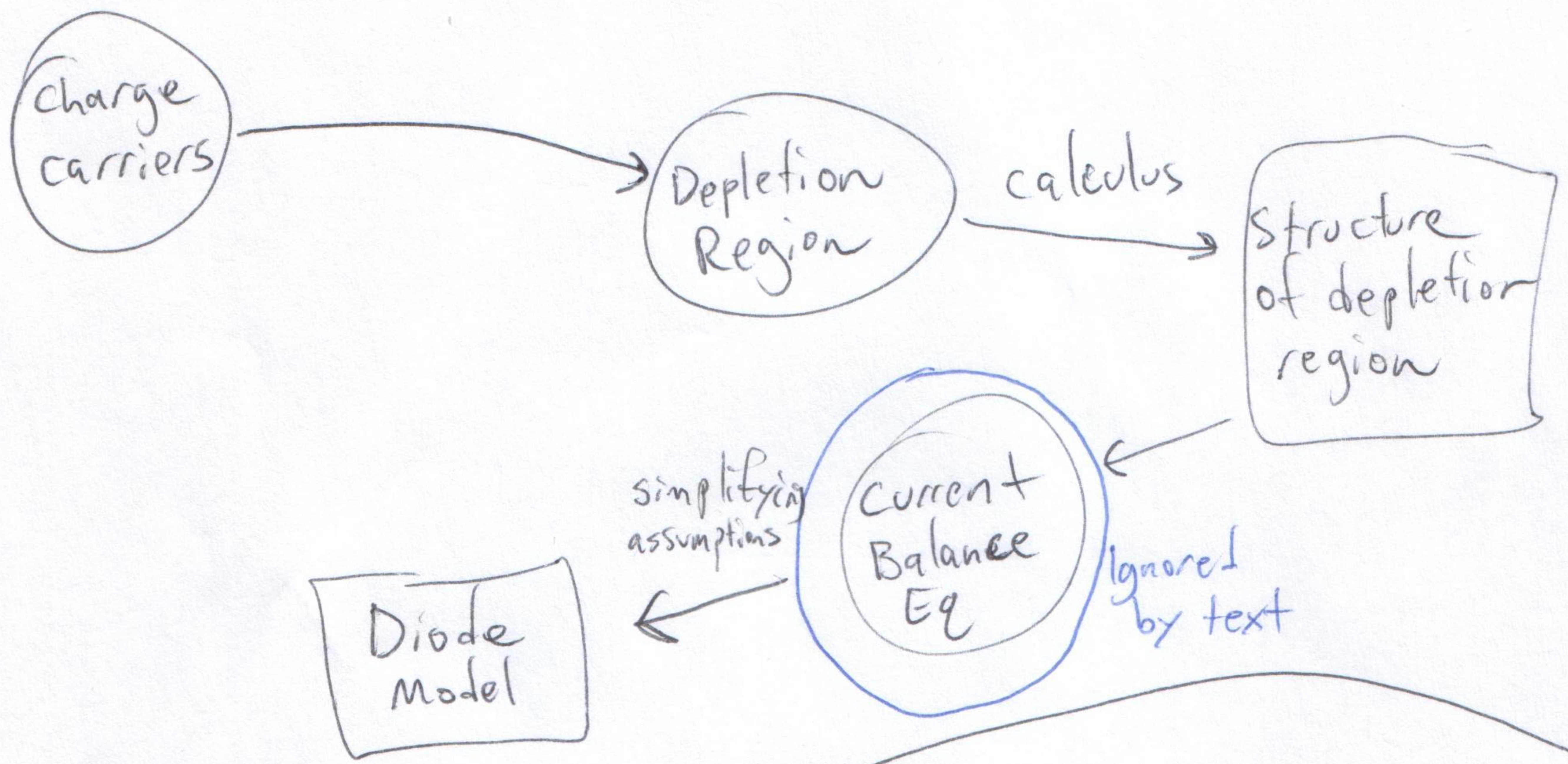

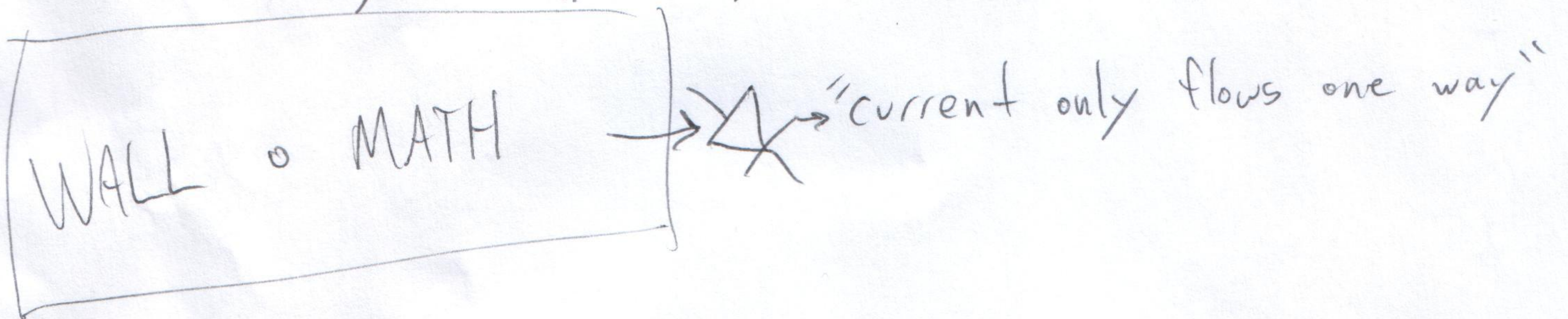From here out, Device Physics and Circuit Theory will have a somewhat rocky relationship. We will solve circuits by stretching math over physics, often in a pretty sloppy way:




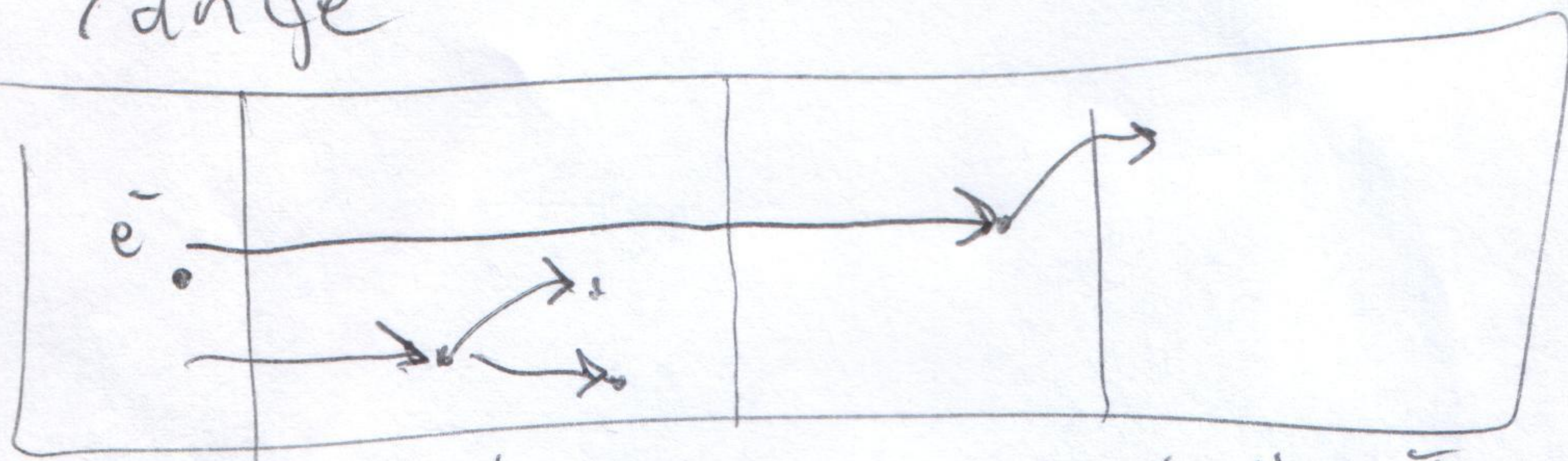In extreme $R.V.$ cases, the inside of the diode junction turns into a kind of electron firing range




essentially "making its own holes" This is Avalanche breakdown.

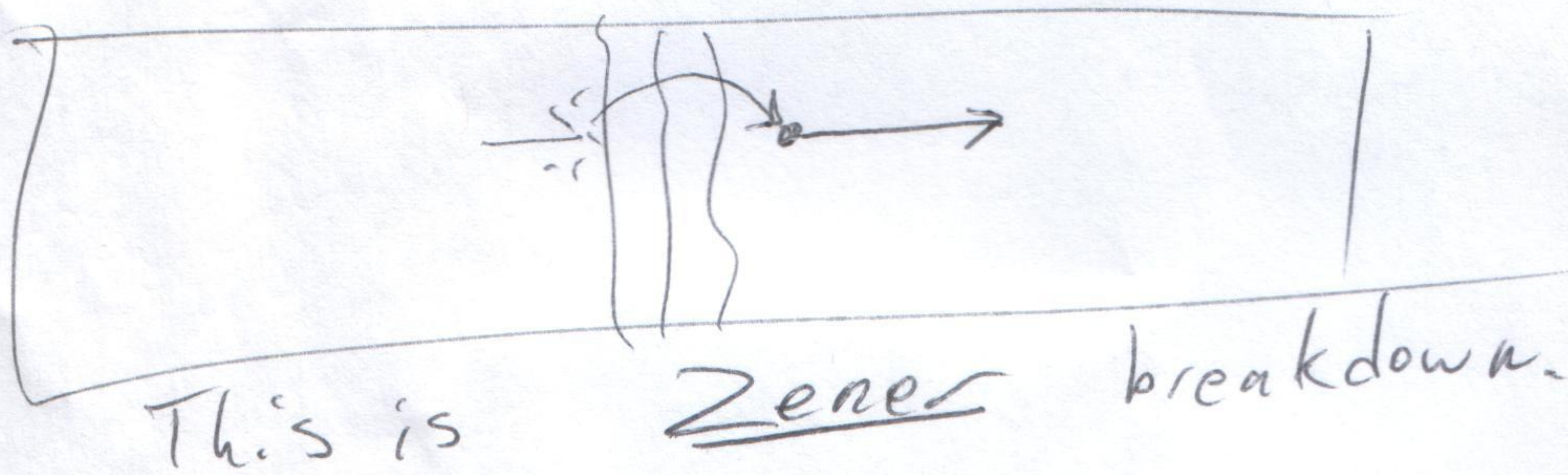Breakdown can also occur because electrons are CRAZY. Heavily-Doped diodes will have very small junction regions which means electrons are not particularly obligated to not just TELEPORT ACROSS.




This is Zener breakdown.

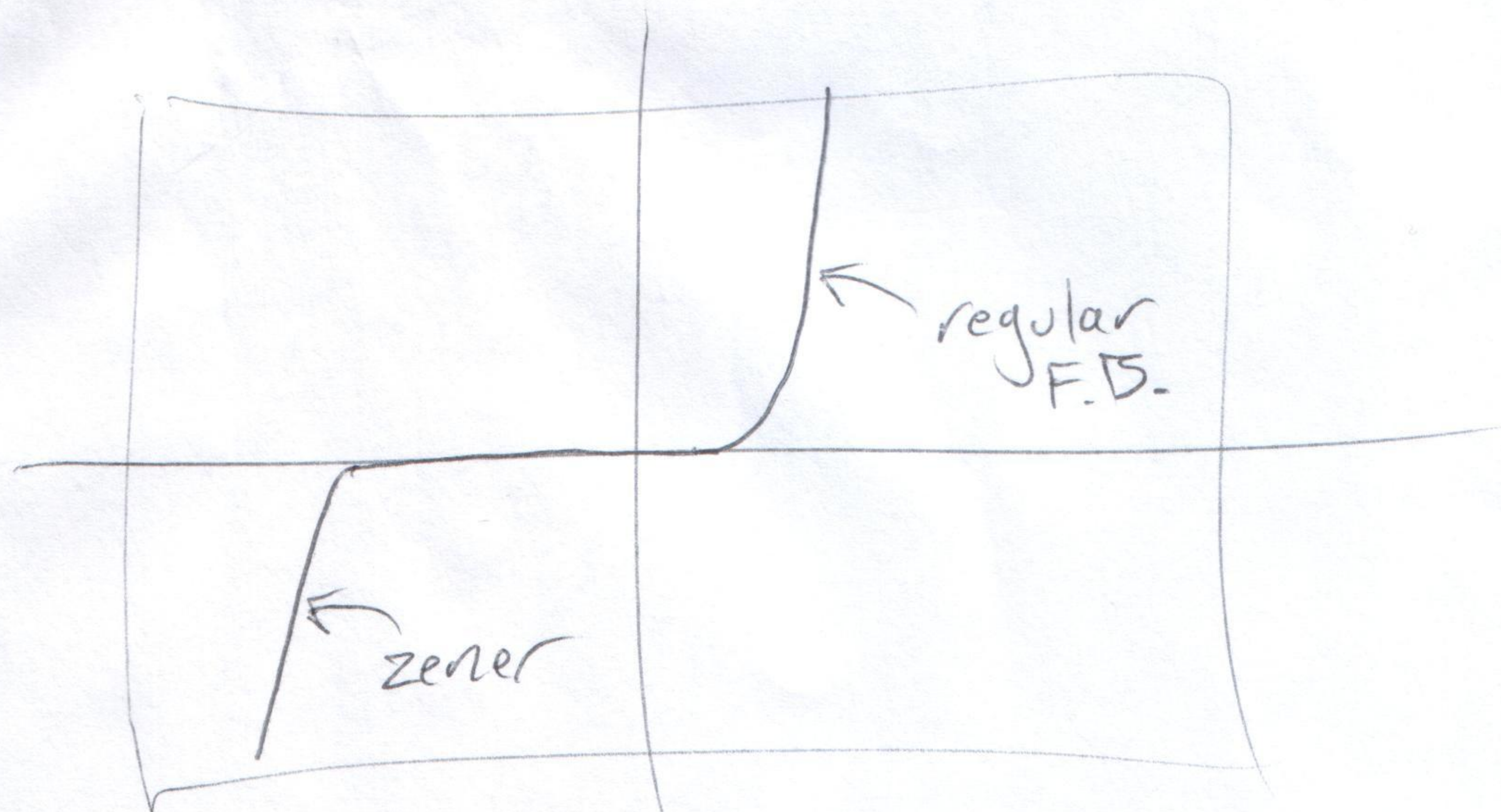

Diodes in Circuits

$I = f(V)$ ← note, assumes transient behavior is instantaneous.

Models with no reverse bias breakdown:

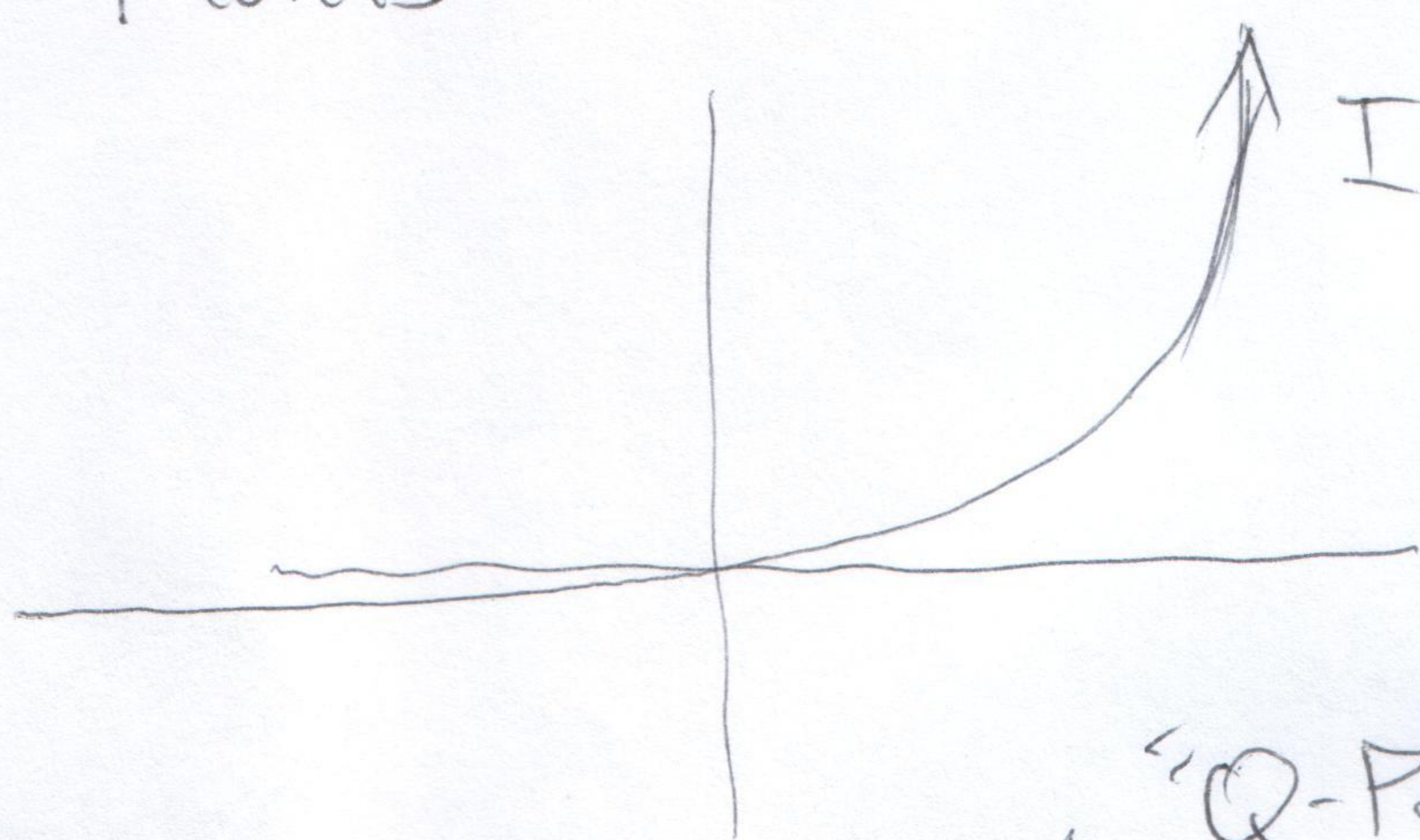

$$I = I_s (e^{V/V_T} - 1)$$


- * pure passive
- * accurate in f.b.
- * quite real

(but, transcendental!)

$$I = I_s e^{V/V_T}$$

mostly accurate!
not -quite- true passive
but algebraically way
easier without much
error.

"Q-Point" - linearization
~~Thevenin~~

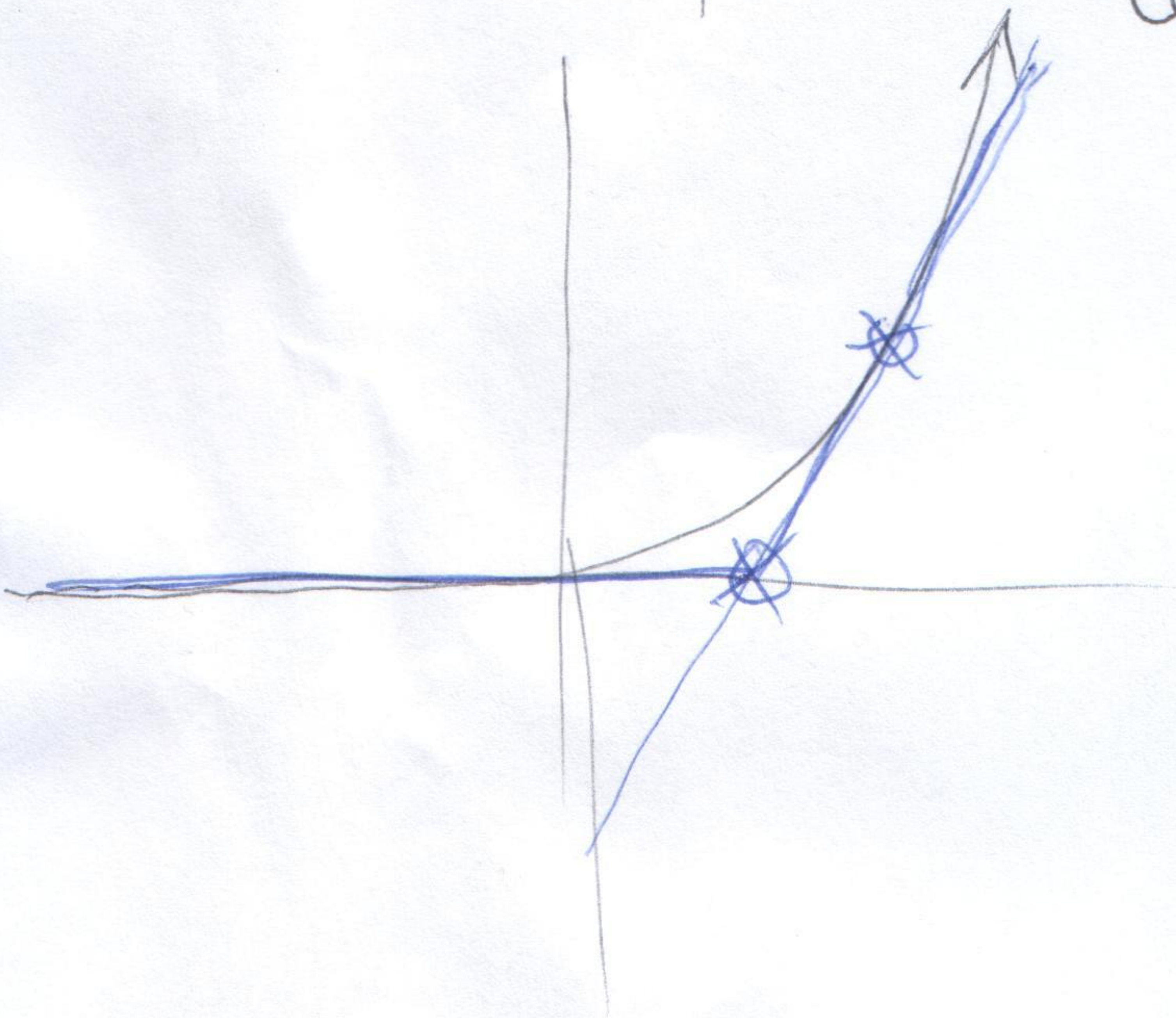

- Derive from above model with:

$$R_m = \left(\frac{\partial I}{\partial V} I_s e^{V/V_T} \right) \Big|_{QPOINT} =$$

$V_m = X$ -intercept

$$R_m = \frac{V_T}{I_{QPT}} \quad V_m = V_{QPT} - V_T$$


$$* V < (V_{QPT} - V_T),$$

$$I = 0$$

dunde

Turn-on Voltage:


$V = e h$, pick something.

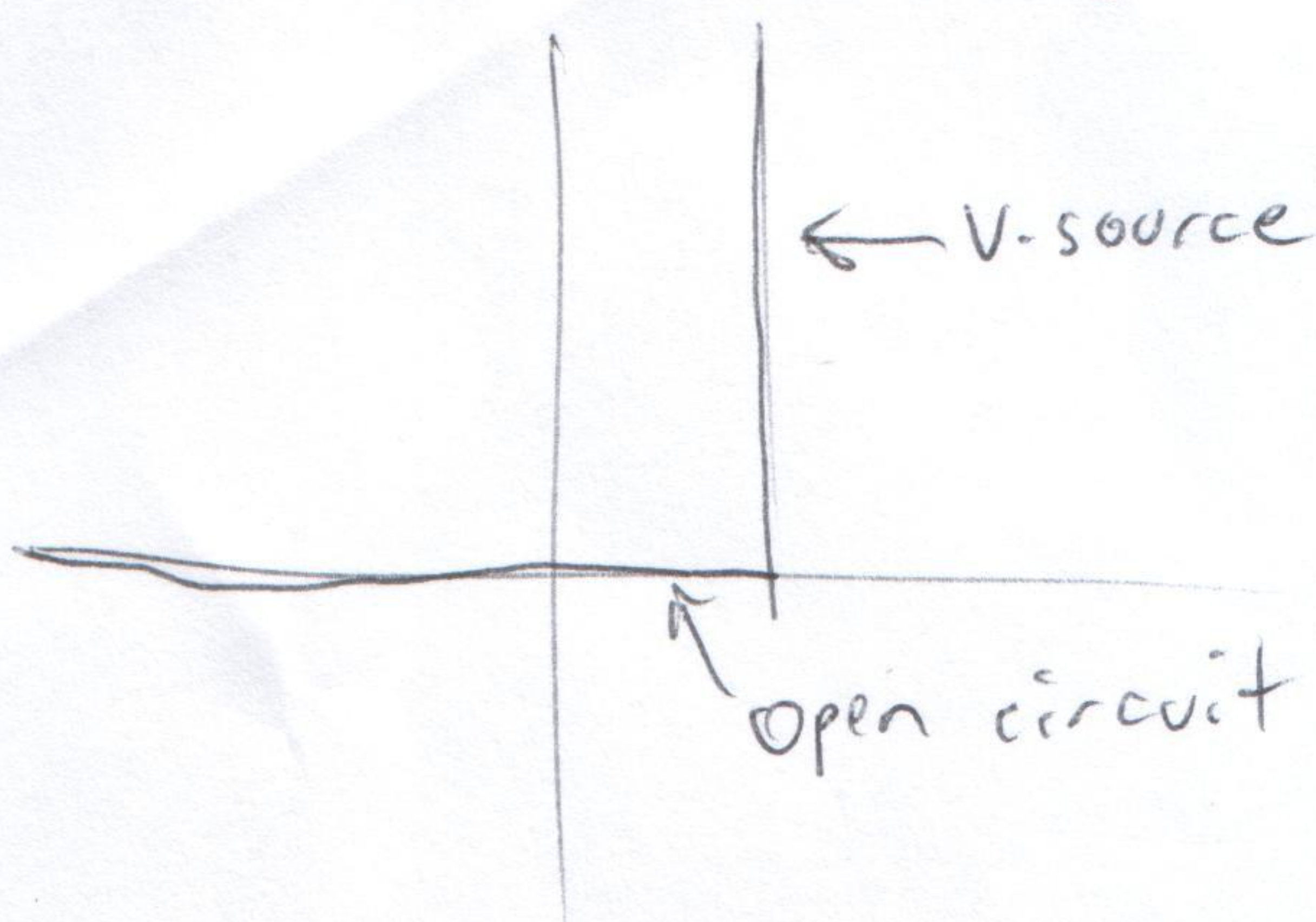

"Ideal Diode"

- best as a mental model or if voltages are $\gg V_{BI}$
- get used to circuits like this being "quick mental first cut"


Reverse Breakdown:

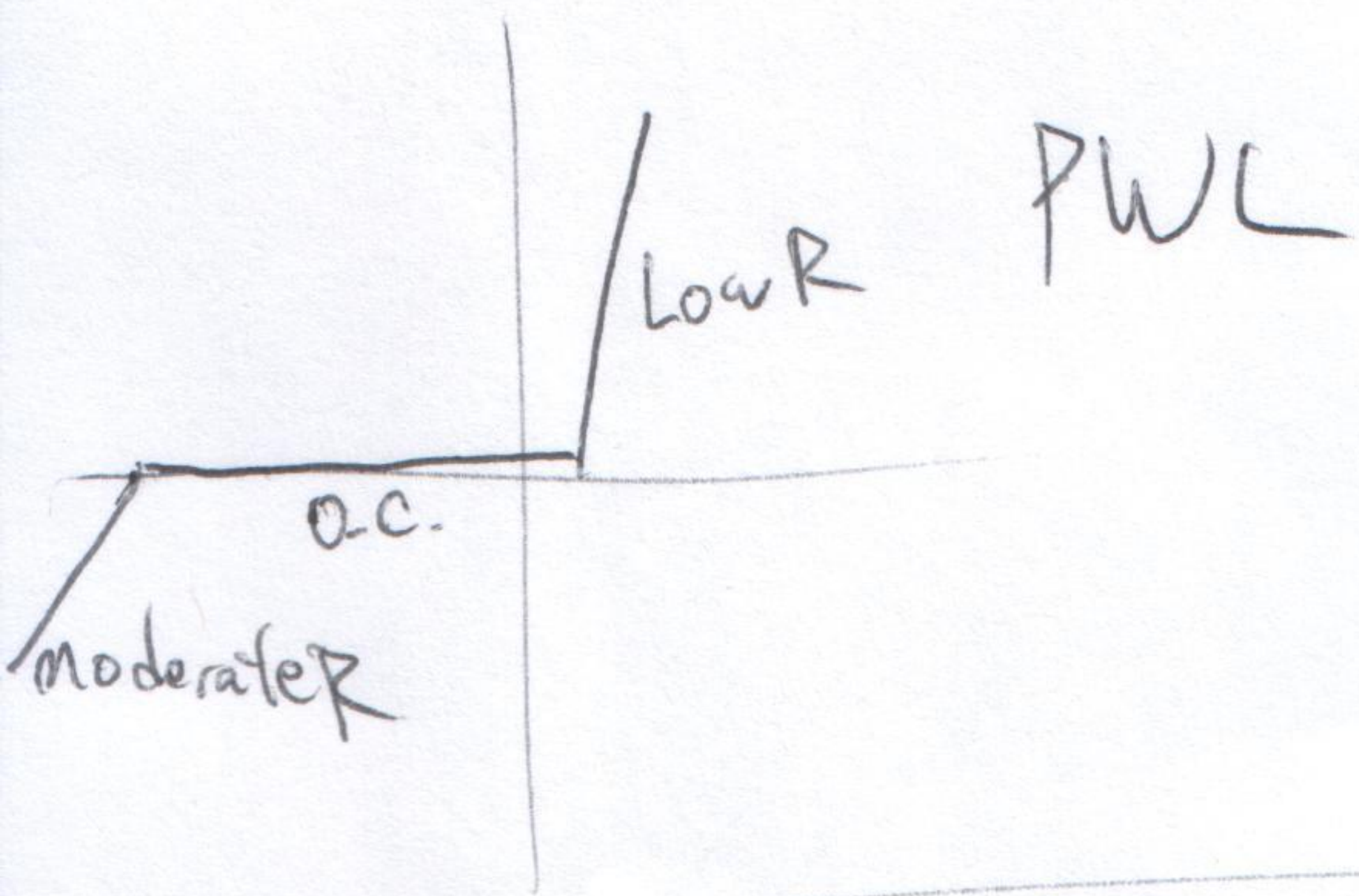

← commonly used in cheap regulators, etc

Enough models! Time for circuits:

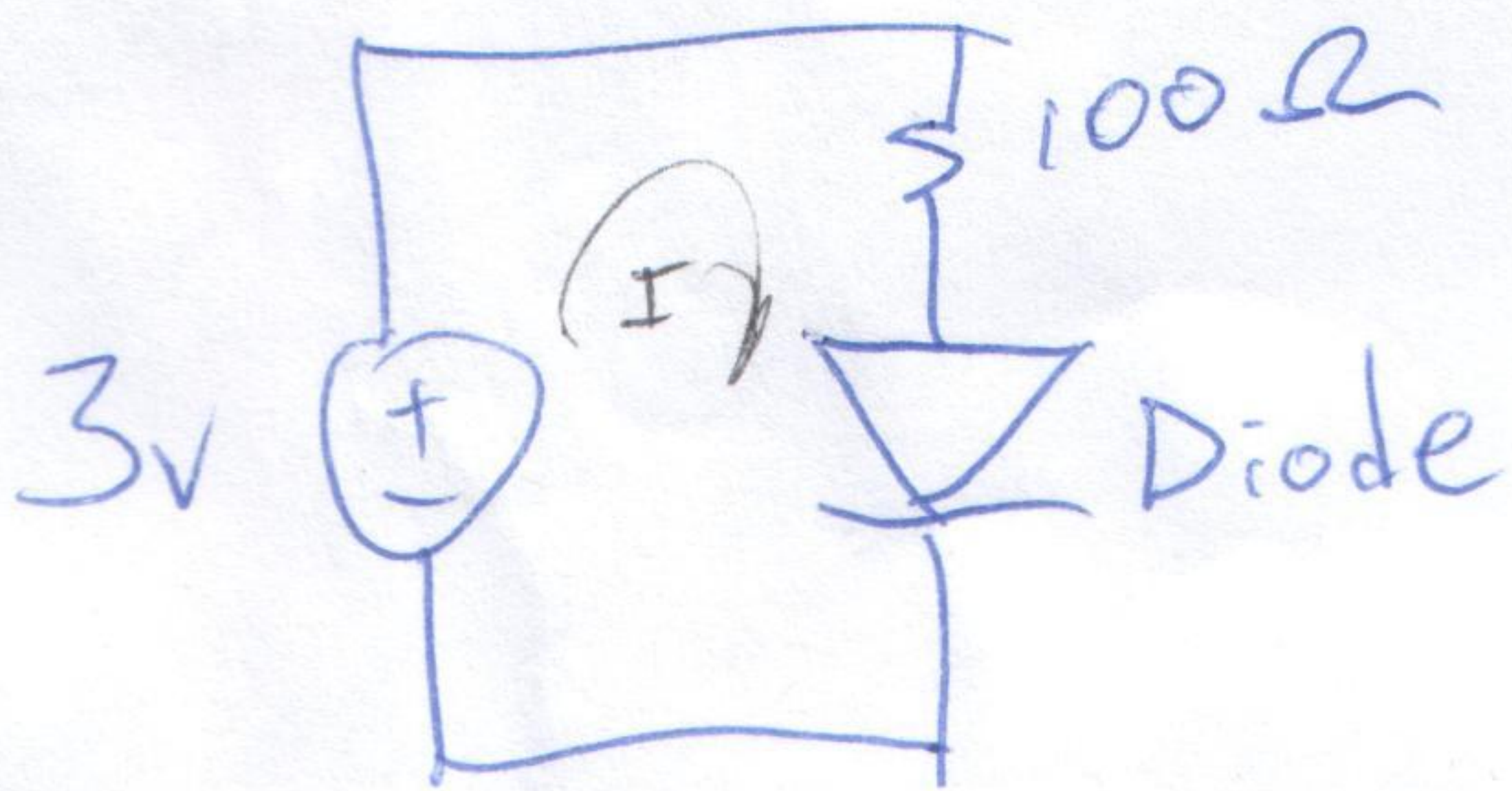Most Accurate: actually solve everything:




KVL:

~~$$3 + 100 \cdot I + V_D(I) = 0$$~~


$$3 + -100I - V_T \ln \frac{I}{I_S} = 0$$

solve that.

But that's irritating.

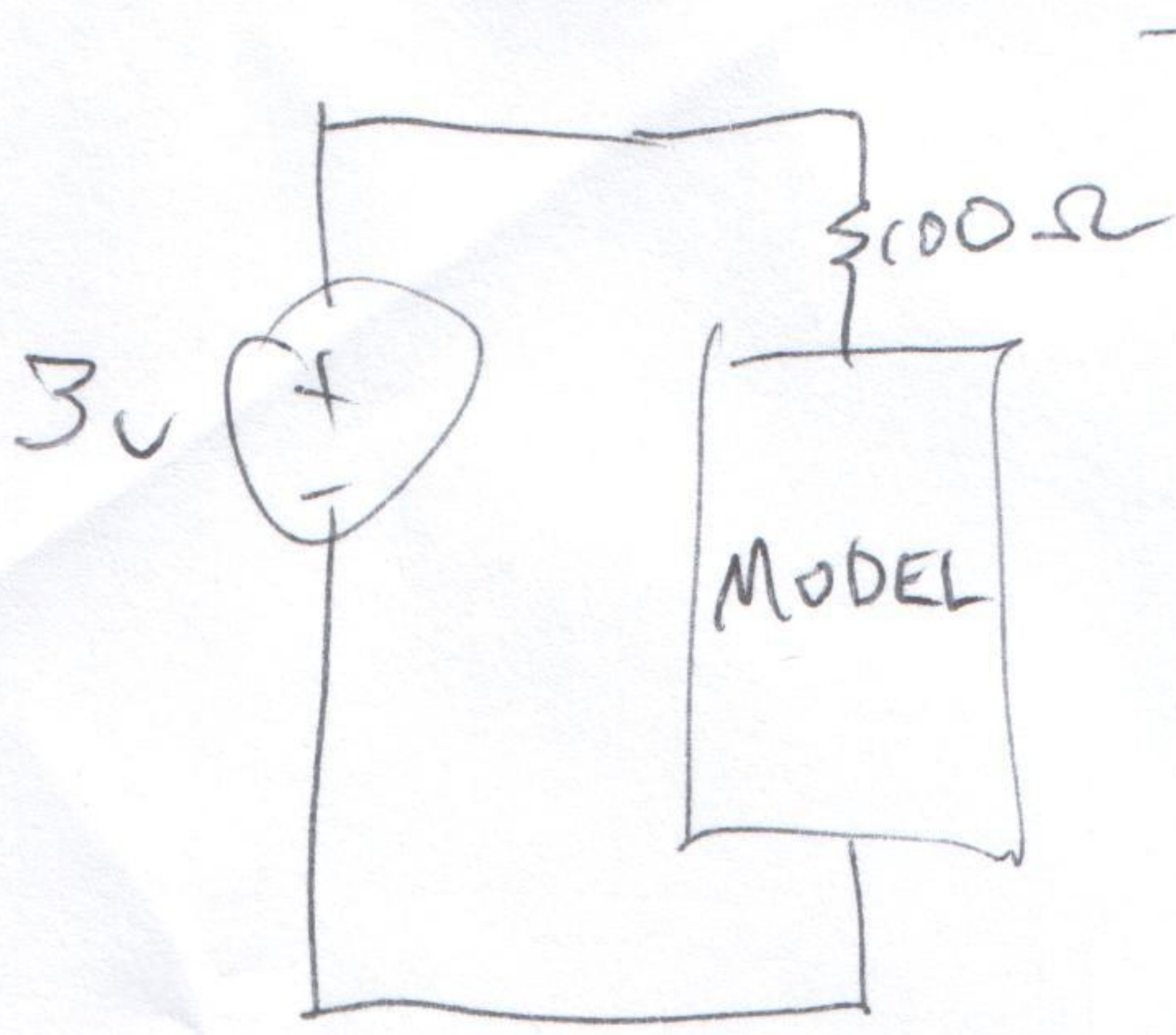

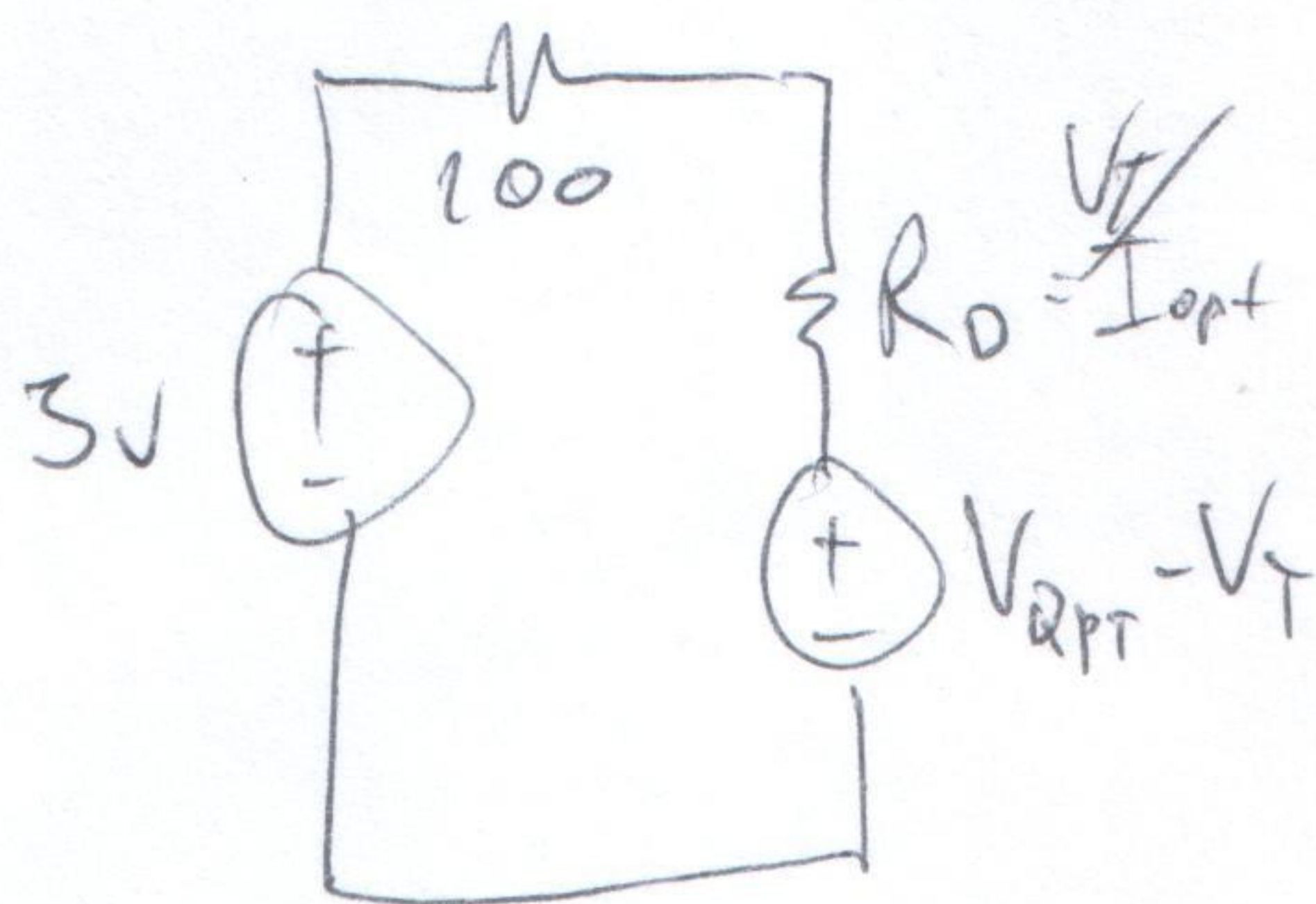Model can be any chosen ~~value~~ model type.




← solve this circuit.

$$3 + -100 \cdot I + \frac{-V_T}{I_Q} \cdot I - V_{QPT} + V_T = 0$$

linear!


* In this circuit it is obvious this is a forward bias situation

easier:

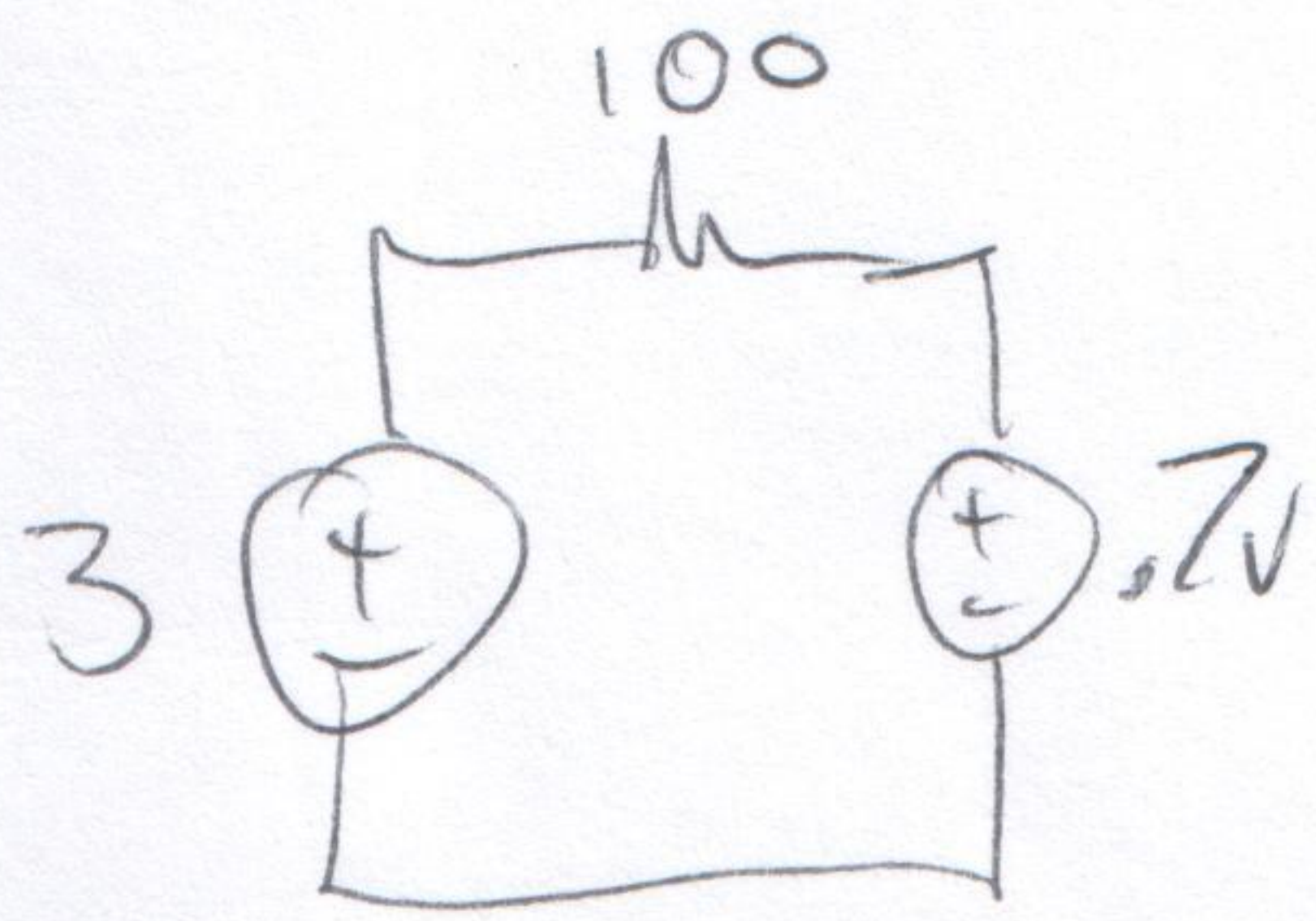


$$I = \frac{2.3V}{100\Omega} = 23mA$$

EASIER!

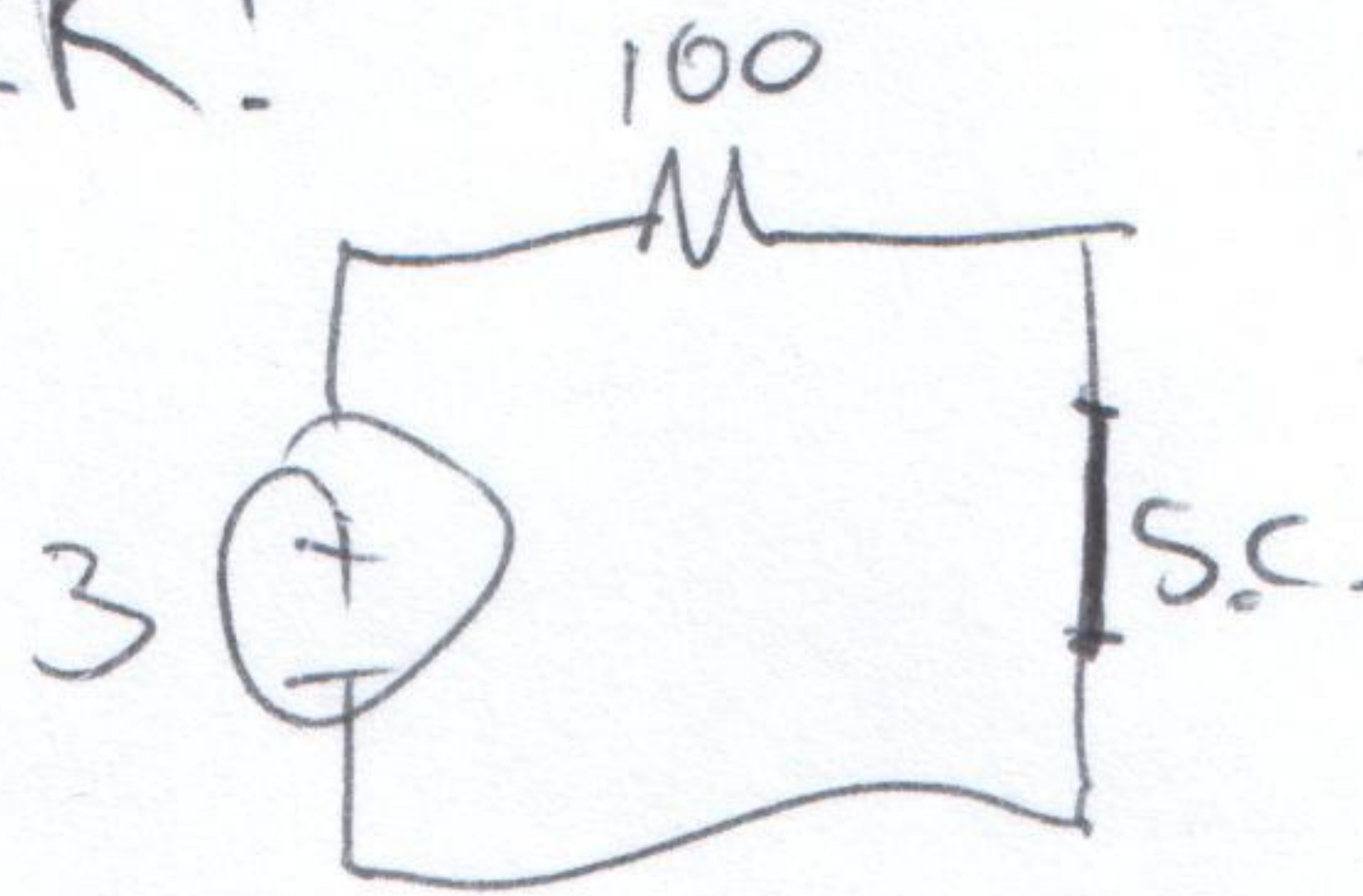

$$I = \frac{3}{100} = 30mA$$

Compare with load-line:


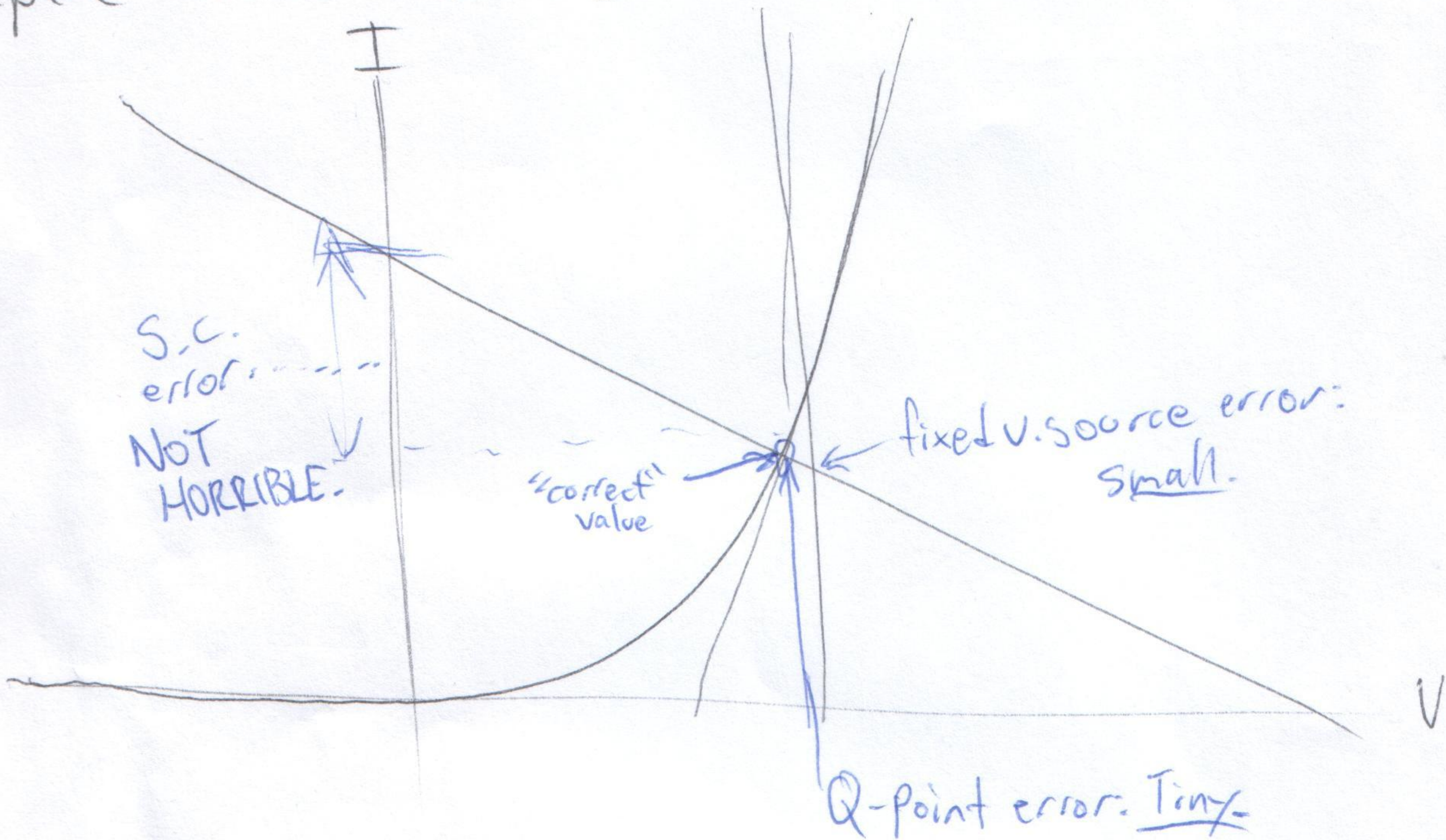


All of these models are imperfect. However, so are diodes! I_s can vary wildly, and temperature shifts will also have an impact.


Figuring out circuits:

- 1 diode: obvious.
- 2 diodes: not hard.
- 3 diodes: not impossible.
- 4 diodes: SPICE.

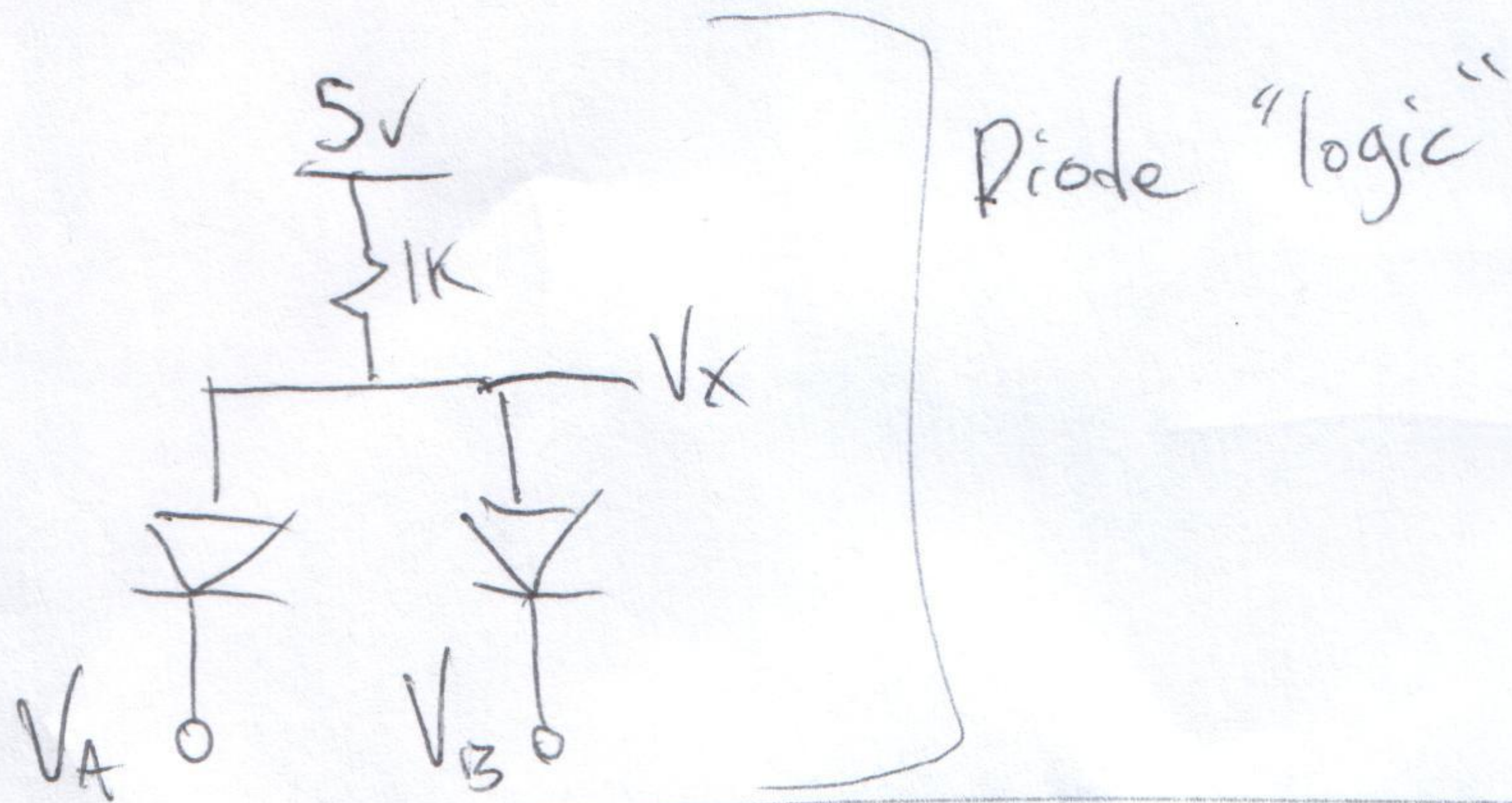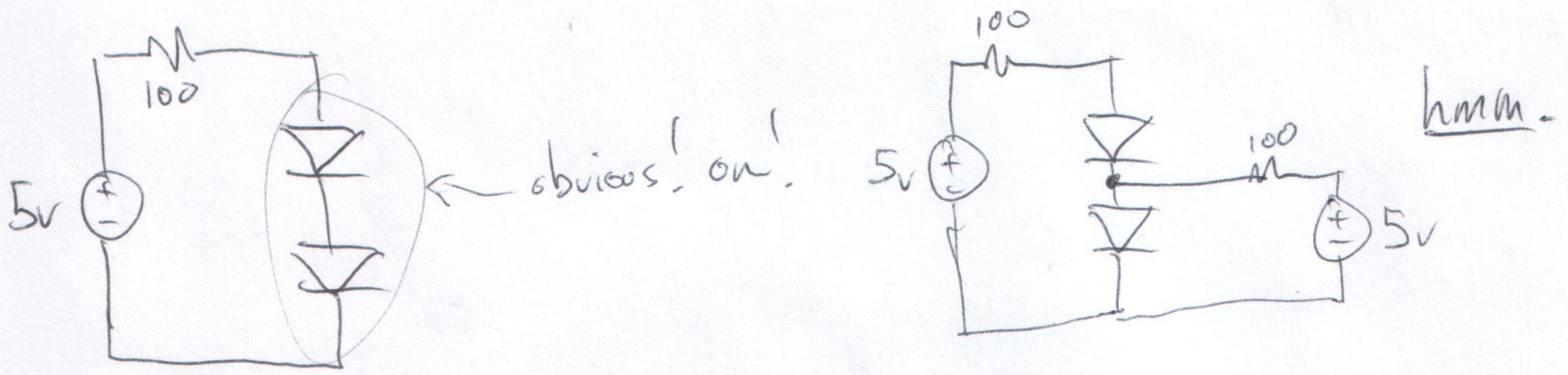Binary search in state-space for active diodes:



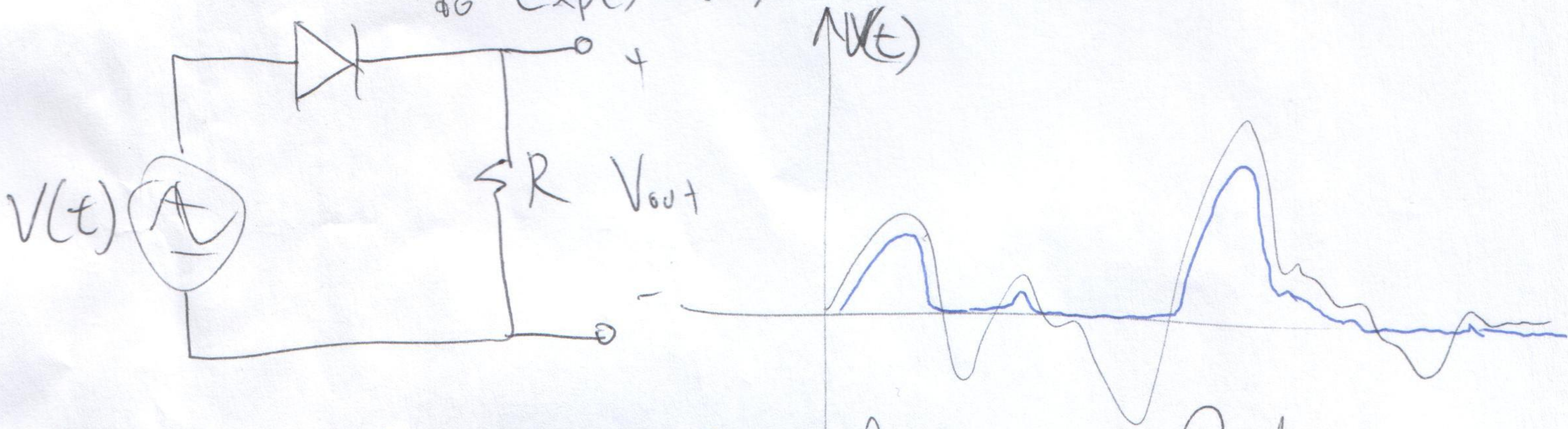
Transients: yeah definitely don't do exp() in your head...



AC vs DC, Rectifiers & Radio




Diodes in Circuits

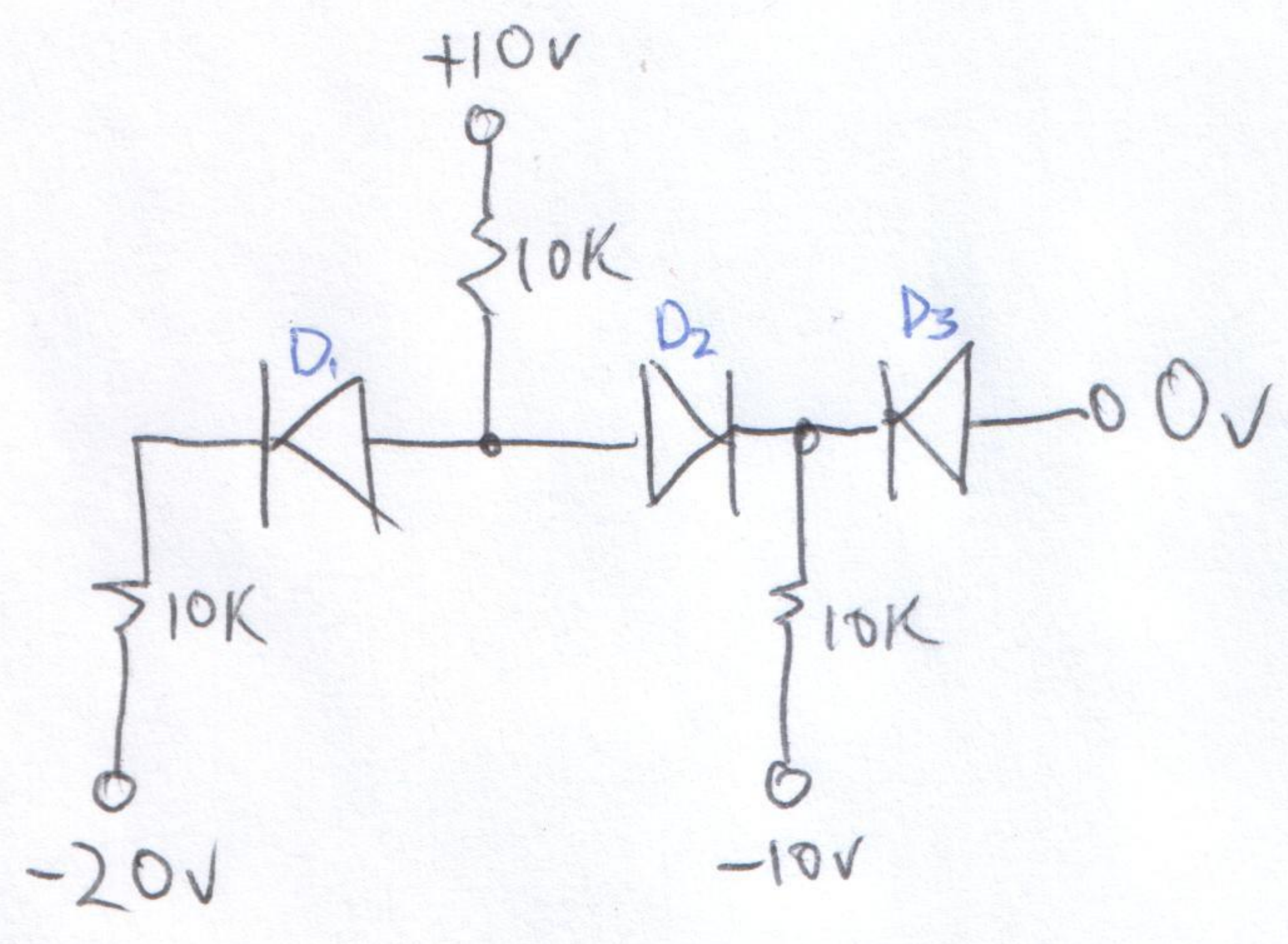


Possible Set of Modes:

D_1	D_2	D_3
off	off	off
off	off	on
off	on	off
off	on	on
on	off	off
on	off	on
on	on	off
on	on	on

However, intuition can help a lot here.

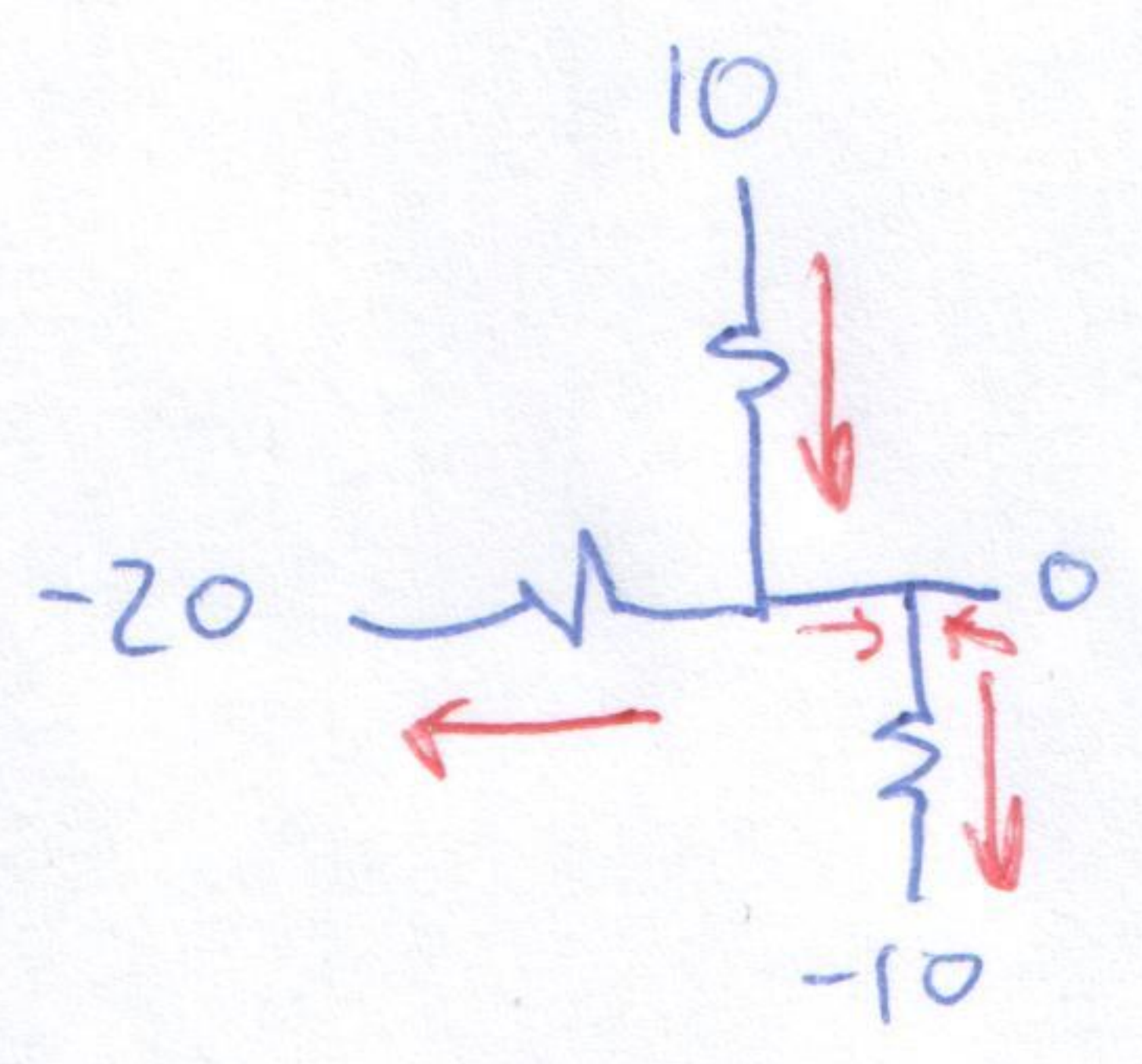


→ Sounds Legit.

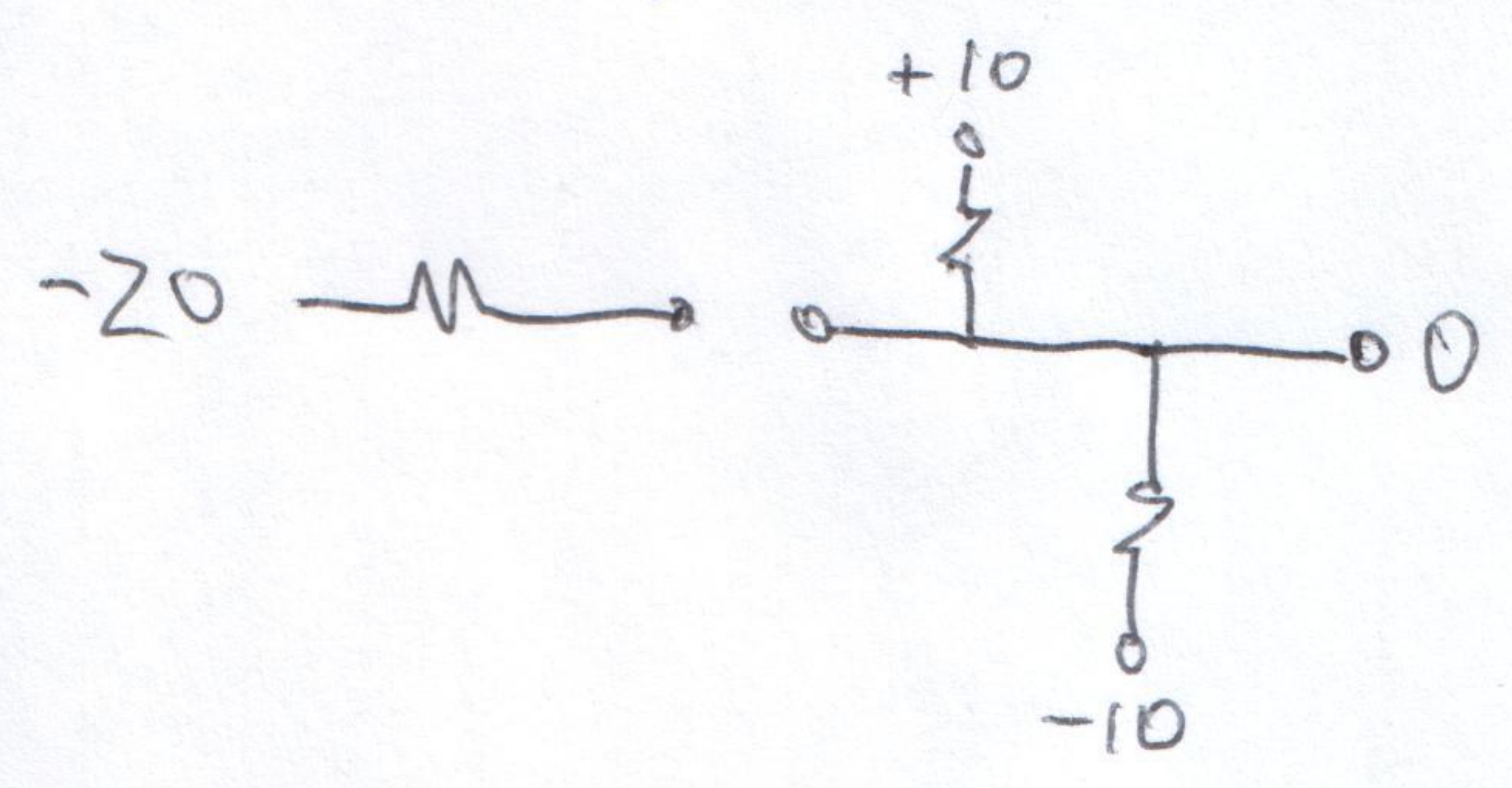


Practice: choosing ~~resistor~~ different diode mode will show +30v across one, obviously F.B.


Regulators I

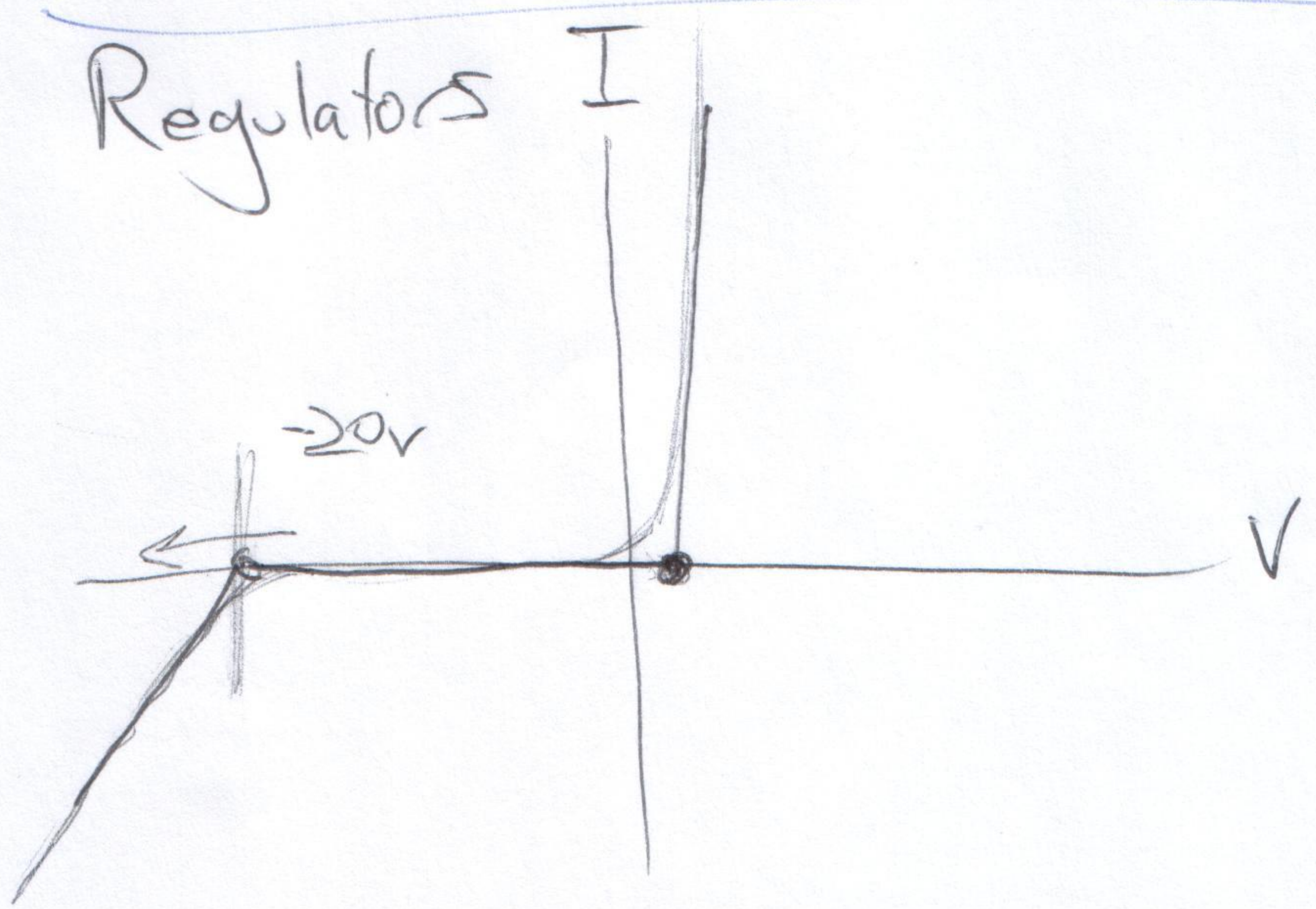

→ Potential use as regulators:

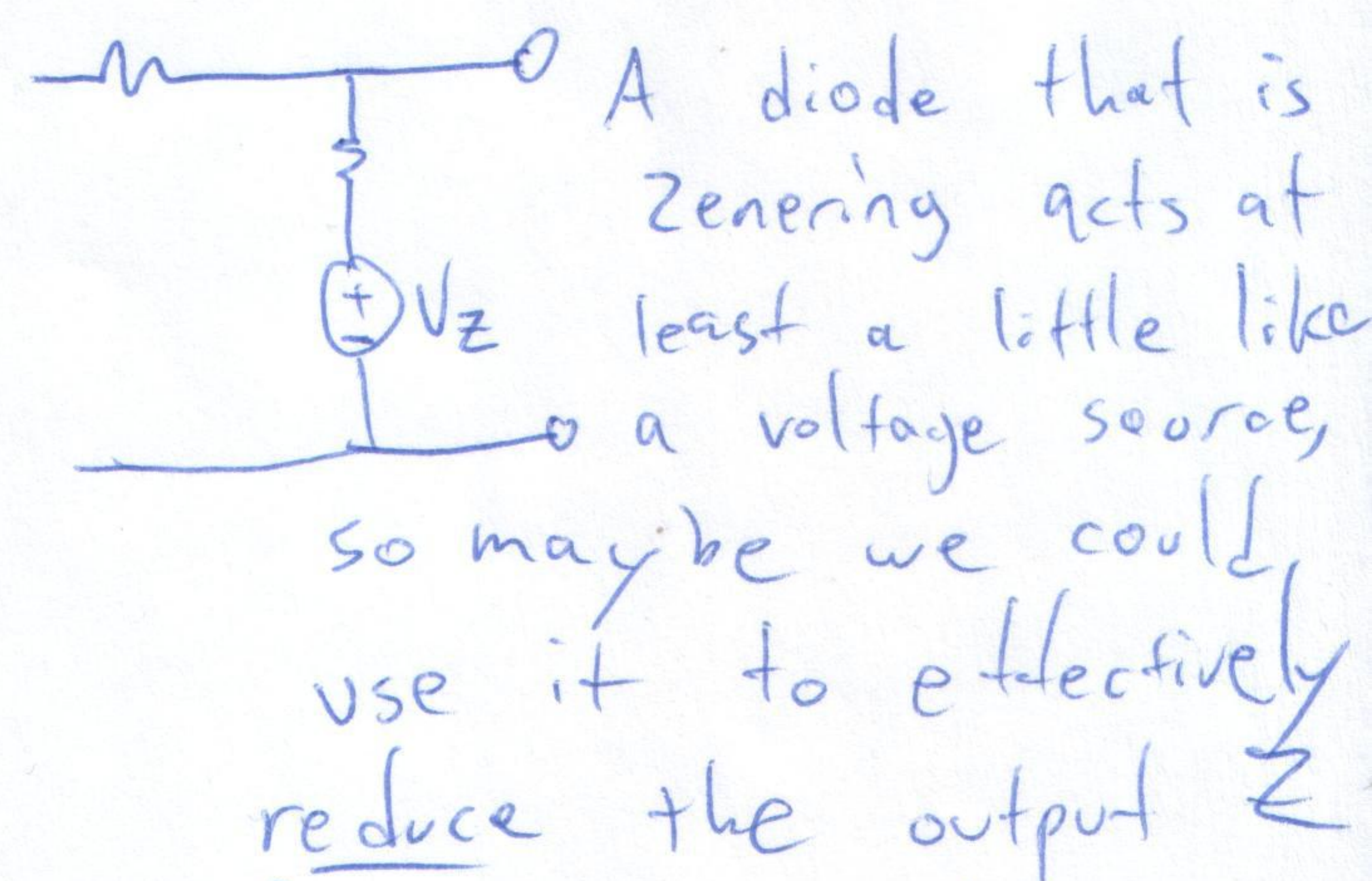

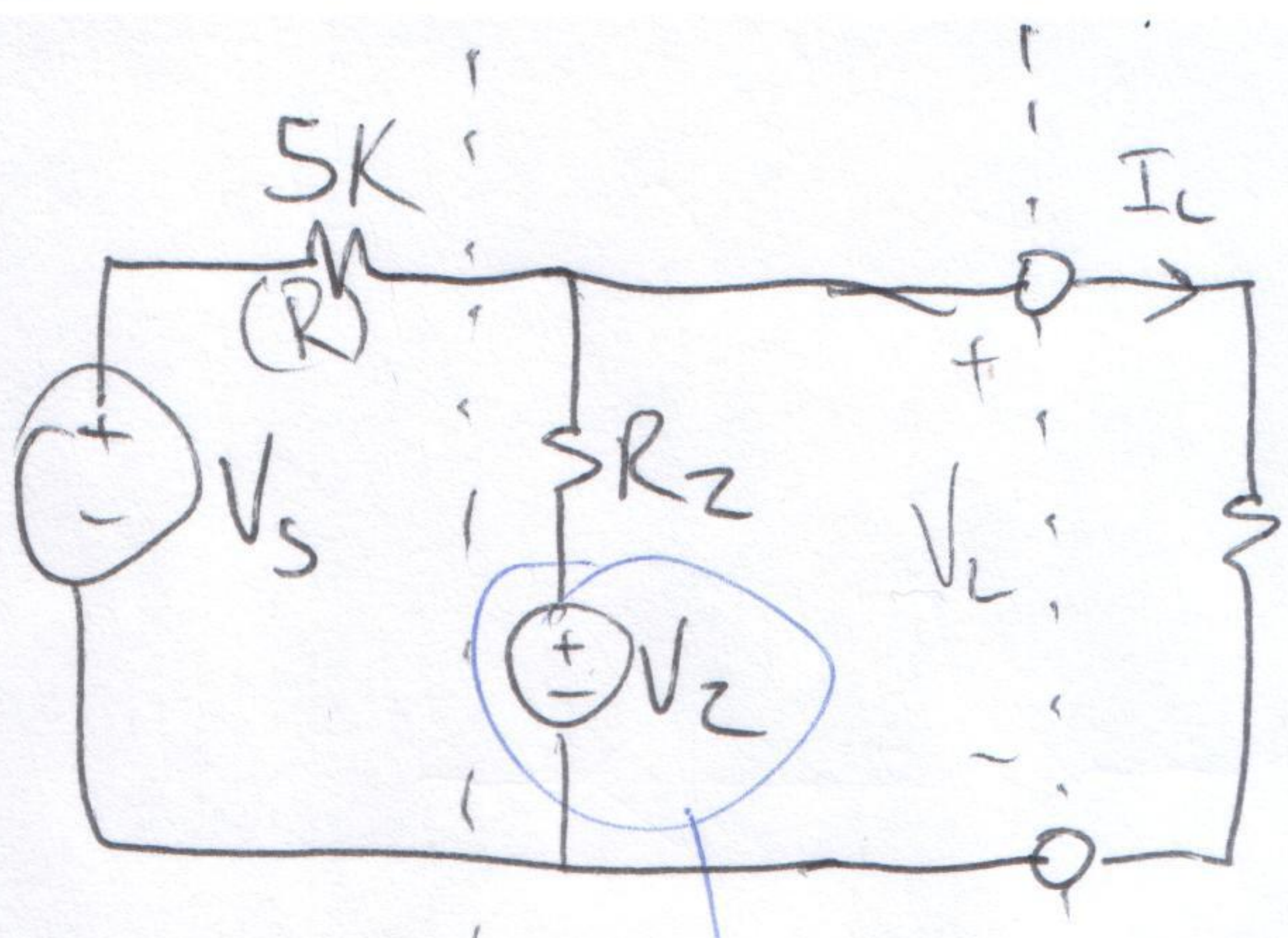A diode that is Zenering acts at least a little like a voltage source, so maybe we could use it to effectively reduce the output Σ of a power supply --- Or hold it steady over input V_s .



Line Regulation

Load Regulation

$$\frac{\partial V_L}{\partial V_S}$$

$$\frac{\partial V_L}{\partial I_L}$$

Assume $R_L \rightarrow \infty$

V_S might change!

handy constant V

V_{out}

$$V_L = V_Z + R_Z \cdot \frac{V_S - V_Z}{R + R_Z}$$

$$= V_Z \left(1 - \frac{1}{R + R_Z}\right) + V_S \underbrace{\frac{R_Z}{R + R_Z}}_{\text{slope!}}$$

$$\frac{\partial V_L}{\partial V_S} = \frac{R_Z}{R + R_Z}$$

good reg: $R_Z \ll R$

$\frac{\partial V_L}{\partial I_L}$: R_L , varying

$$V_L = V_S - R \left(I_L + \frac{V_L - V_Z}{R_Z} \right)$$

~~$V_L = V_Z$~~

~~$$V_L = V_S - R I_L - R \frac{V_L - V_Z}{R_Z} + R \frac{V_L - V_Z}{R_Z}$$~~

$$V_L = V_S - R I_L + \frac{R}{R_Z} V_Z - \frac{R}{R_Z} V_L$$

~~$$V_L (1 + \frac{R}{R_Z}) = V_S - R I_L + R \frac{V_Z}{R_Z}$$~~

$$V_L \left(1 + \frac{R}{R_Z}\right) = V_S - R I_L + \frac{R}{R_Z} V_Z$$

~~$$V_L = \frac{1}{1 + \frac{R}{R_Z}} V_S + \frac{\frac{R}{R_Z}}{1 + \frac{R}{R_Z}} V_Z - \frac{R}{1 + \frac{R}{R_Z}} I_L$$~~

$$V_L = \frac{1}{1 + \frac{R}{R_Z}} V_S \left[\frac{R}{1 + \frac{R}{R_Z}} I_L + \frac{\frac{R}{R_Z}}{1 + \frac{R}{R_Z}} V_Z \right]$$


Slope!

$$- \frac{R R_Z}{R + R_Z} \approx - R // R_Z$$






good reg: both small

reciprocal of slope


Half-Wave Rectifier

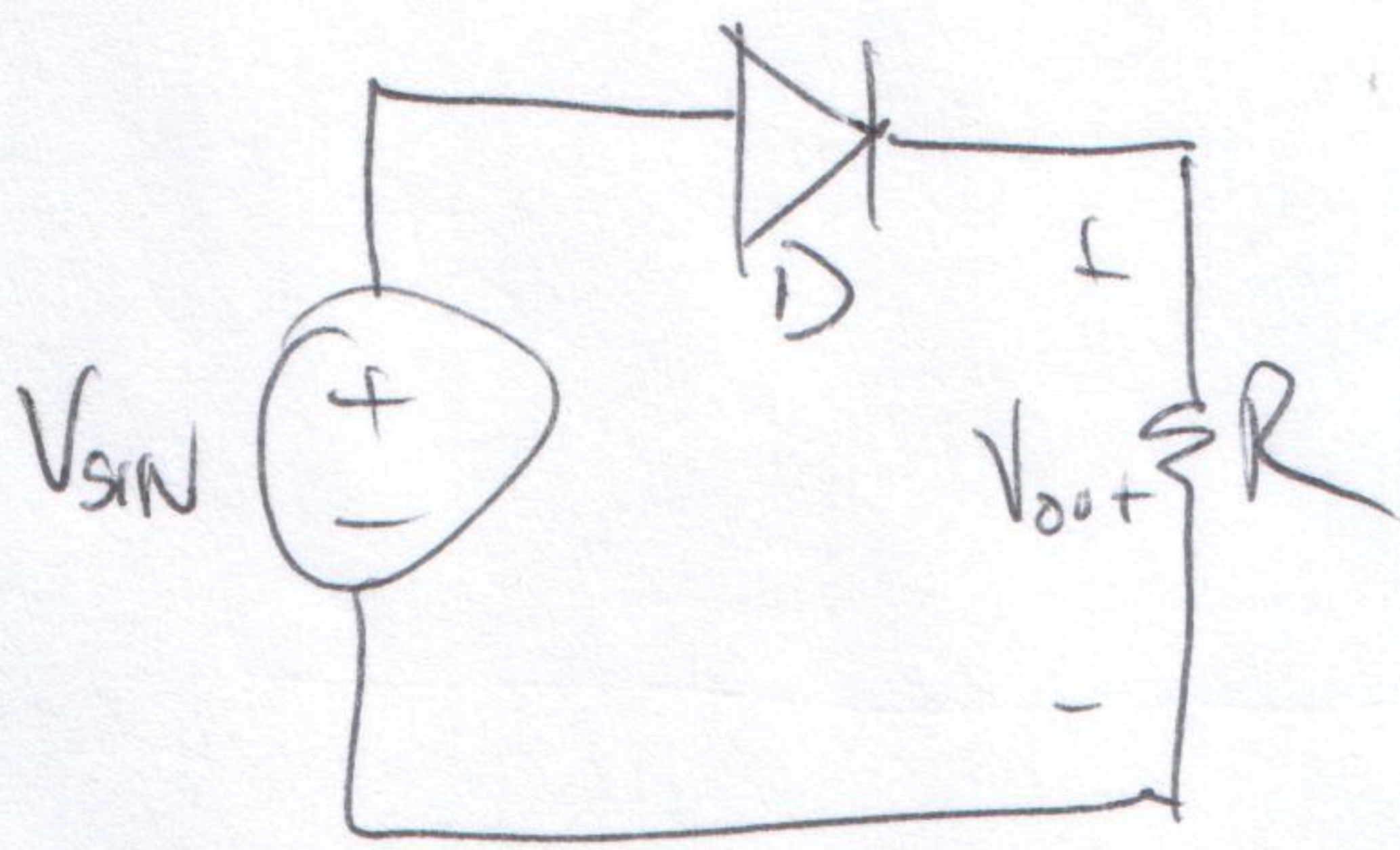

Basic Operation:

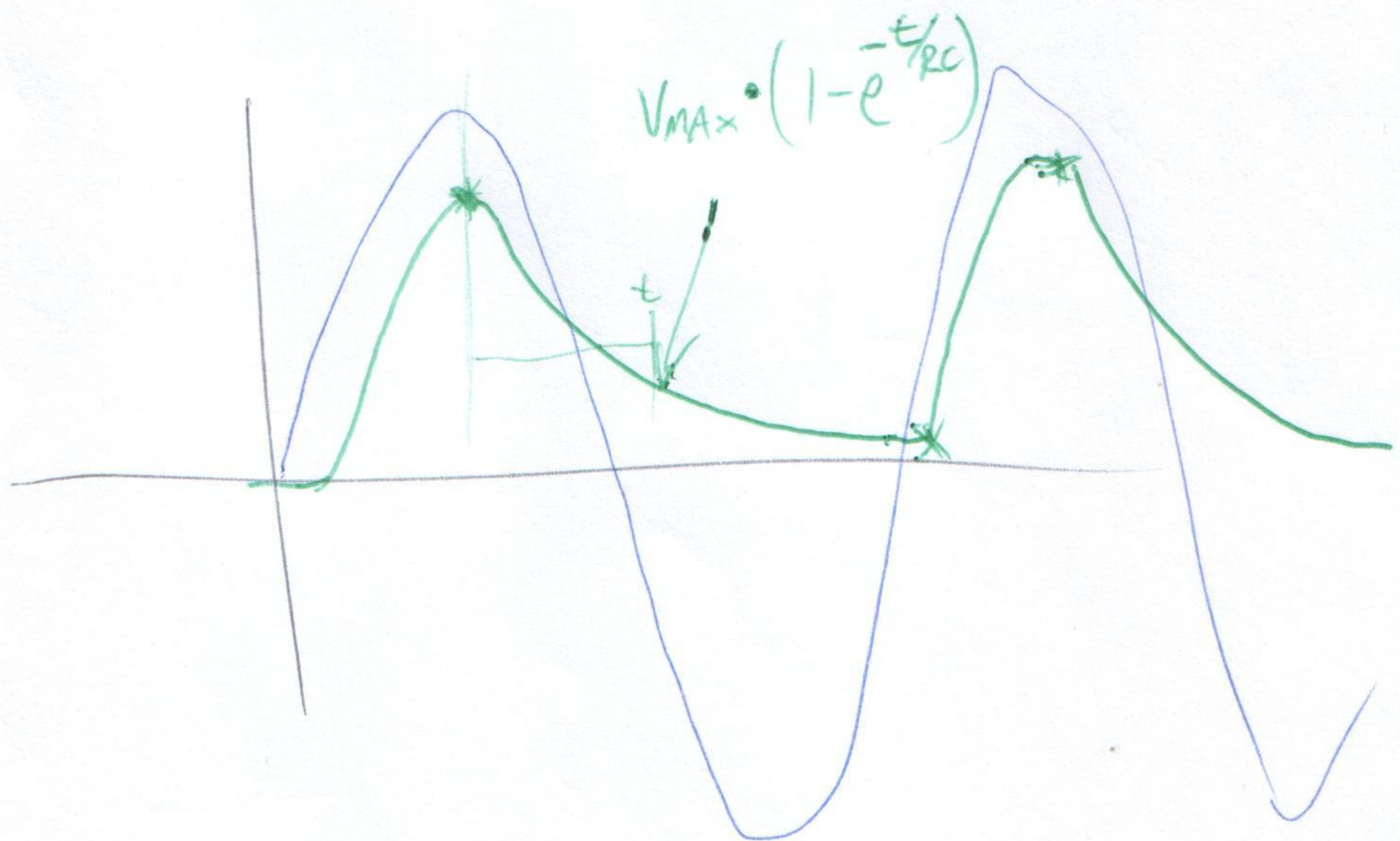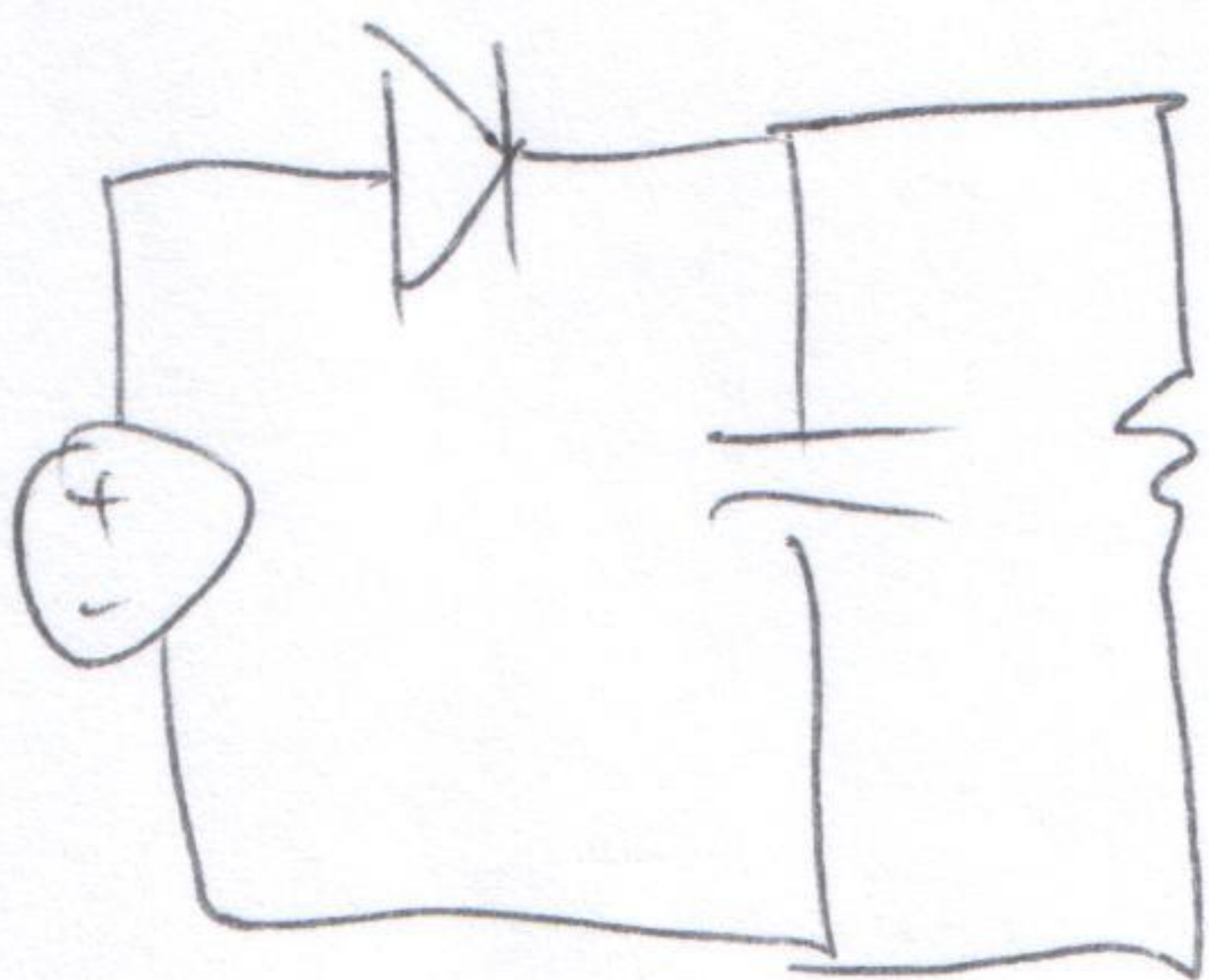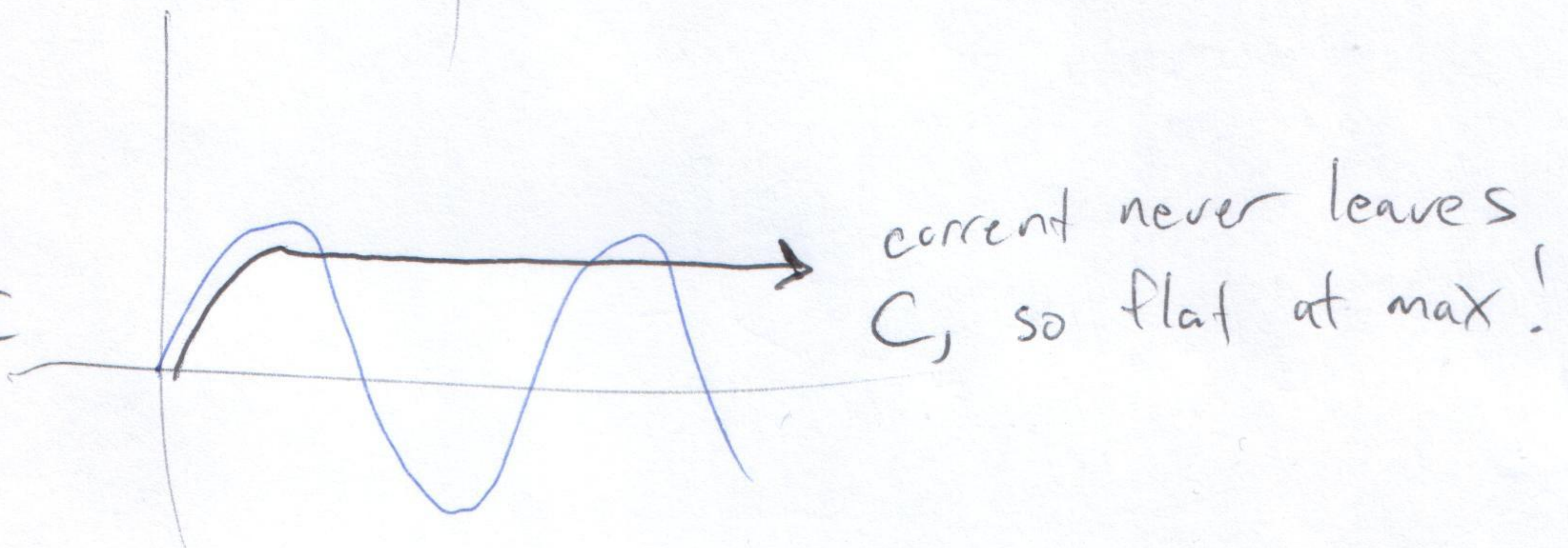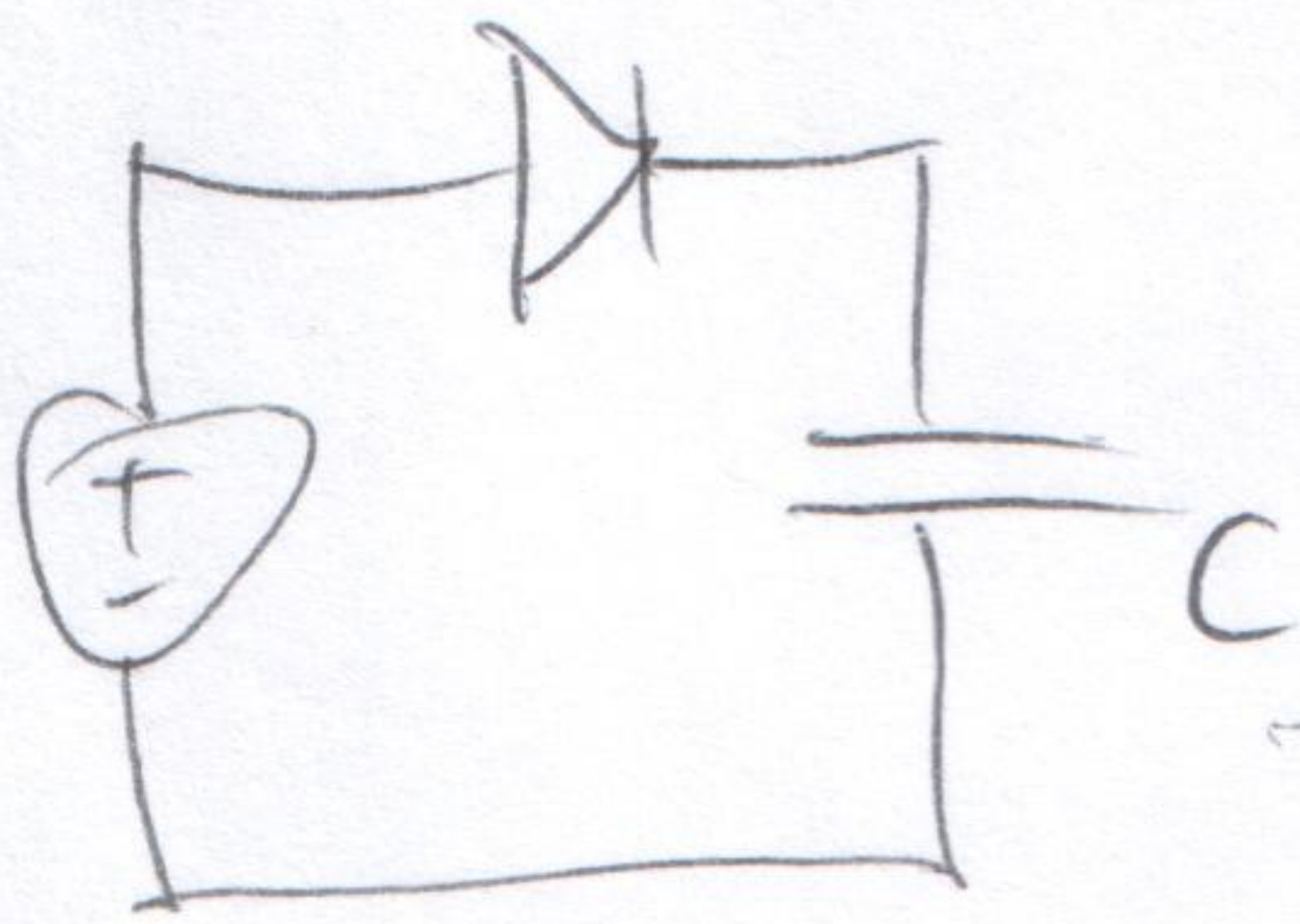
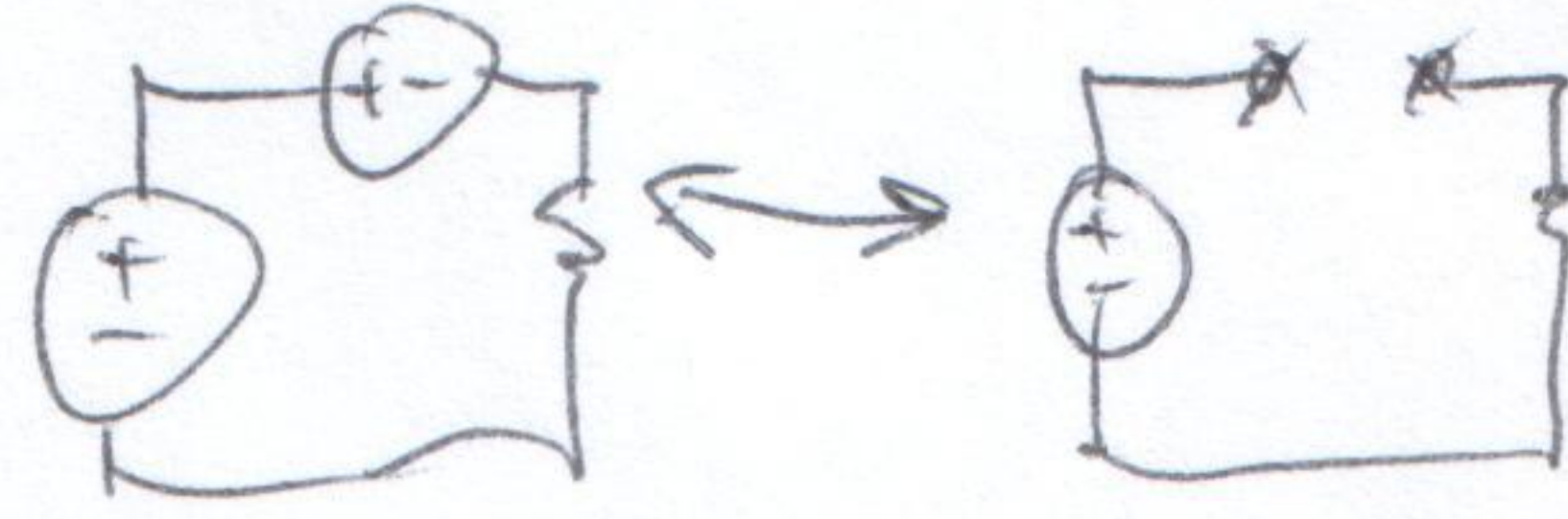


Special Case: $RC \gg \frac{1}{f_{pwr}}$

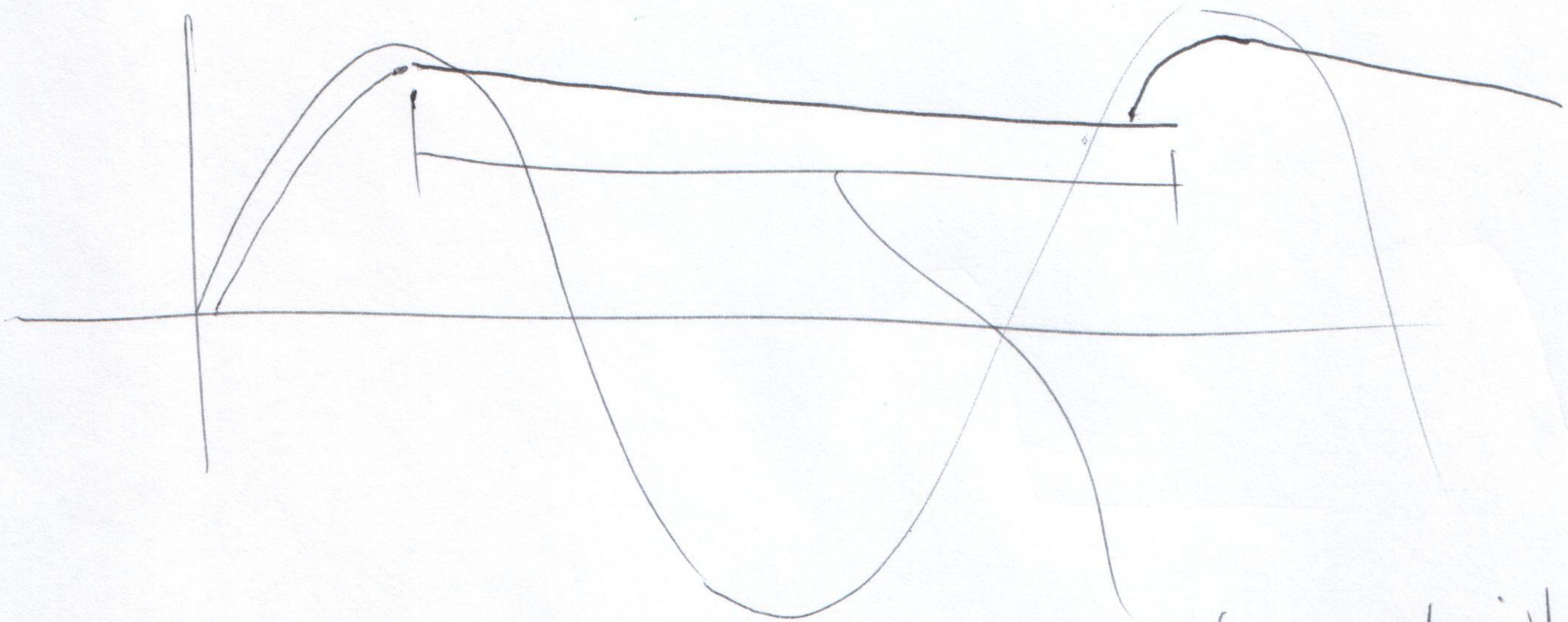

roughly a straight line
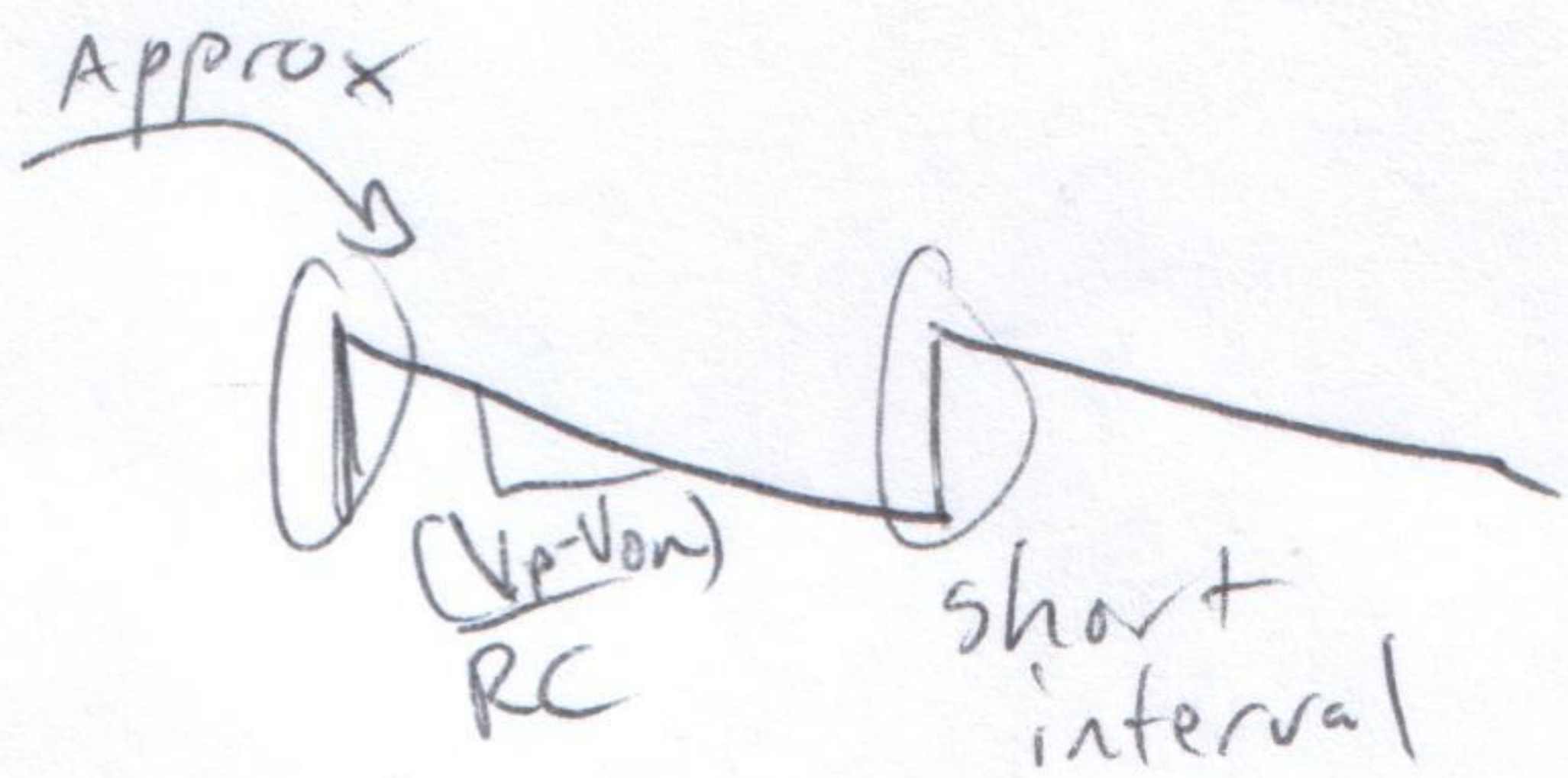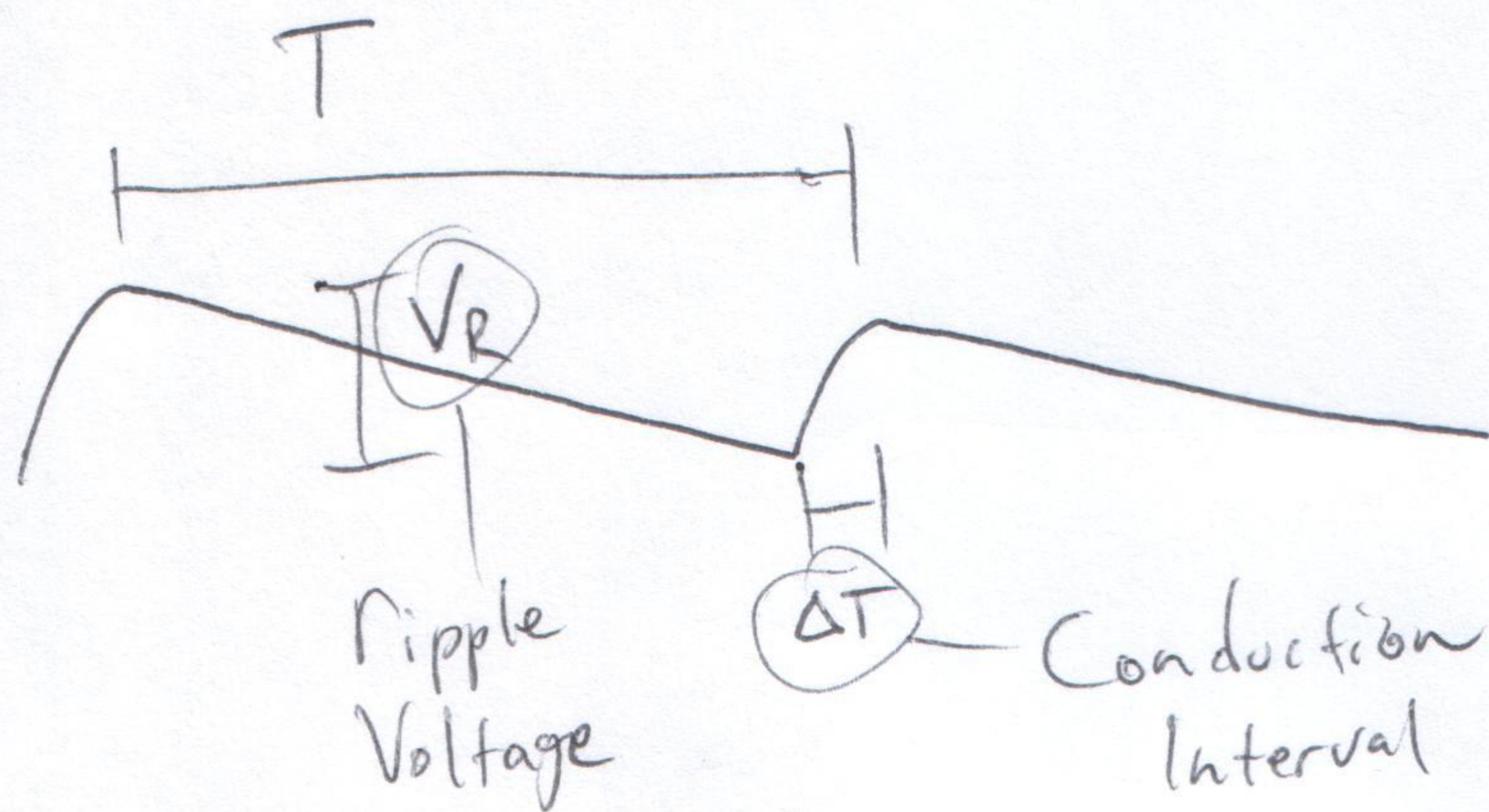
$$\frac{dV}{dt} = \frac{d}{dt} e^{-t/RC} = -\frac{(V_p - V_{on})}{RC}$$



$$V_r = \frac{V_p - V_{on}}{RC} \cdot T$$

— Note: half the power doesn't go anywhere, the AC only pushes a little bit, and C should be very big for heavy loads.

Power brick LED: goes out after you unplug — faster for laptop plugged in.

