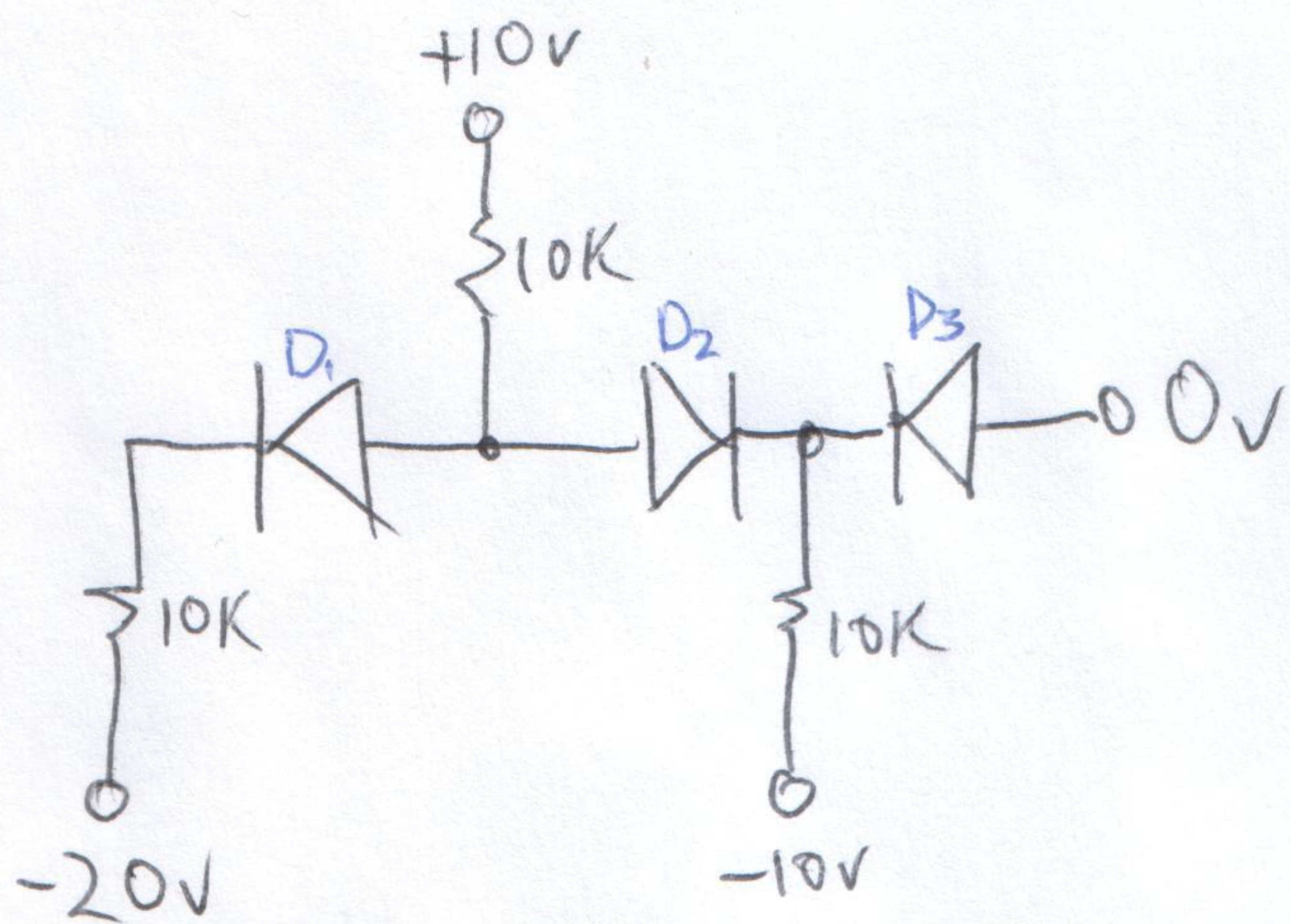



Diodes in Circuits




Possible Set of Modes:

D_1	D_2	D_3
off	off	off
off	off	on
off	on	off
off	on	on
on	off	off
on	off	on
on	on	off
on	on	on

However, intuition can help a lot here.

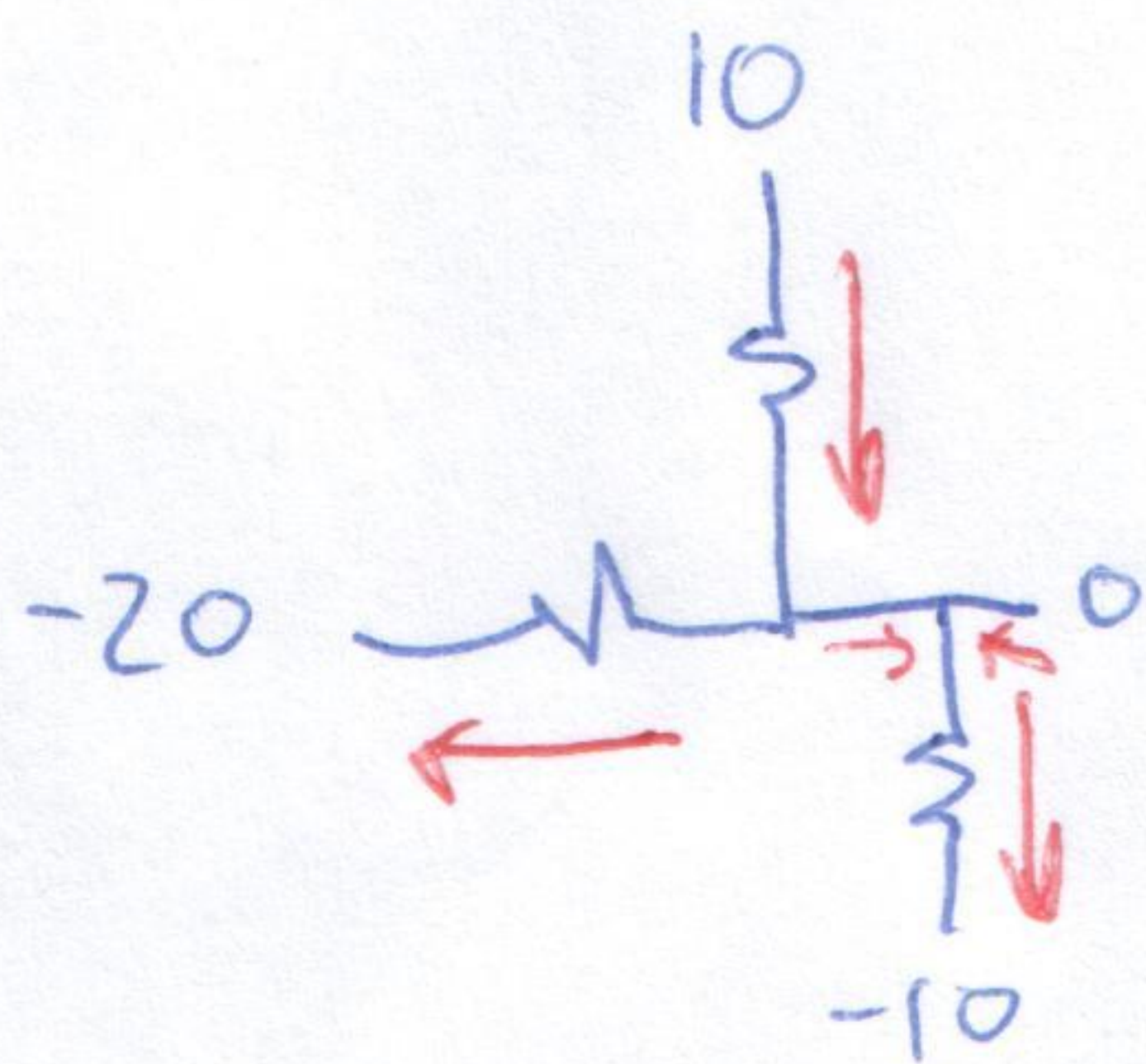


→ Sounds Legit.

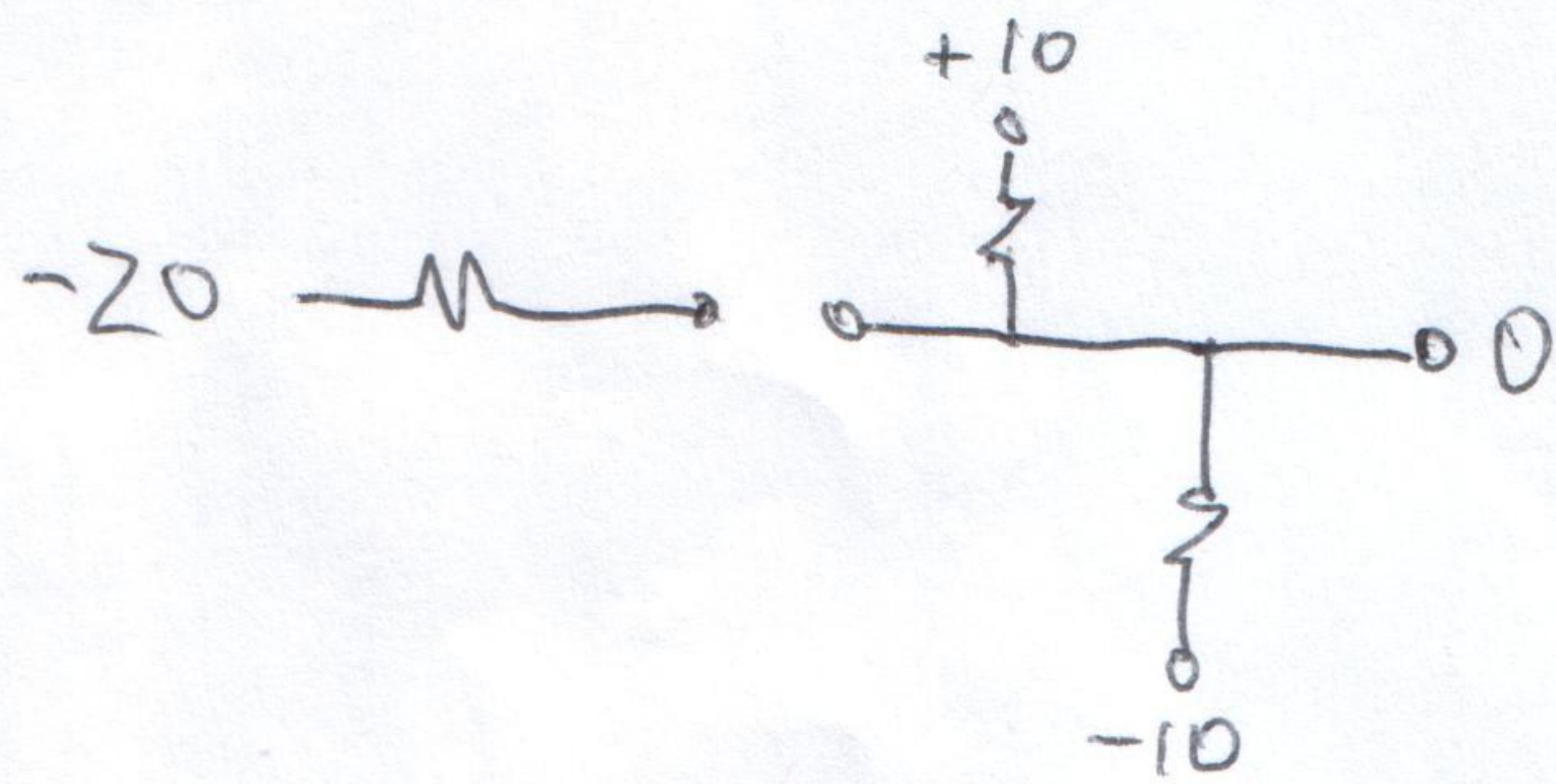


Practice: choosing ~~resistor~~ different diode mode will show +30V across one, obviously F.B.


Regulators I

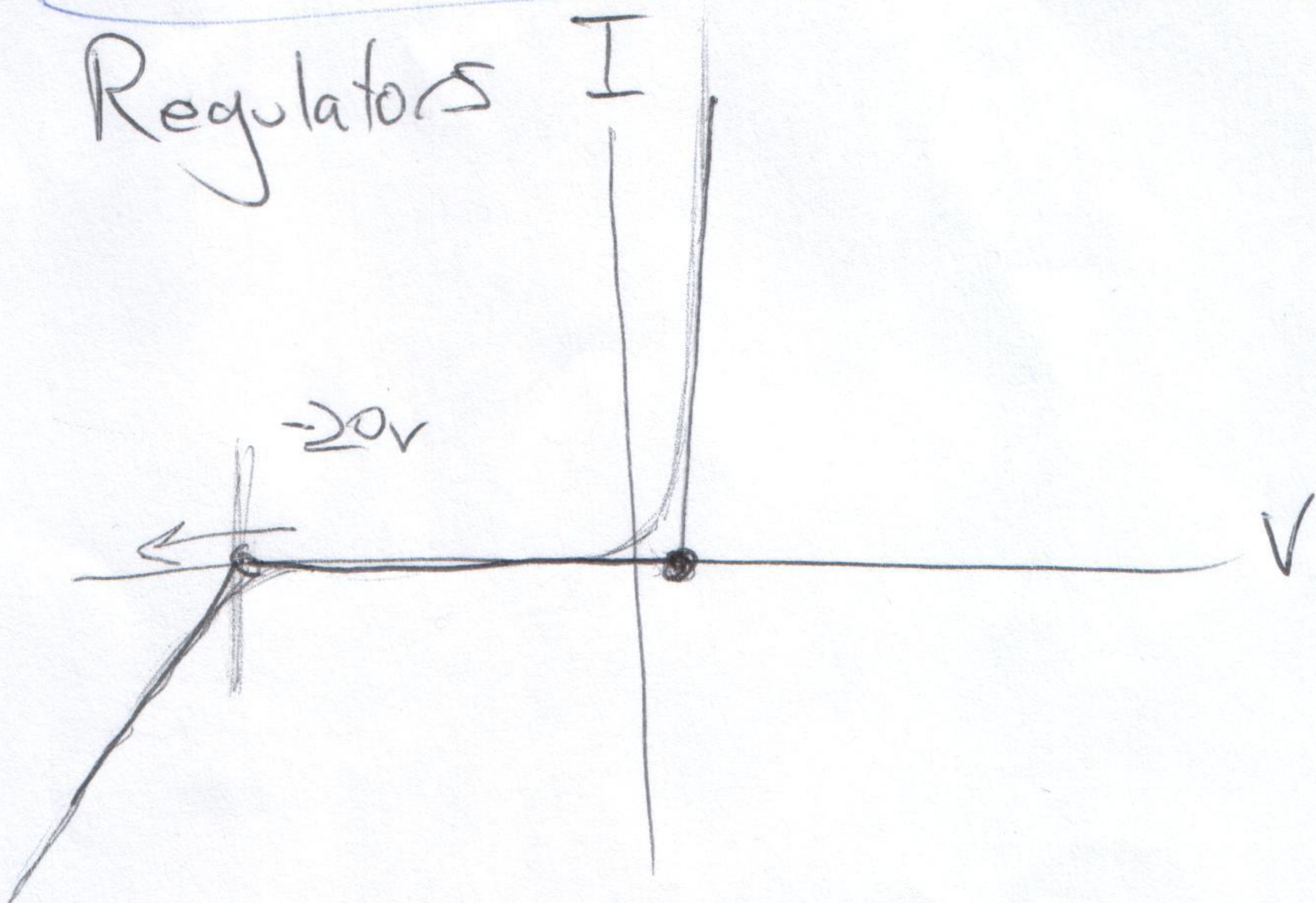

→ Potential use as regulators:

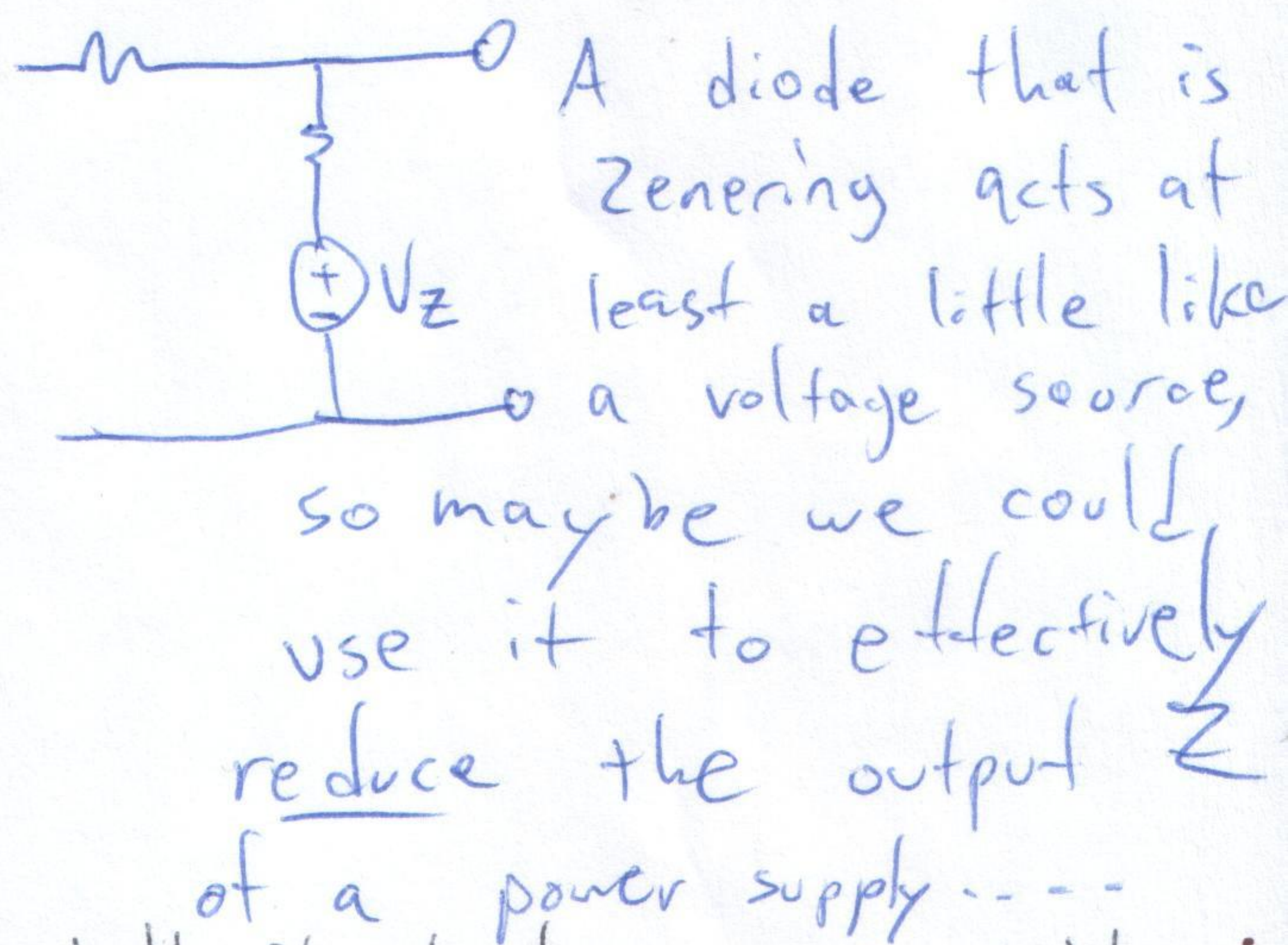

Or hold it steady over input V_s .

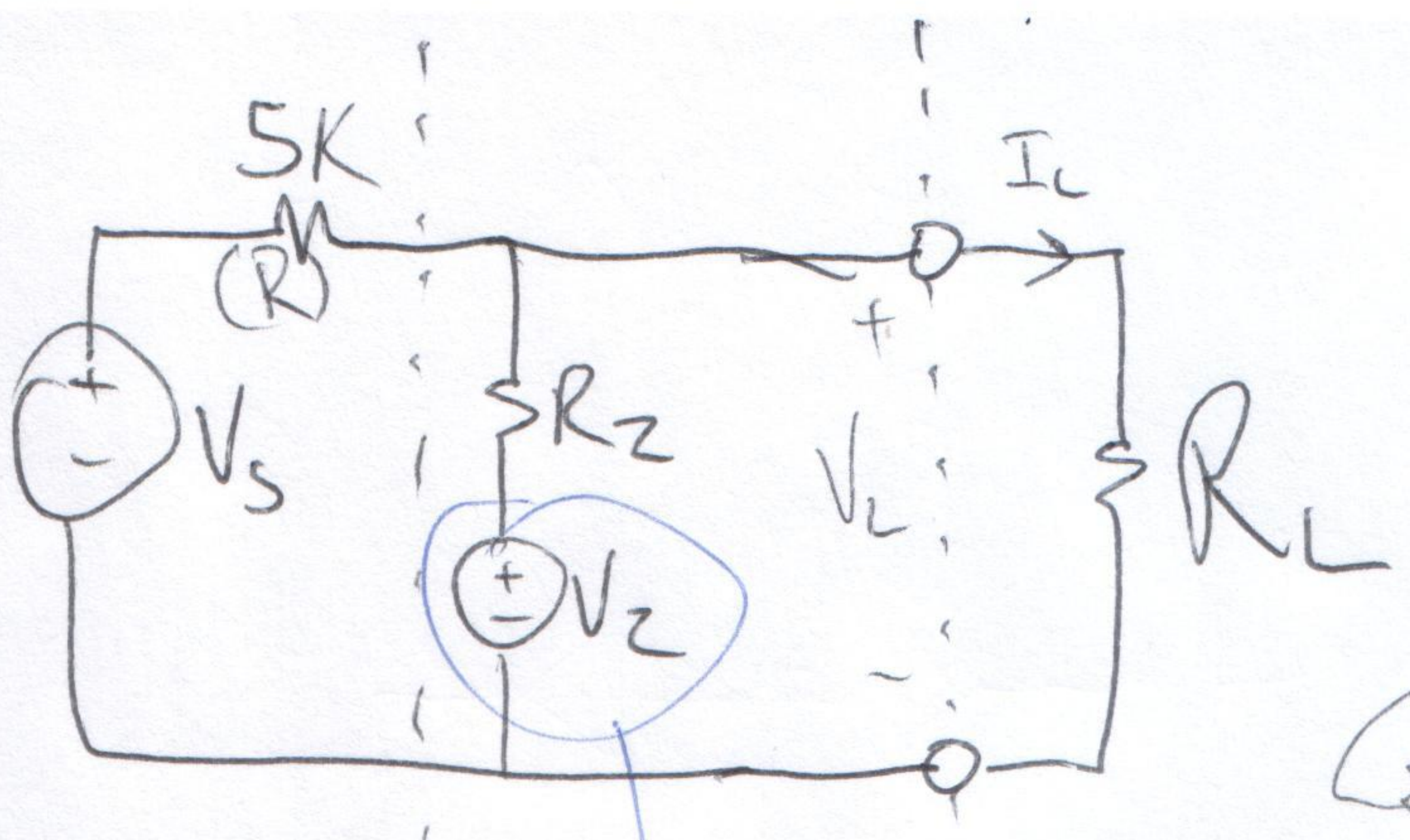

Line Regulation

Load Regulation

$$\frac{\partial V_L}{\partial V_S}$$

$$\frac{\partial V_L}{\partial I_L}$$

Assume $R_L \rightarrow \infty$

V_S might change!

handy constant V

V_{out}

$$V_L = V_Z + R_Z \cdot \frac{V_S - V_Z}{R + R_Z}$$

$$= V_Z \left(1 - \frac{1}{R + R_Z}\right) + V_S \underbrace{\frac{R_Z}{R + R_Z}}_{\text{slope!}}$$

$$\frac{\partial V_L}{\partial V_S} = \frac{R_Z}{R + R_Z}$$

good reg: $R_Z \ll R$

$\frac{\partial V_L}{\partial I_L}$: R_L , varying

$$V_L = V_S - R \left(I_L + \frac{V_L - V_Z}{R_Z} \right)$$

$$V_L = V_S - R I_L + \frac{R}{R_Z} V_Z - \frac{R}{R_Z} V_L$$

$$V_L \left(1 + \frac{R}{R_Z}\right) = V_S - R I_L + \frac{R}{R_Z} V_Z$$

$$V_L = \frac{1}{1 + \frac{R}{R_Z}} V_S - \frac{R}{1 + \frac{R}{R_Z}} I_L + \frac{R/R_Z}{1 + \frac{R}{R_Z}} V_Z$$

Slope!

$$- \frac{R R_Z}{R + R_Z} \approx - R / R_Z$$

good reg: both small


~~$V_L = V_S - R I_L - \frac{R R_Z}{R + R_Z} V_L + \frac{R R_Z}{R + R_Z} V_Z$~~

~~$V_L (1 + \frac{R R_Z}{R + R_Z}) = V_S - R I_L + \frac{R R_Z}{R + R_Z} V_Z$~~






~~$V_L = \frac{1}{1 + \frac{R R_Z}{R + R_Z}} V_S + \frac{R R_Z}{1 + \frac{R R_Z}{R + R_Z}} V_Z - \frac{R}{1 + \frac{R R_Z}{R + R_Z}} I_L$~~

reciprocal of slope


Half-Wave Rectifier

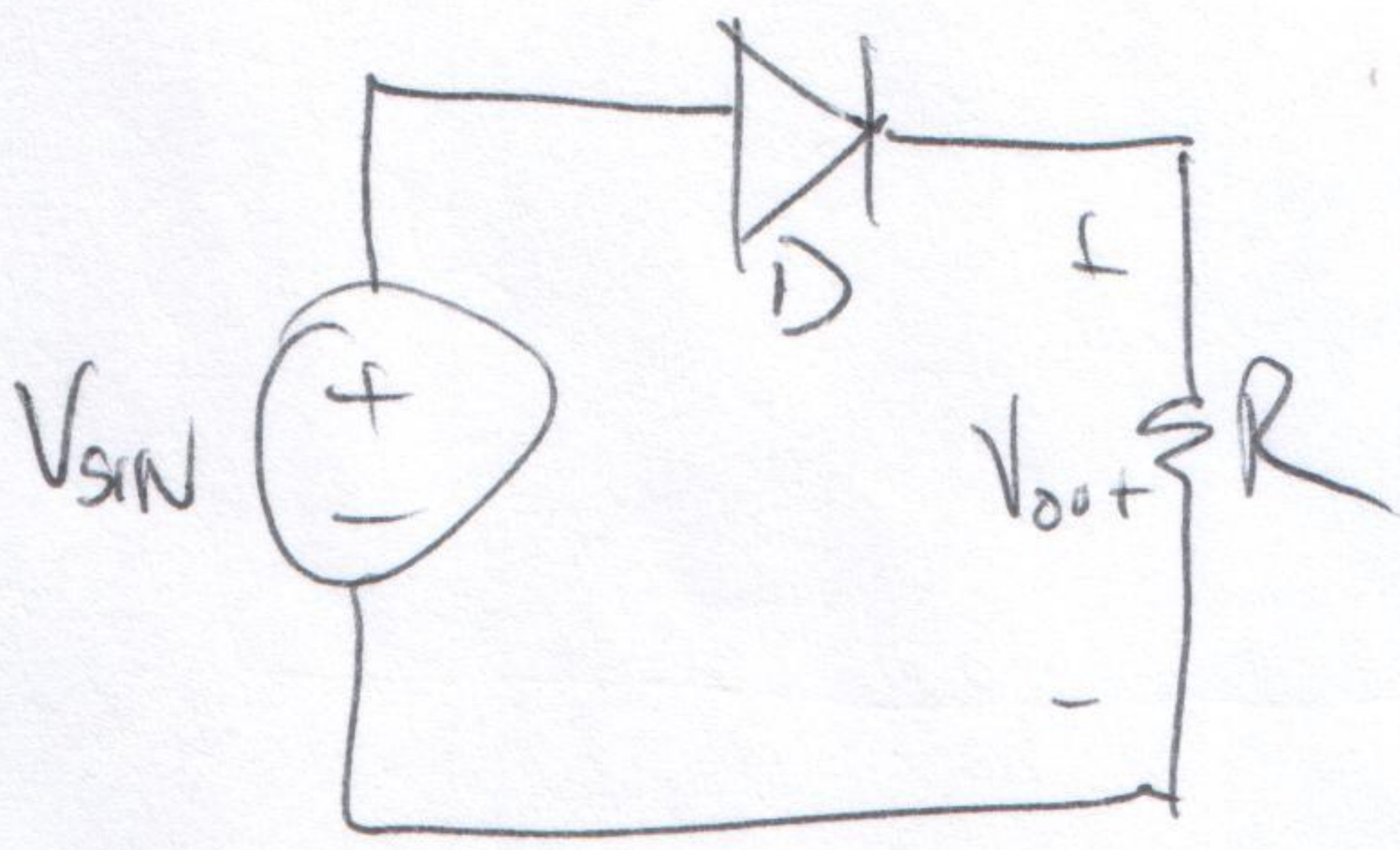

Basic Operation:

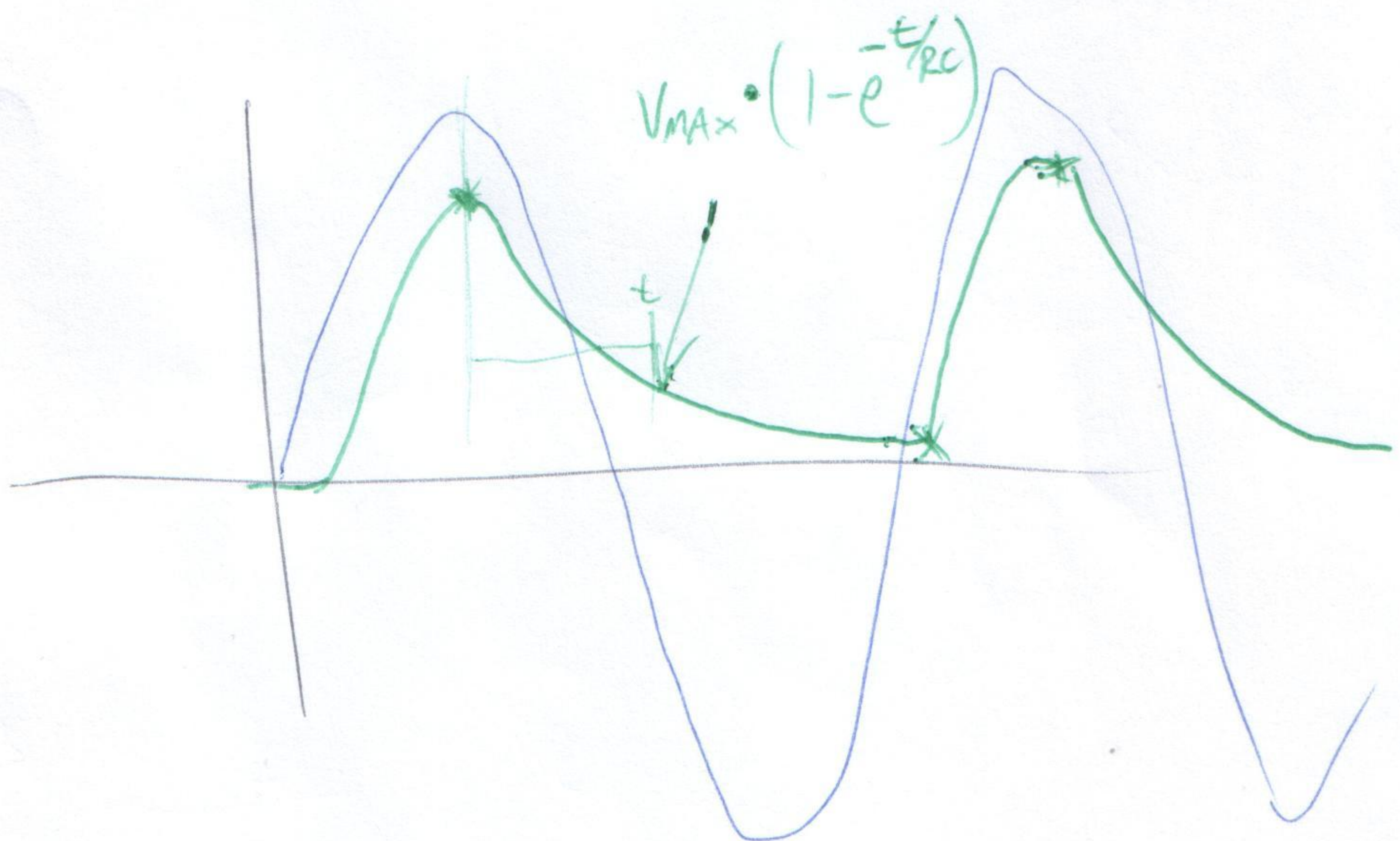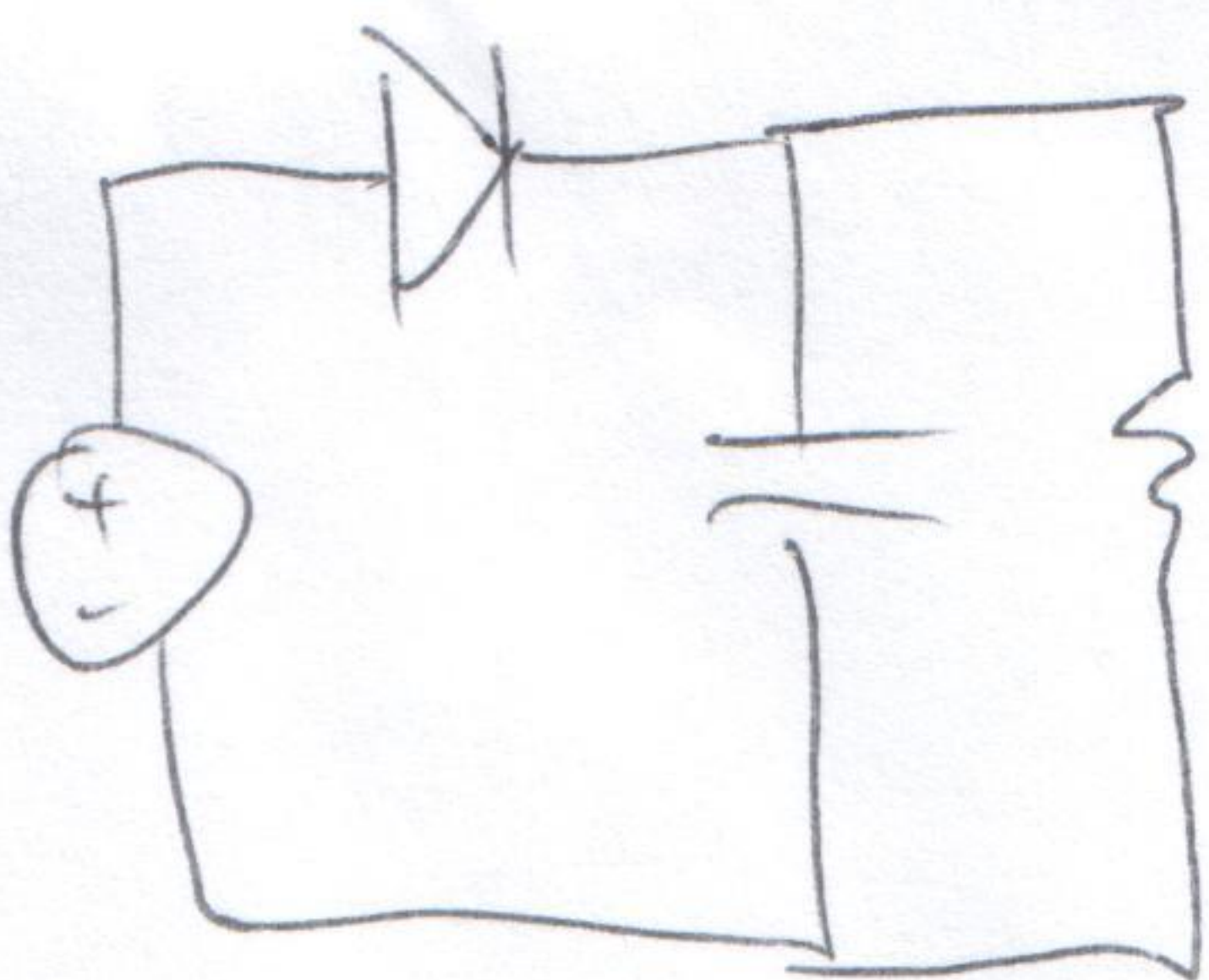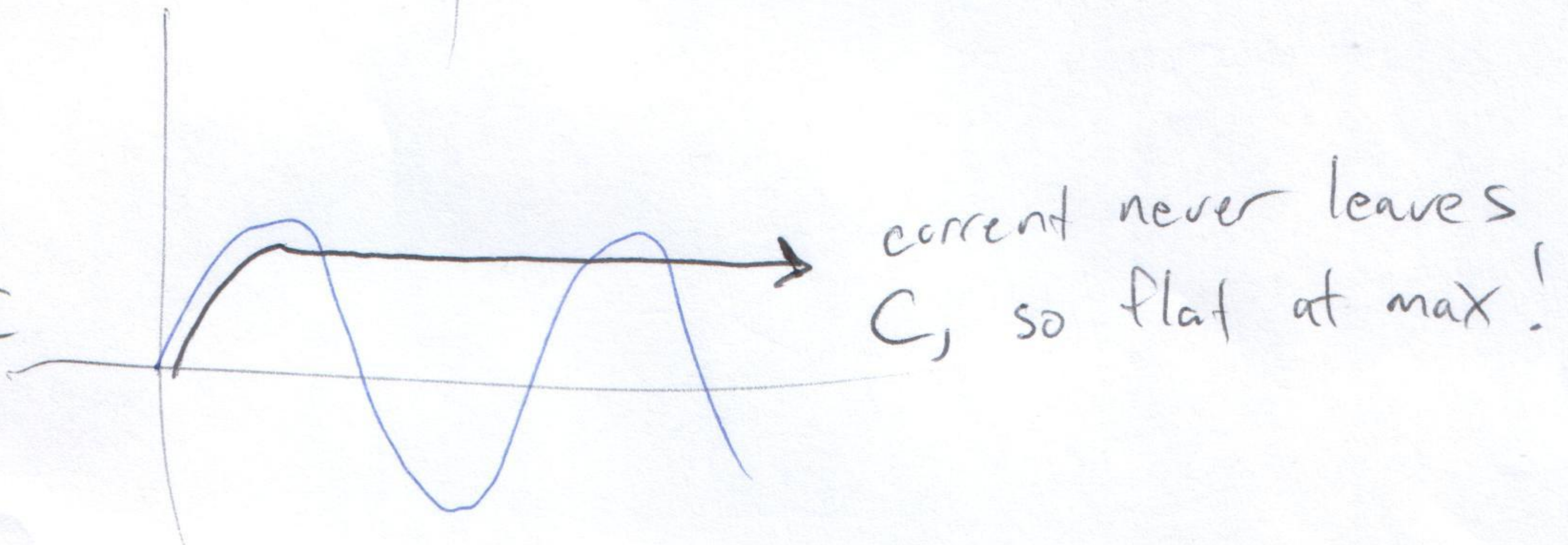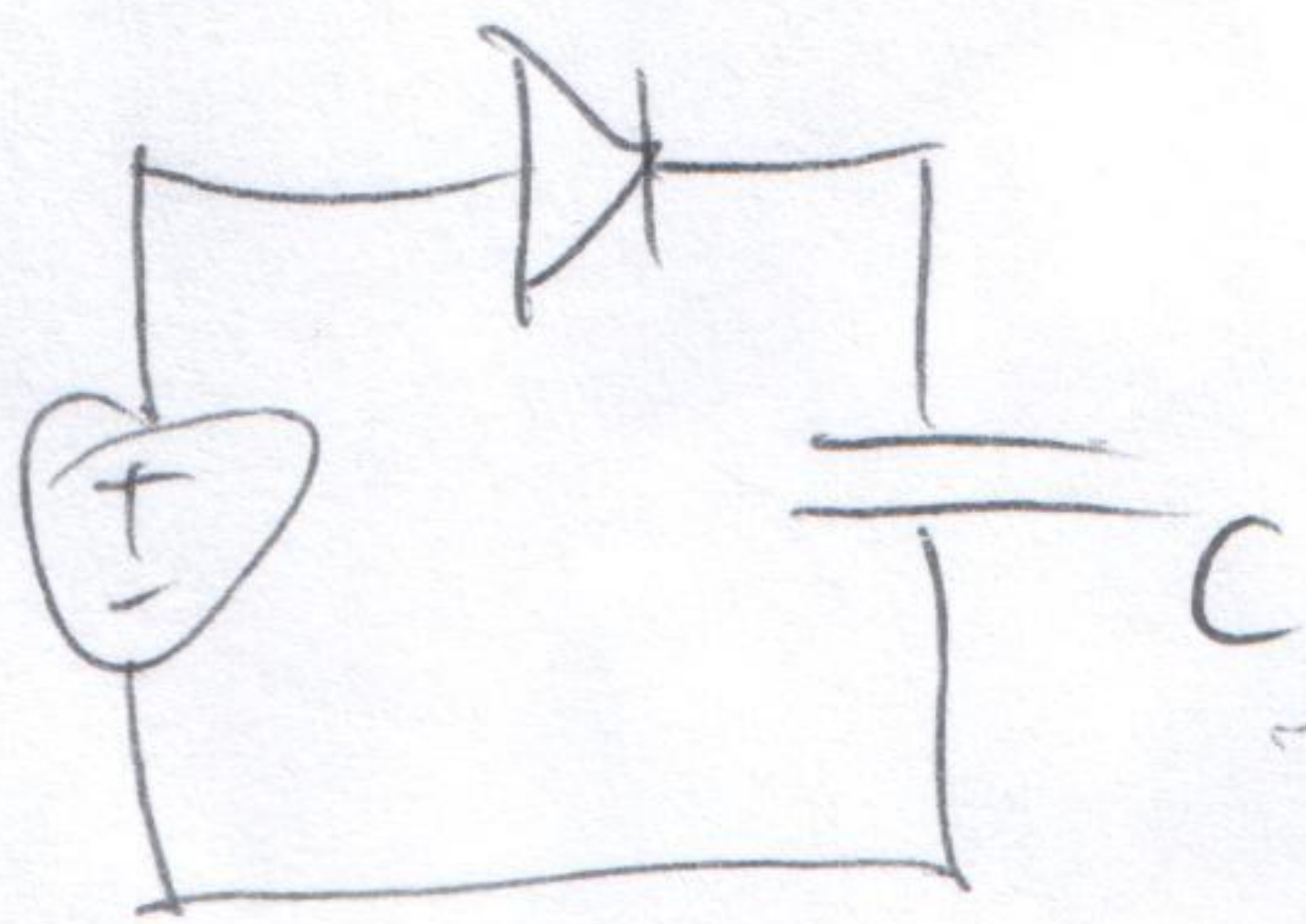
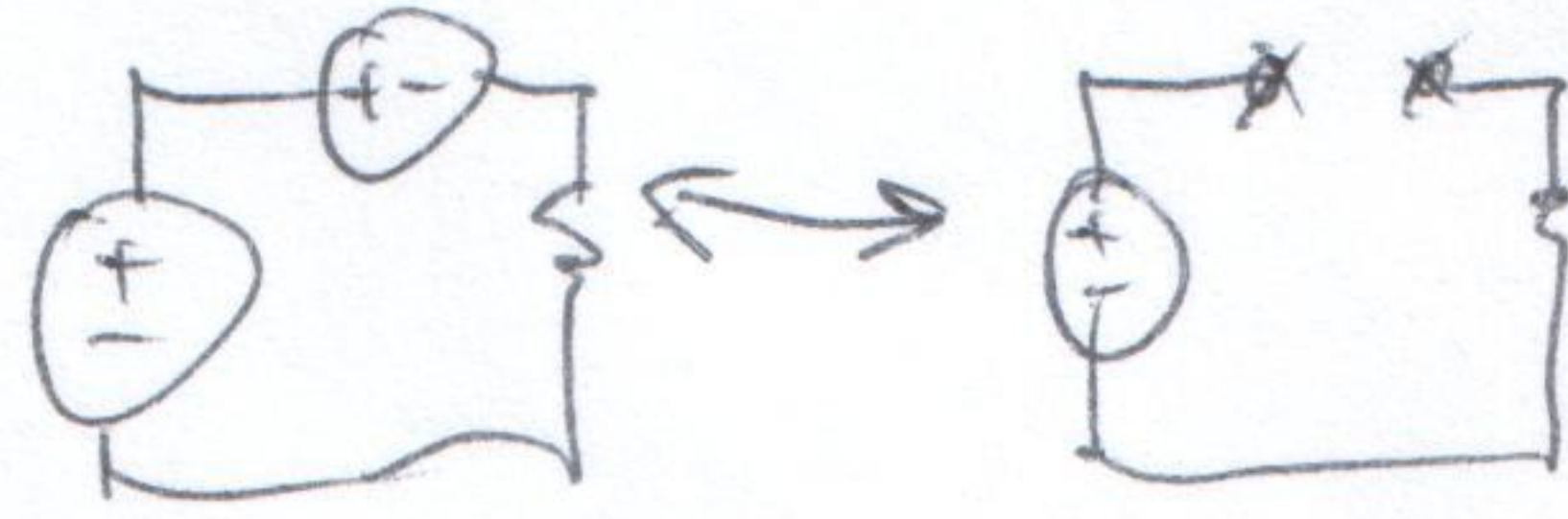


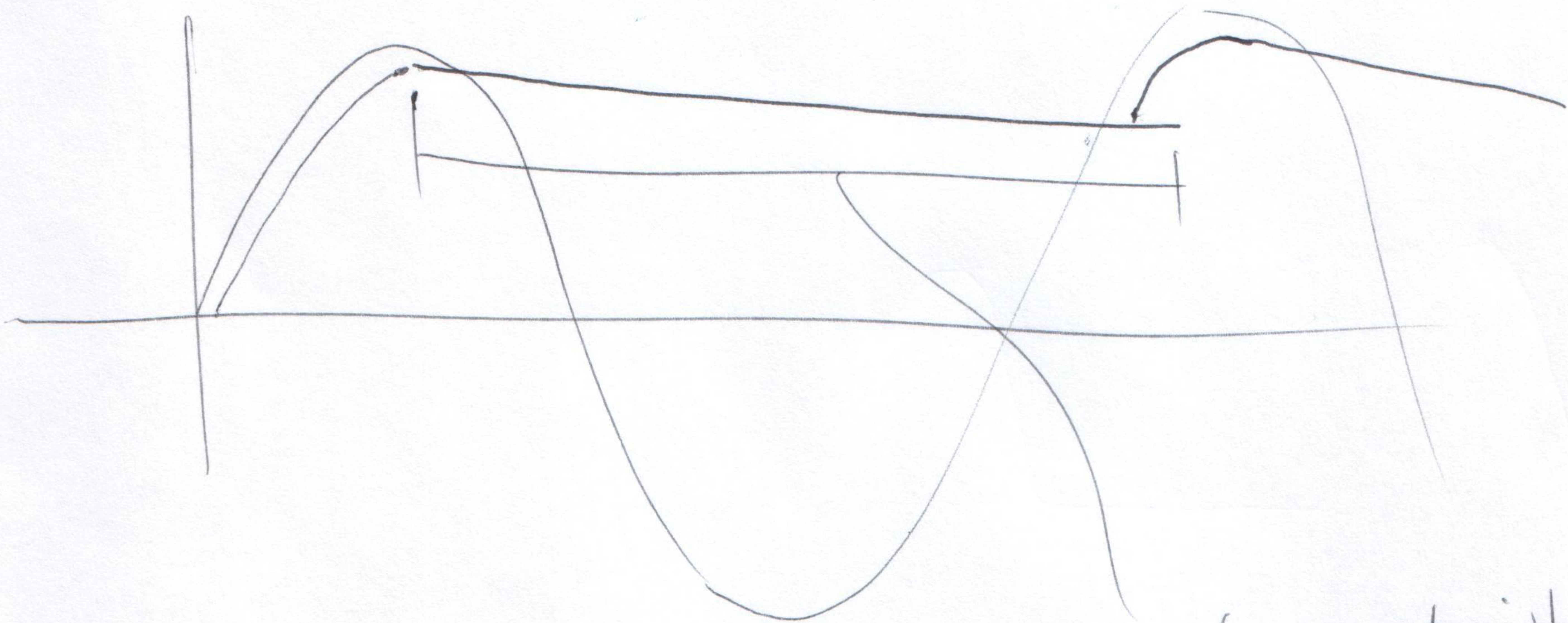Special Case: $RC \gg \frac{1}{f_{\text{power}}}$



roughly a straight line

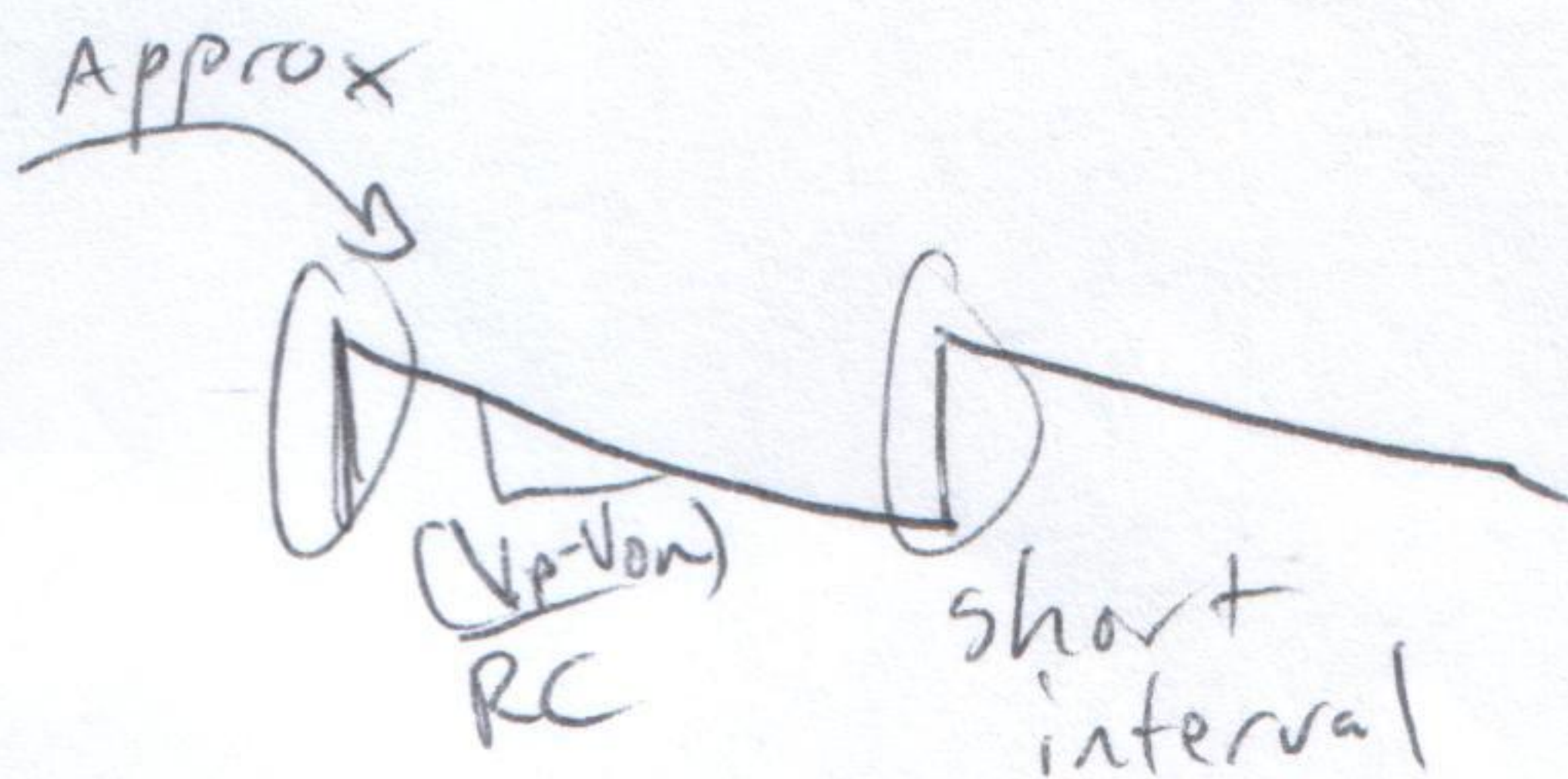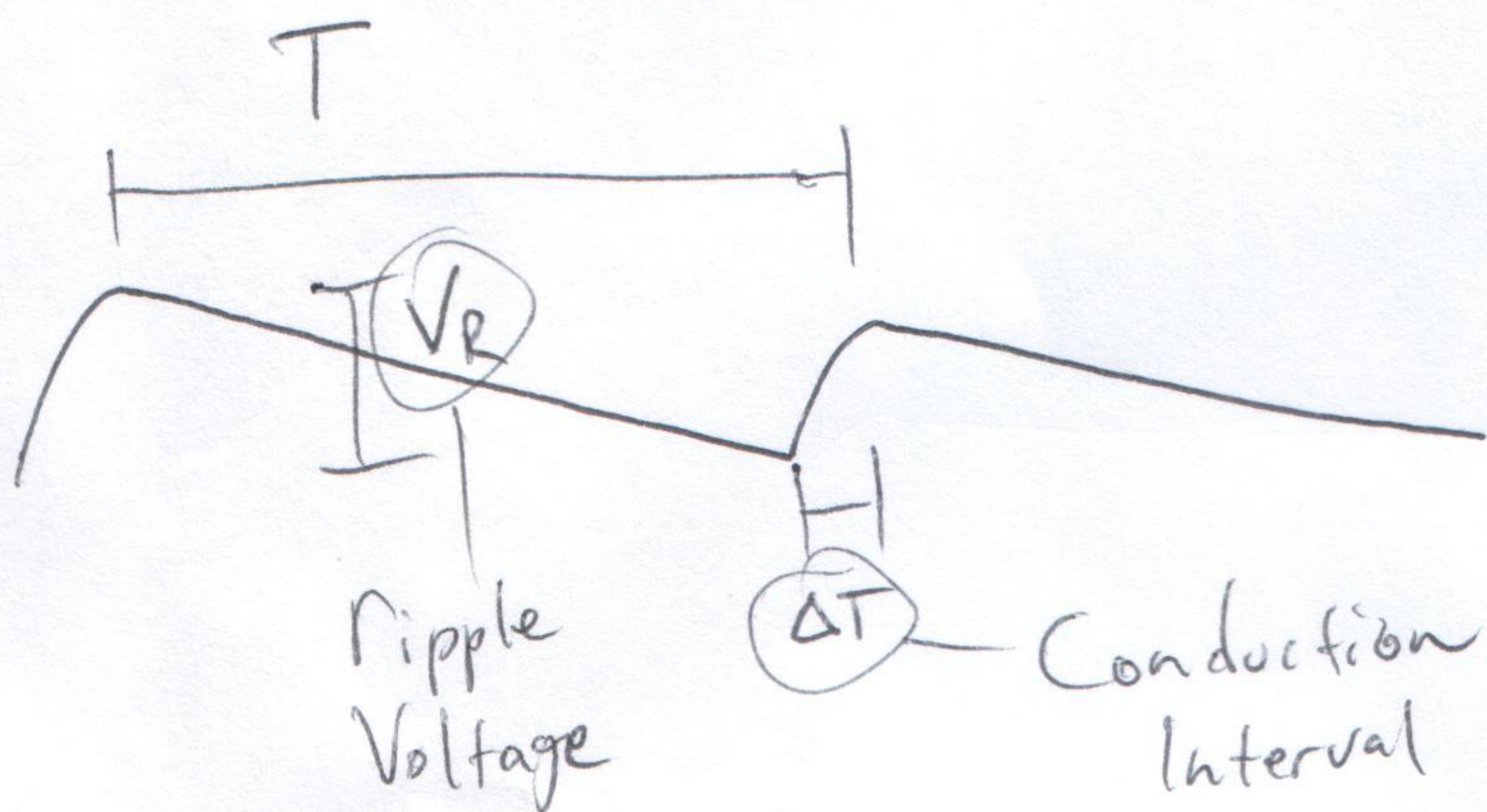
$$\frac{dV}{dt} = \frac{d}{dt} e^{-t/RC} = -\frac{(V_p - V_{on})}{RC}$$




$$V_r = \frac{V_p - V_{on}}{RC} \cdot T$$

— Note: half the power doesn't go anywhere, the AC only pushes a little bit, and C should be very big for heavy loads.

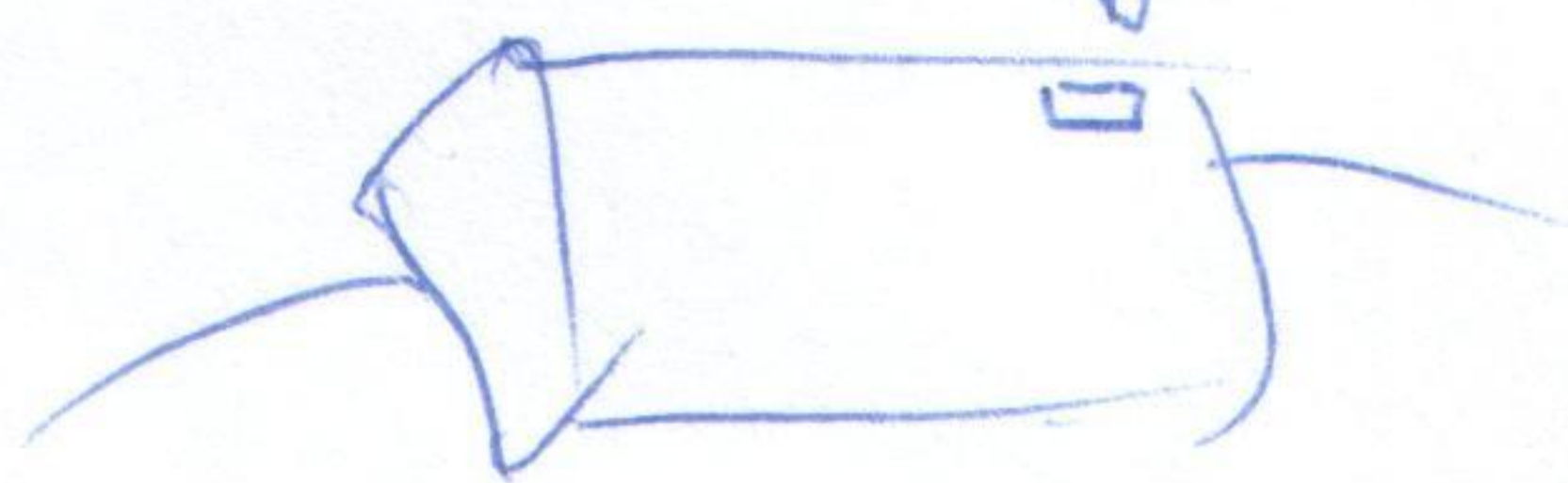Power brick LED: goes out after you unplug — faster for laptop plugged in.




Regulators: In Depth

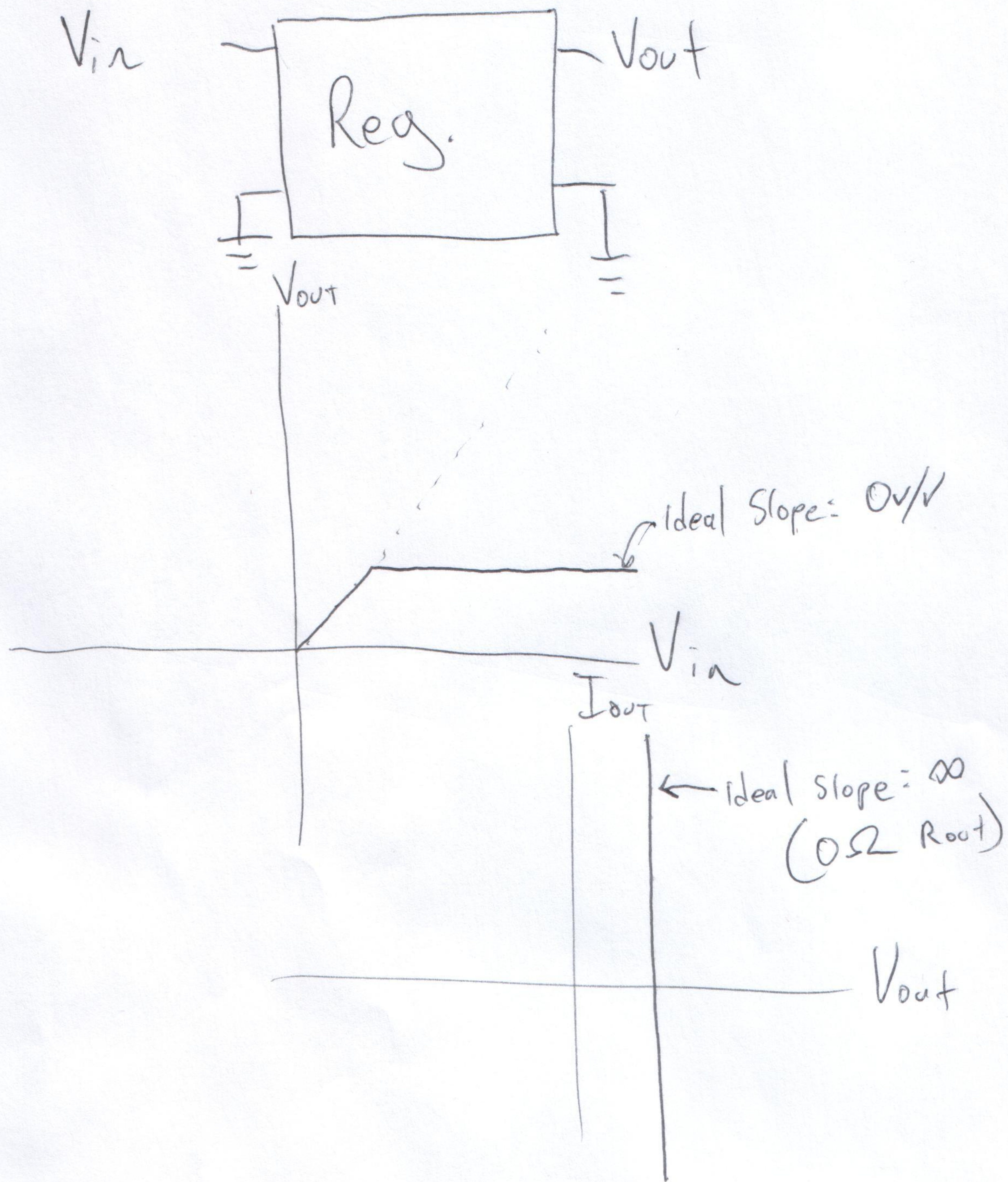


Important Reason to use nonlinear Circuits:

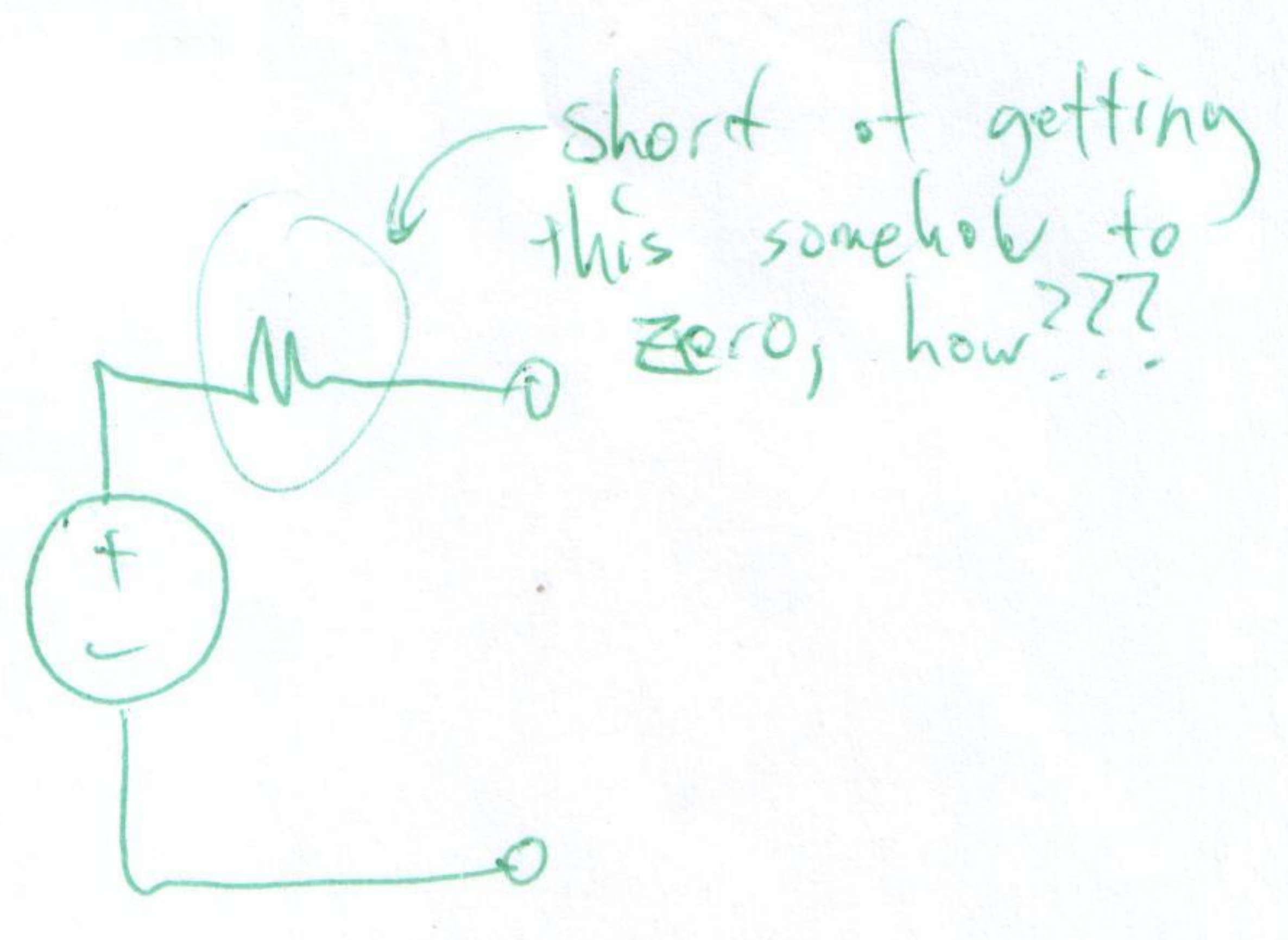Resistors are terrible at meeting either goal without using tons of power and/or failing at least one goal.





Complex circuits can not only achieve very good regulation numbers but also reference the band gap energy - directly - which is amazing and also beyond the scope of this course.

So let's make a simple one:


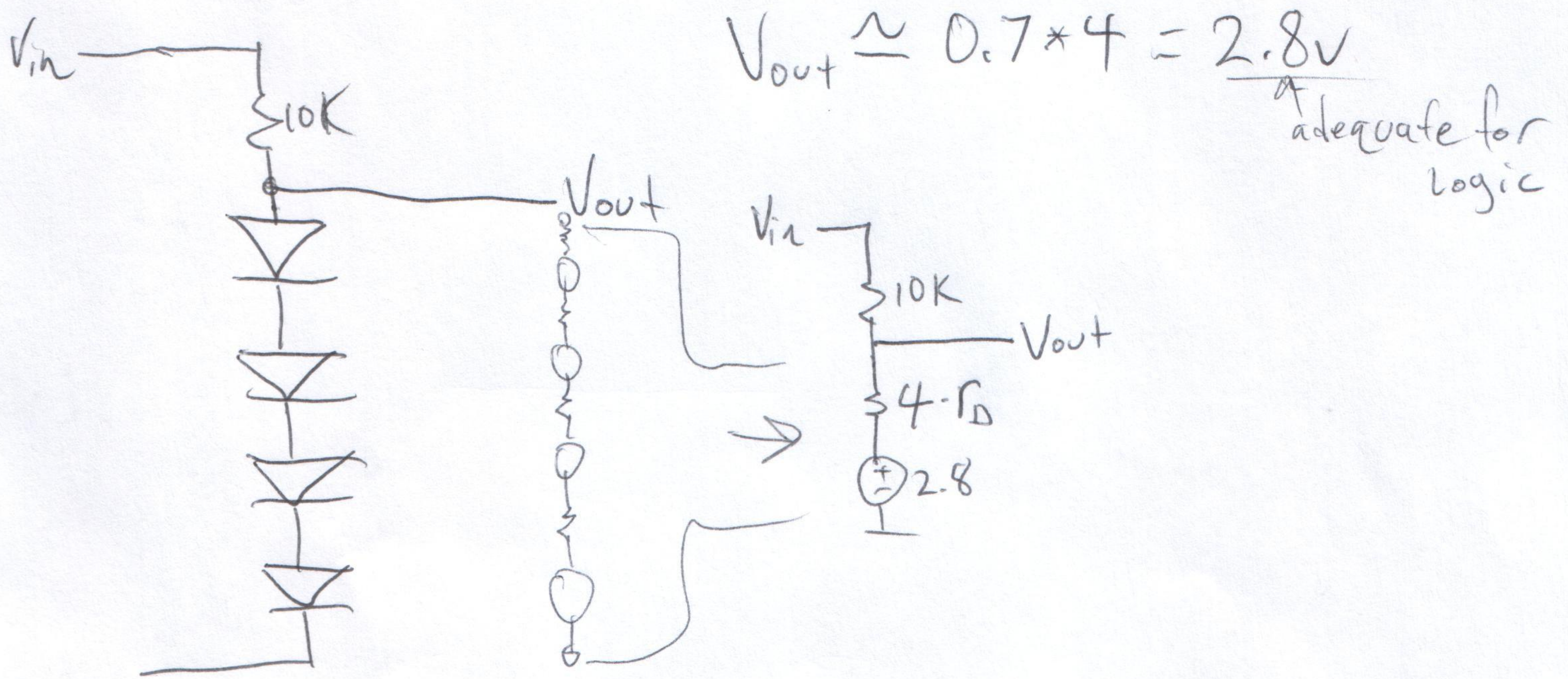


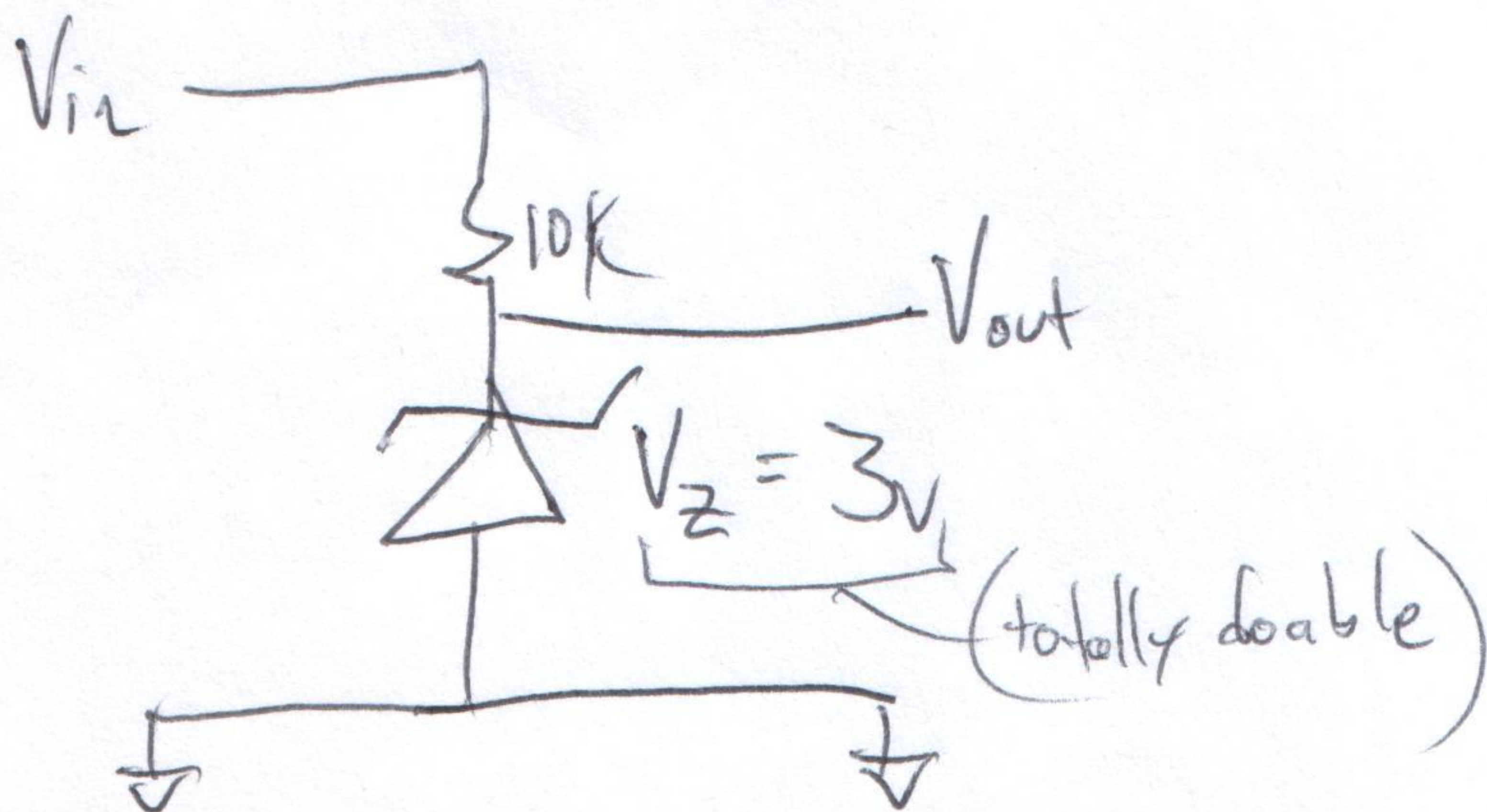If r_D is very small, and the attached load doesn't pull a huge amount of current, this will work, but being made of 4 diodes is kind of a mess, so:



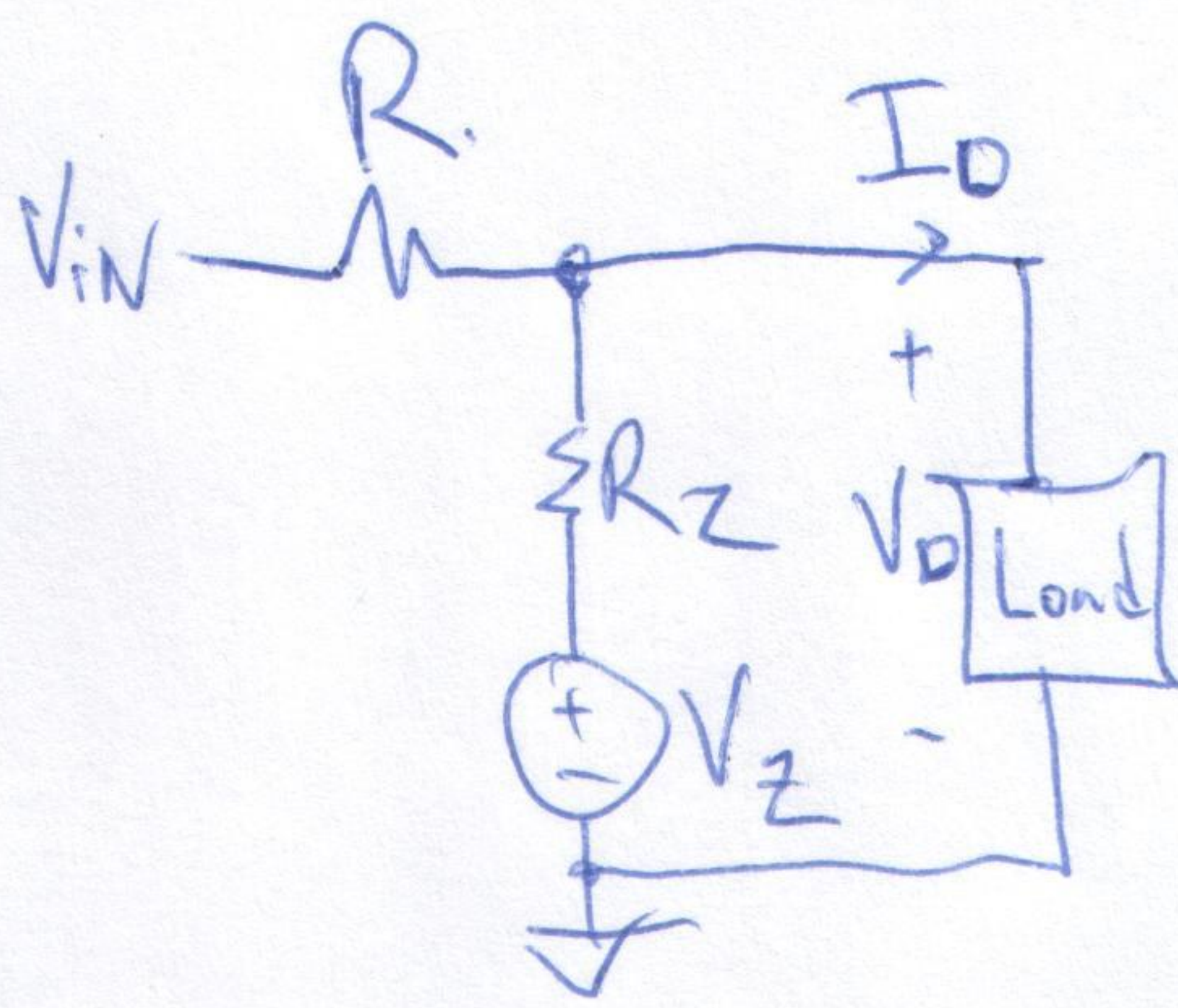

Ideal behavior: $V_O \equiv V_Z$

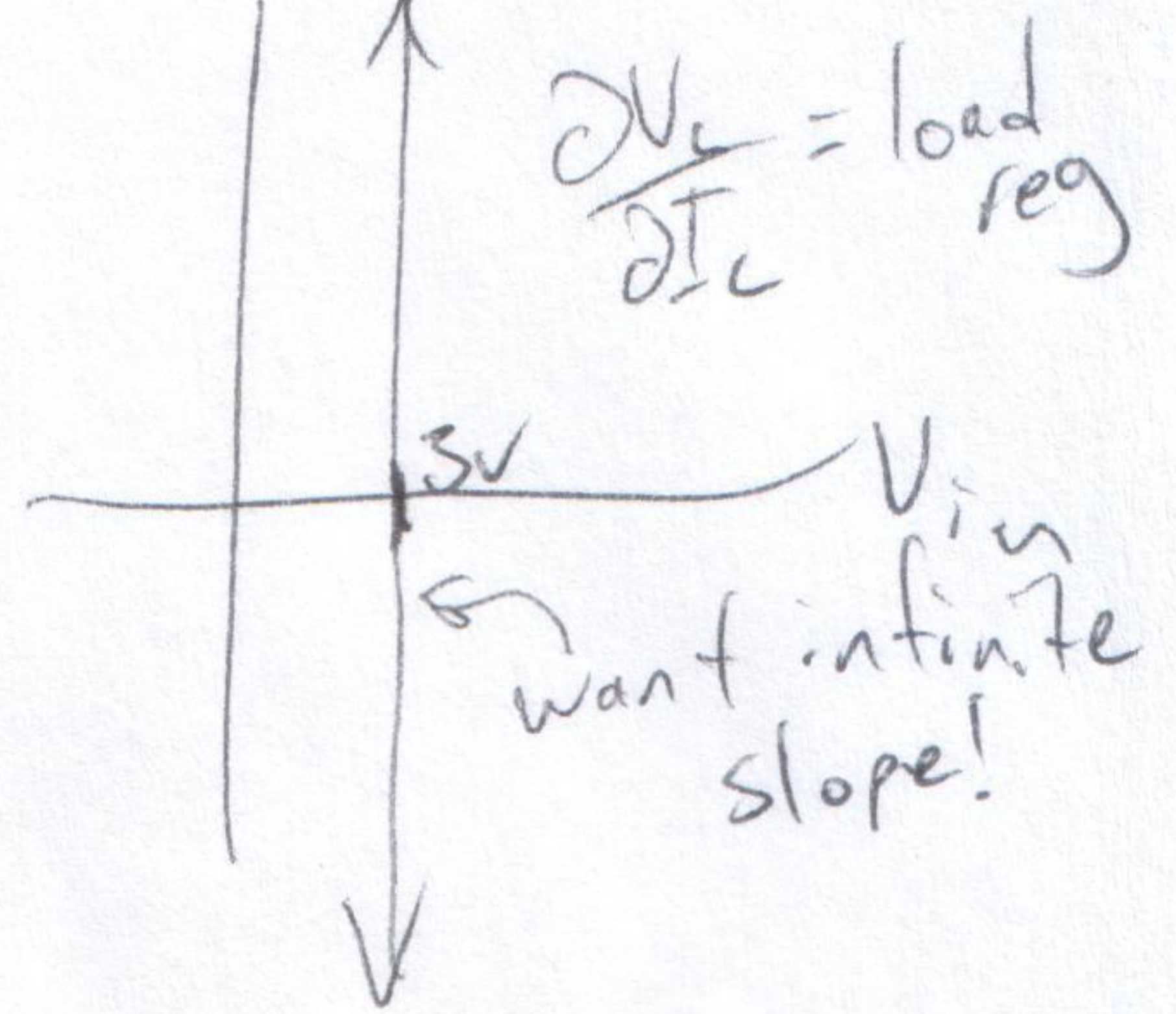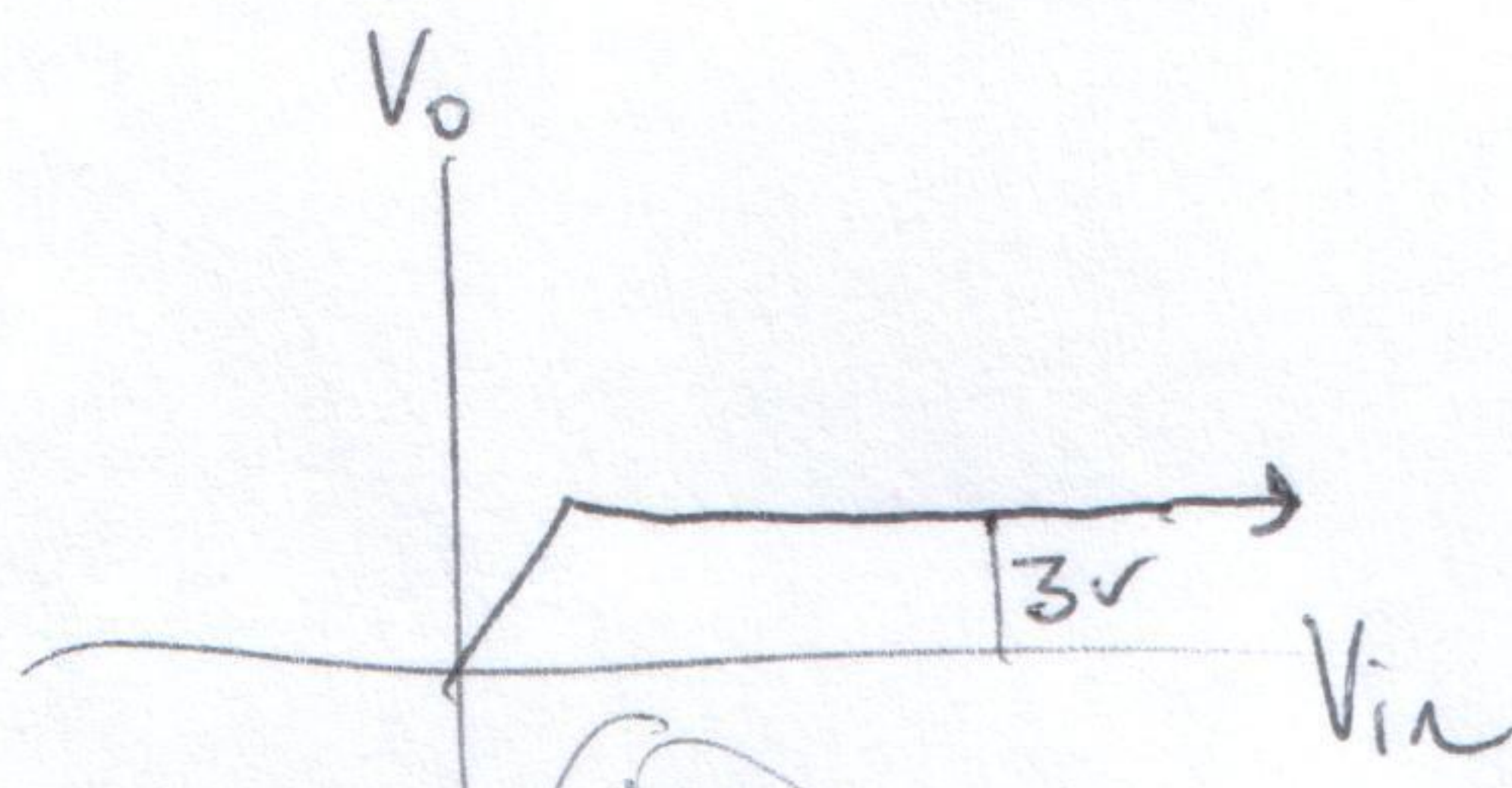

$\frac{\partial V_O}{\partial I_L} = \text{load reg}$

want infinite slope!

$\frac{dV_{in}}{dV_O} = \text{Line Regulation}$
 $(\frac{dV_O}{dV_{in}})^{-1}$, flat $\Rightarrow 0$,
 $\frac{dV_{in}}{dV_O} = \infty$

Line Regulation assumes $I_O = 0$

$$V_O = V_Z + R_Z \cdot I$$

$$I = \frac{V_{in} - V_Z}{R + R_Z}$$

$$V_O = V_Z + R_Z \frac{V_{in} - V_Z}{R + R_Z}$$

Load Regulation:

Circuit trick: try not to use variables you don't want in your final answer.

$$V_O = V_Z + \frac{R_Z}{R + R_Z} \cdot V_{in} - \frac{R_Z}{R + R_Z} V_Z$$


derivative!

~~V_O, I_O~~ ~~R_{load}~~

$$\frac{dV_O}{dV_{in}} = \frac{R_Z}{R + R_Z} \quad \text{reg} = \frac{dV_{in}}{dV_O} = \frac{R + R_Z}{R_Z}$$

$$V_O = V_S - R(I_O + I_{DIODE})$$

$$I_{DIODE} = \frac{V_O - V_Z}{R_Z}$$

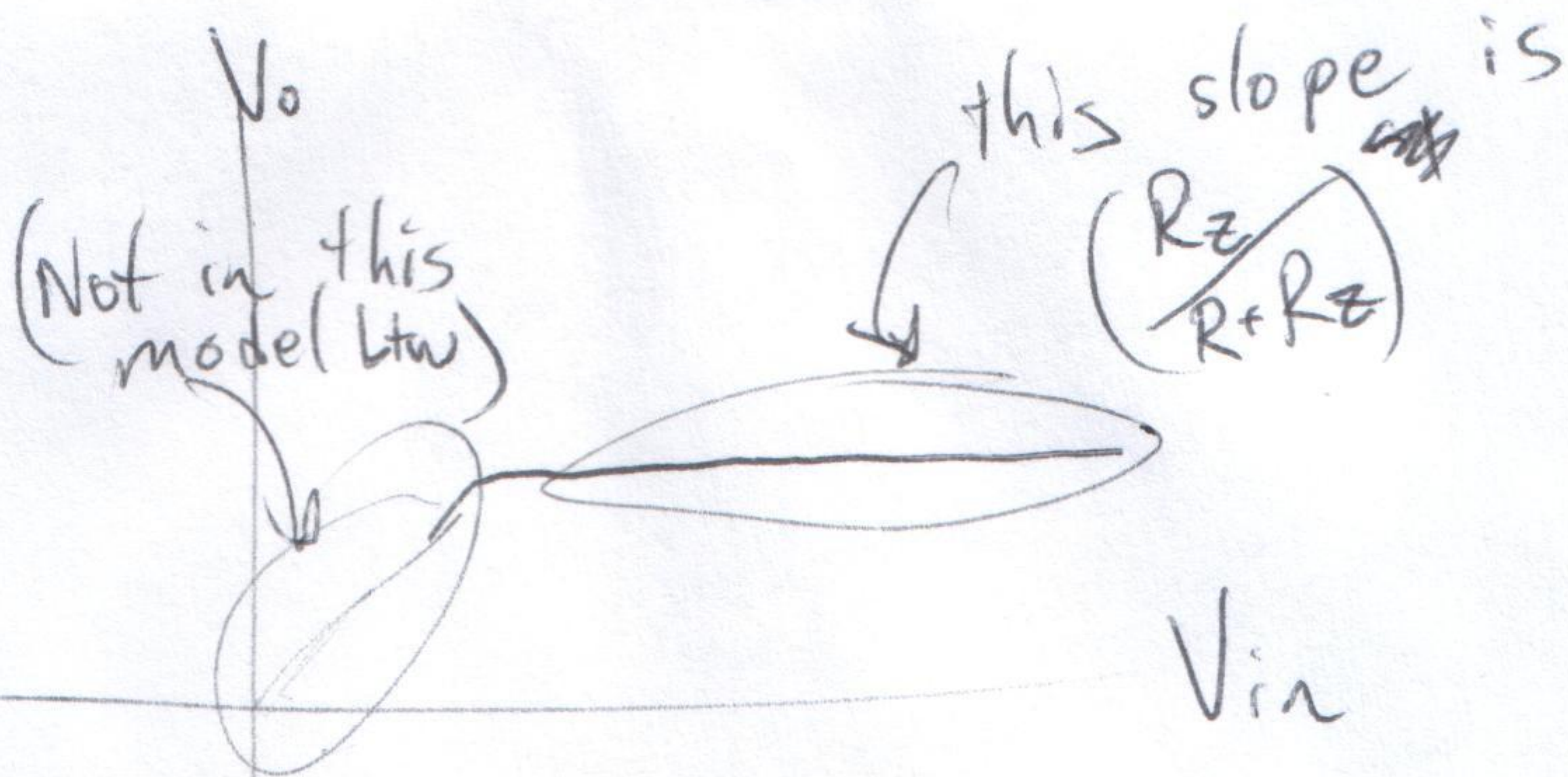

$$V_O = V_S - R I_O - R \frac{V_O - V_Z}{R_Z}$$

$$V_O = V_S - R I_O - \frac{R}{R_Z} V_O + \frac{R}{R_Z} V_Z$$

$$V_O \left(1 + \frac{R}{R_Z}\right) = V_S - R I_O + \frac{R}{R_Z} V_Z$$

$$V_O = V_S \frac{1}{1 + \frac{R}{R_Z}} - \frac{R}{1 + \frac{R}{R_Z}} I_O + \frac{R}{R_Z \left(1 + \frac{R}{R_Z}\right)} V_Z$$

Slope!

$$\frac{\partial V_O}{\partial I_O} = \frac{R R_Z}{R + R_Z} \rightarrow \sim 20\% \quad \rightarrow \text{Circuit diagram showing } 20\Omega \text{ resistor and } V_Z \text{ diode}$$

Regulation =

V_{in} can be moved between 20 and 50V, and if, say,

$$R_Z = 20 \Omega \text{ \& } R = 10K,$$

V_O will only move by 0.06V!
 (Regulation = 50%)

This regulator: looks like $\sim 10k\Omega$ loading the supply

if current does not deactivate the diode, looks like 20Ω R!

Takes a change of 50V to move V_{out} by 100mV!

Lab Prep aside:


- Lab will ask for lots of data on $I=f(V)$.

- Read questions ahead of time!

- Remember that curve tracing can have weird limits

Regulators Redox

Line Regulation: $\Delta I_o = 0$:

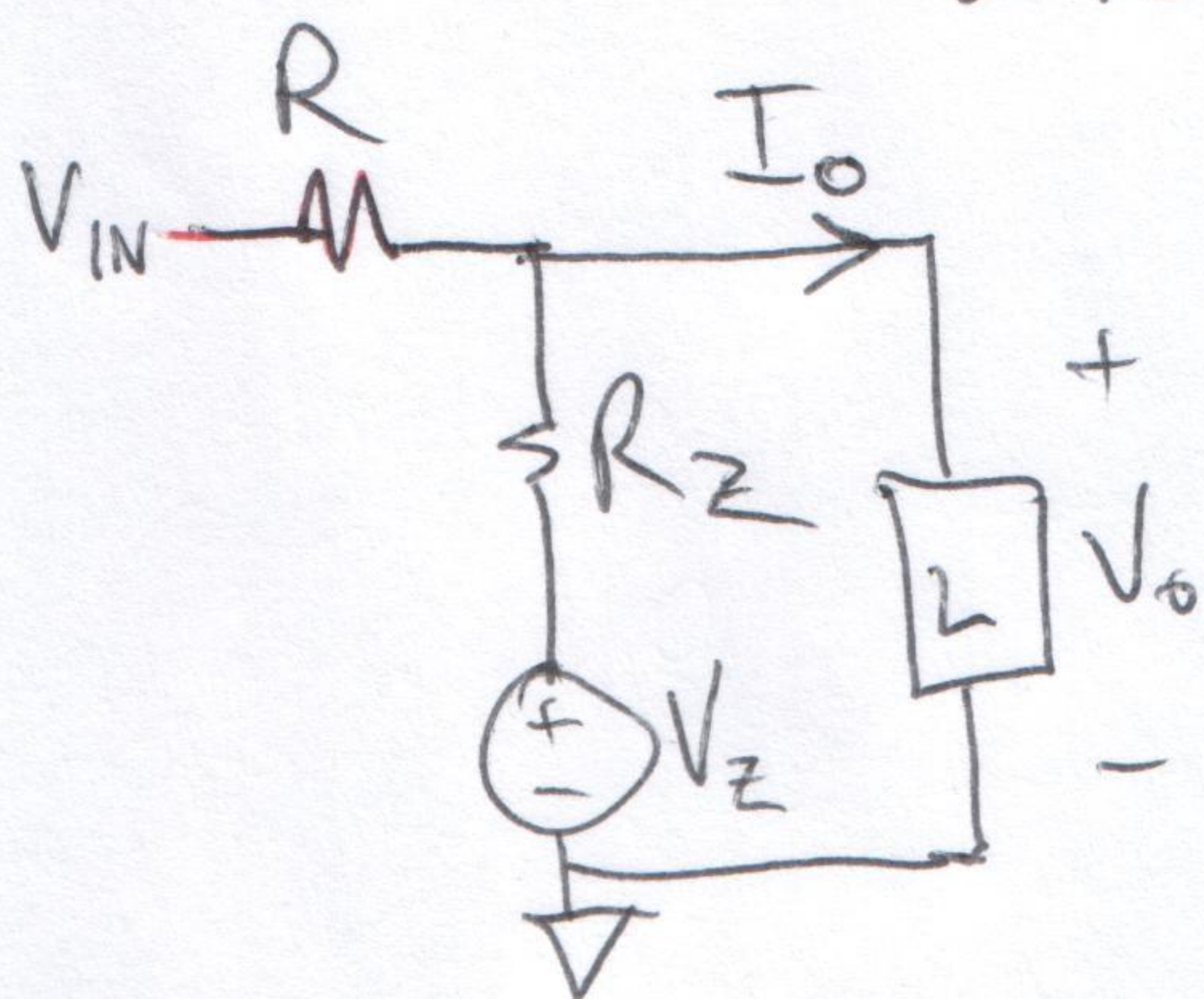


$$V_o = V_Z + R_Z \cdot I_x \quad \left(I_x = \frac{V_{in} - V_Z}{R + R_Z} \right)$$

$$V_o = V_Z + R_Z \frac{V_{in} - V_Z}{R + R_Z}$$

$$V_o = V_Z + V_{in} \cdot \frac{R_Z}{R + R_Z} + \cancel{V_Z} - V_Z \frac{R_Z}{R + R_Z}$$
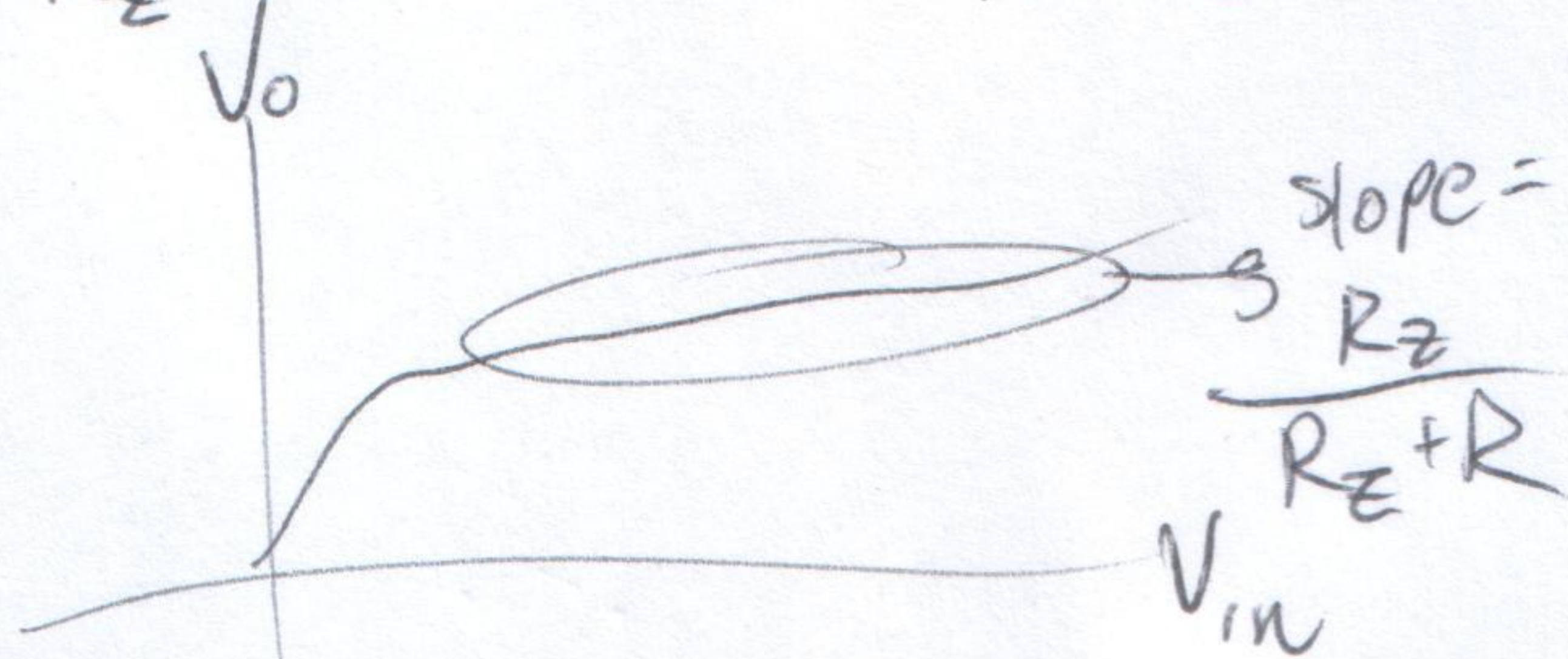
$$\frac{\partial V_{in}}{\partial V_o} = \frac{R + R_Z}{R_Z}$$



$R_Z = 20, R = 10K\Omega$
 Line Regulation = $\frac{10.02K}{.02K} = 501 \text{ V/V}$

$\Delta V_{in} = 10 \text{ V} \rightarrow \Delta V_o = \frac{10}{501} \approx 20 \text{ mV}$ ✓ Decent!

Load Regulation: $\frac{\partial V_o}{\partial I_o}$ KCL Route


~~$V_o = V_{in} - R \cdot (I_o + I_x) \quad I_x =$~~

$$\frac{V_o - V_{in}}{R} + \frac{V_o - V_Z}{R_Z} + I_o = 0$$

$$V_o \left(\frac{1}{R} + \frac{1}{R_Z} \right) - V_{in} \frac{1}{R} + V_Z \frac{1}{R_Z} + I_o = 0$$

$$\frac{\partial V_o}{\partial I_o} = - \frac{1}{\frac{1}{R} + \frac{1}{R_Z}}$$



it is negative.
ok.

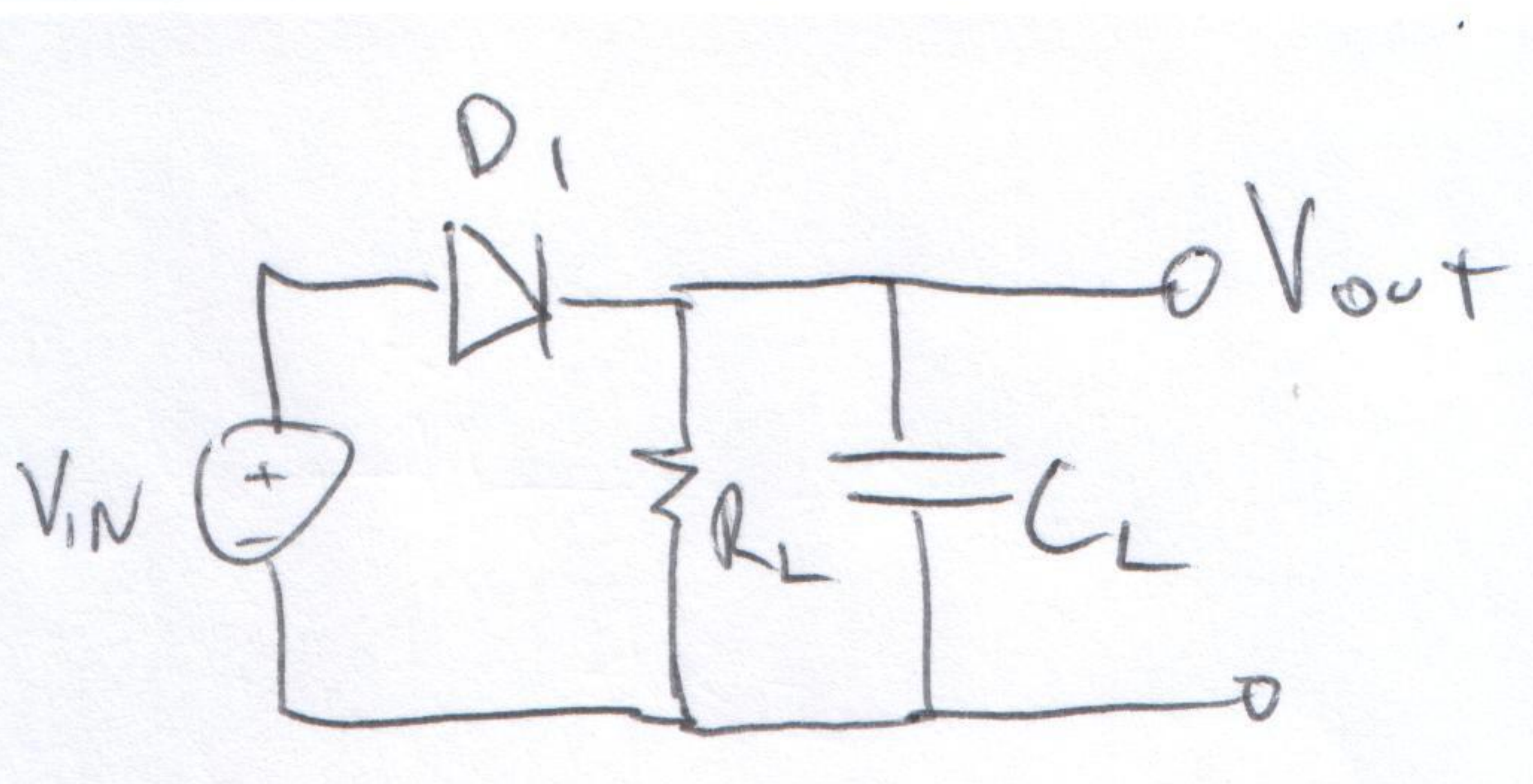


~~$\frac{1}{R_L C_L}$~~

$R_L C_L \gg \frac{1}{f_{sin}} \rightarrow \text{constant } V_{out} \text{ DC}$

Construction Detail:

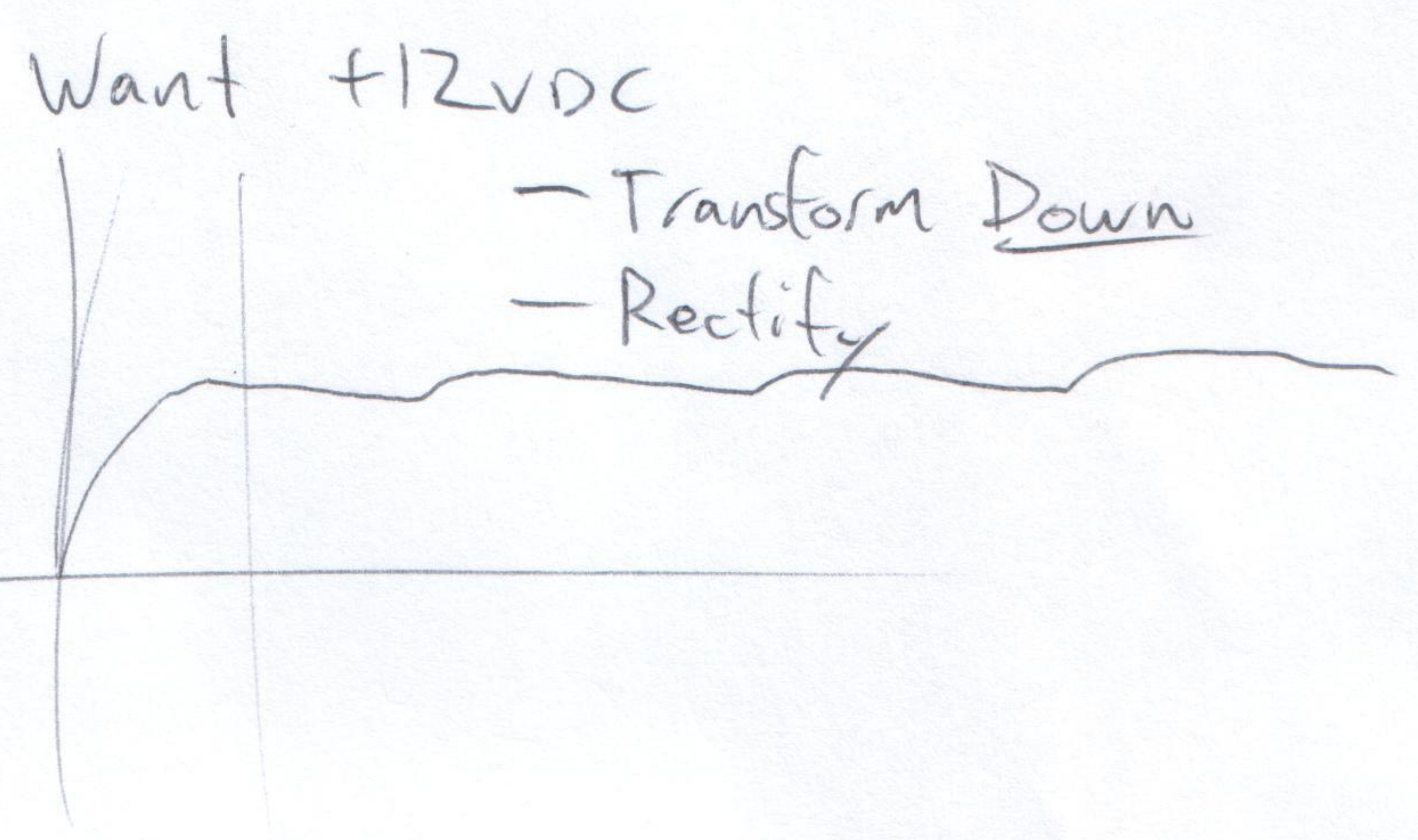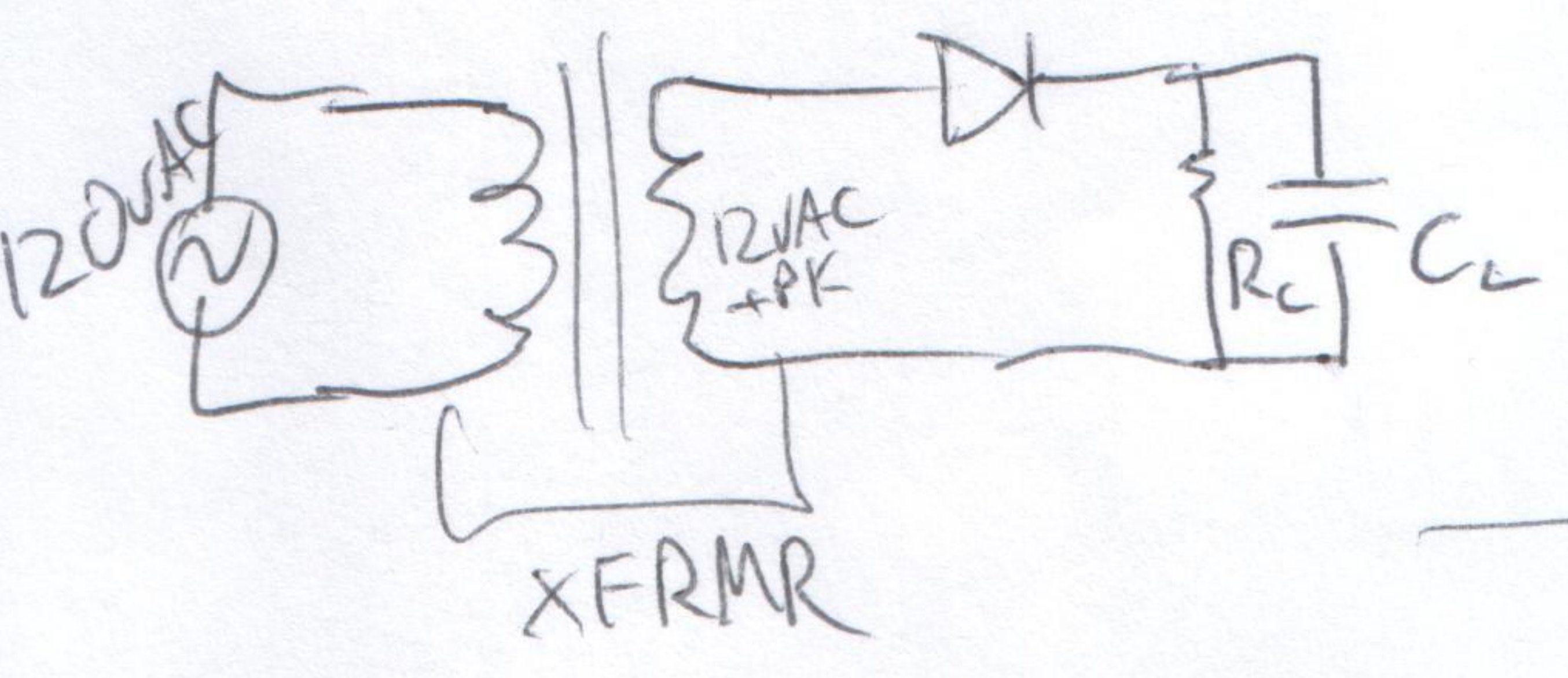

Ripple Voltage:

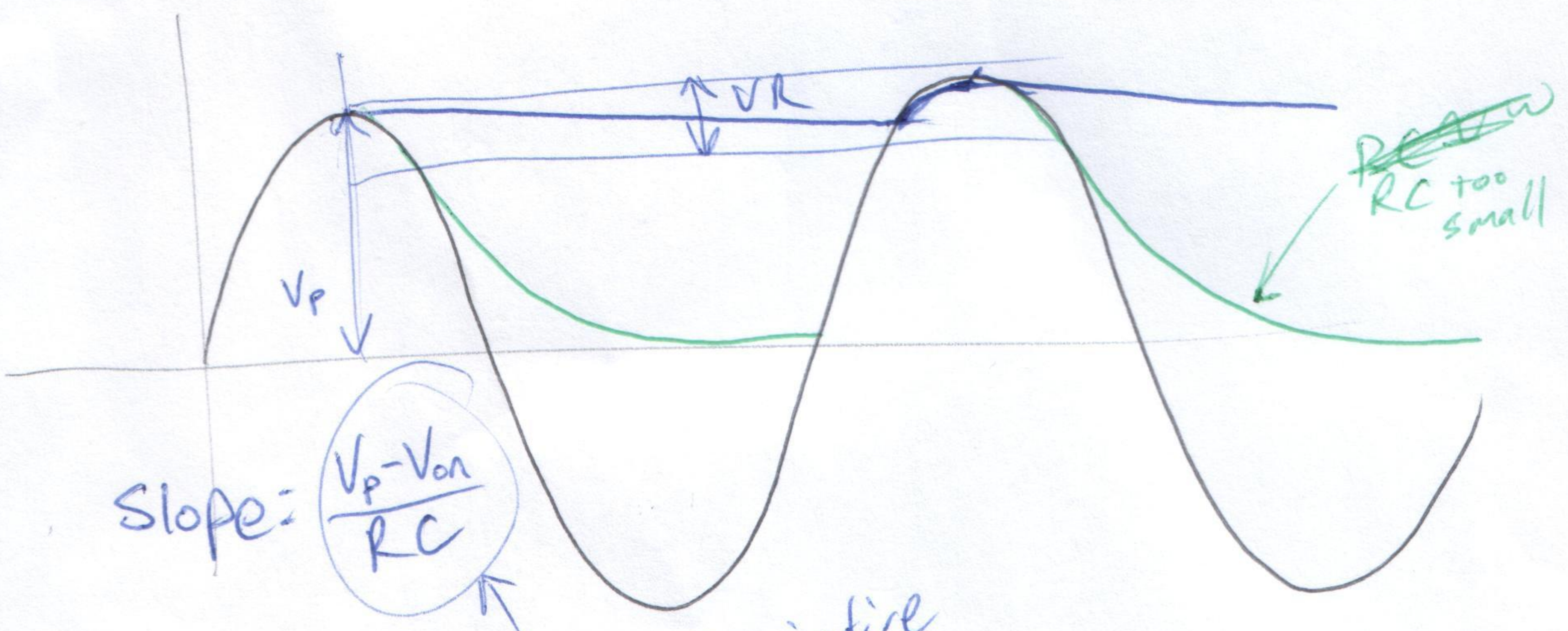


Slope = $\frac{V_p - V_{on}}{RC}$


$V_R = \frac{(V_p - V_{on})}{RC} \cdot T$

RC time constant derivative

period

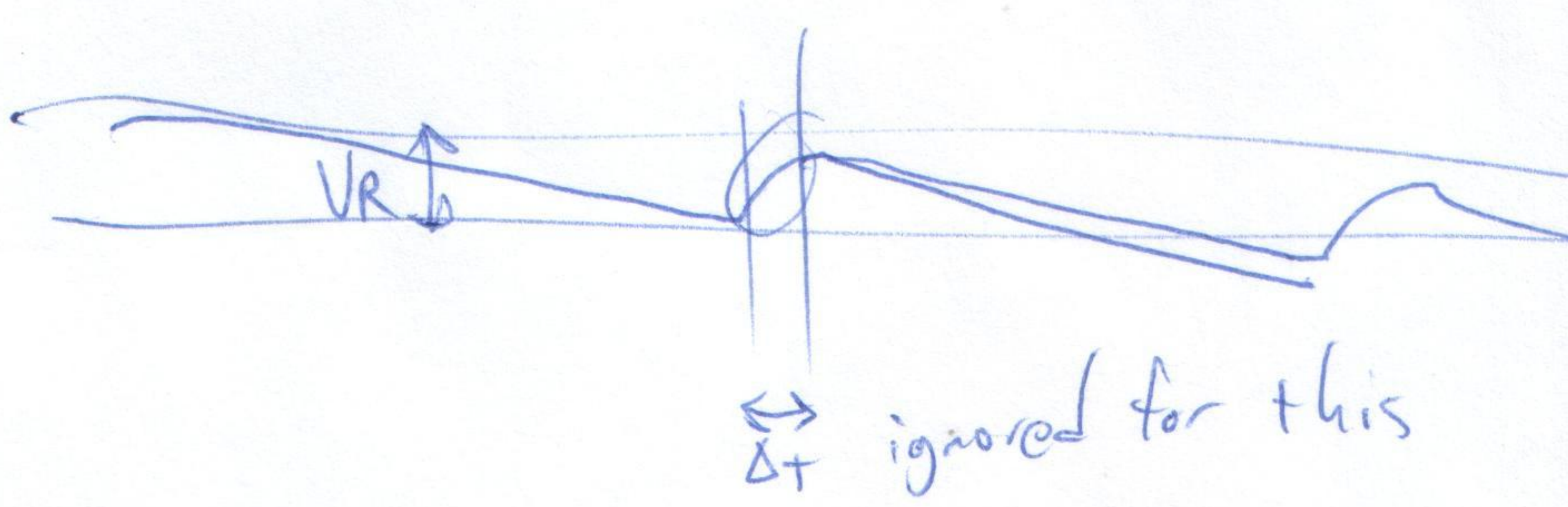


ΔT :

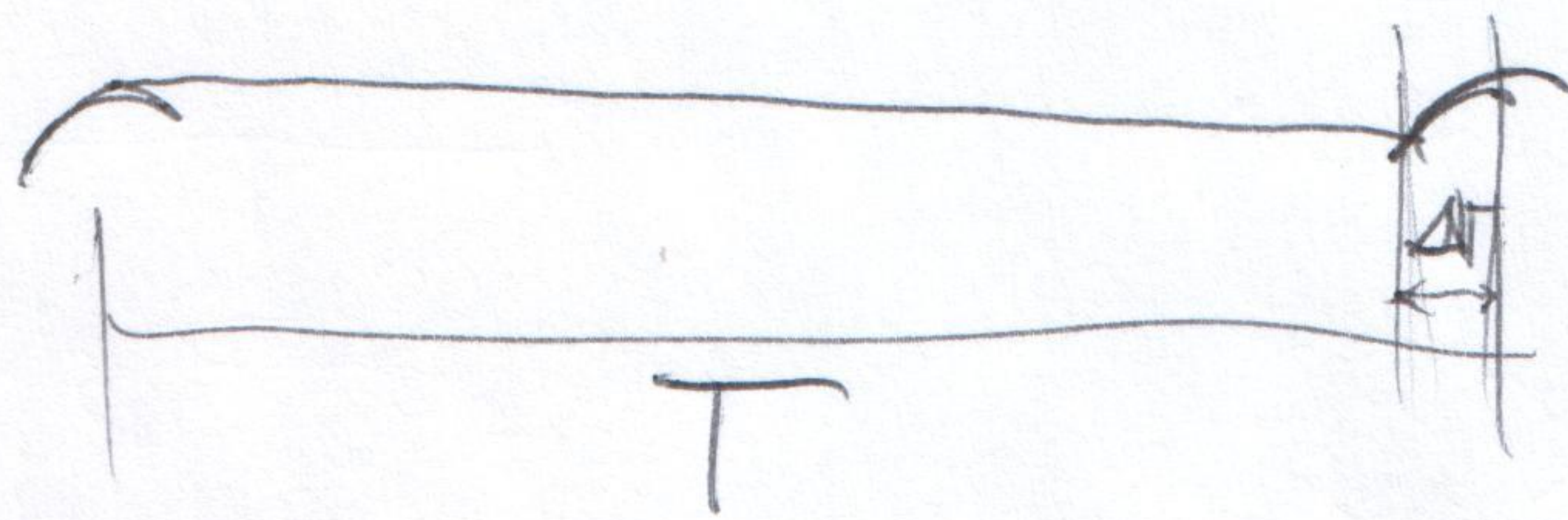

$$\theta_c \approx \sqrt{\frac{2V_r}{V_p}}$$

$$\Delta T \approx \frac{\theta_c}{\omega}$$

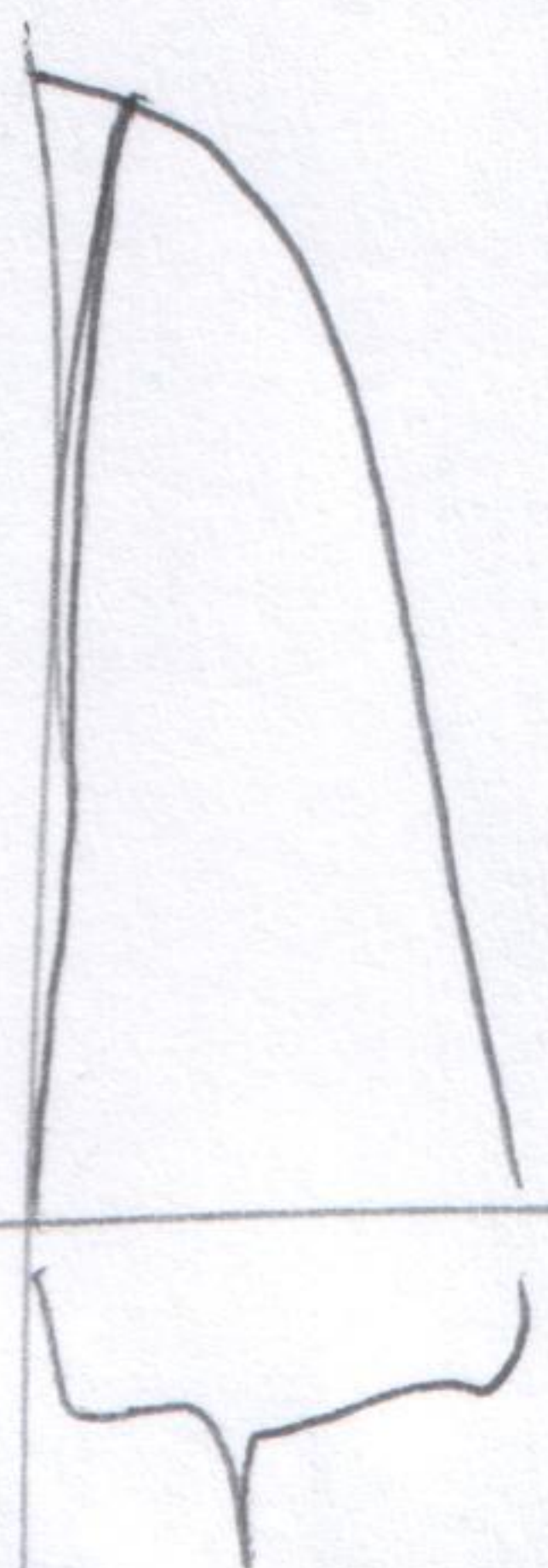Major Points: Current is only flowing during ΔT !



Capacitor needs to change voltage nearly instantly



Computing the peak of the surge current is ugly, but we can do good work with charge:

$$Q_{SURGE} = C_L \cdot V_{OUT}$$

$$I_{AVERAGE (SURGE)} = \frac{Q_{SURGE}}{\frac{T}{4}}$$

← how long it takes to charge

$$Q_{repeating} \approx \underbrace{I_{OUT} \cdot T}_{\text{total drain over one period}}$$

$$I_{REP} = \frac{Q_{REP}}{\Delta T}$$

$$I_{AVE} = \frac{4Q}{T}$$


$$I = C \frac{d}{dt} V_p \sin \omega t$$

$$I = \omega C V_p \cos \omega t$$

$$PK = \omega C V_p$$

These equations are less important than the idea: a big load of current at startup followed by slow drain with little bursts of refill current.

Peak Inverse Voltage

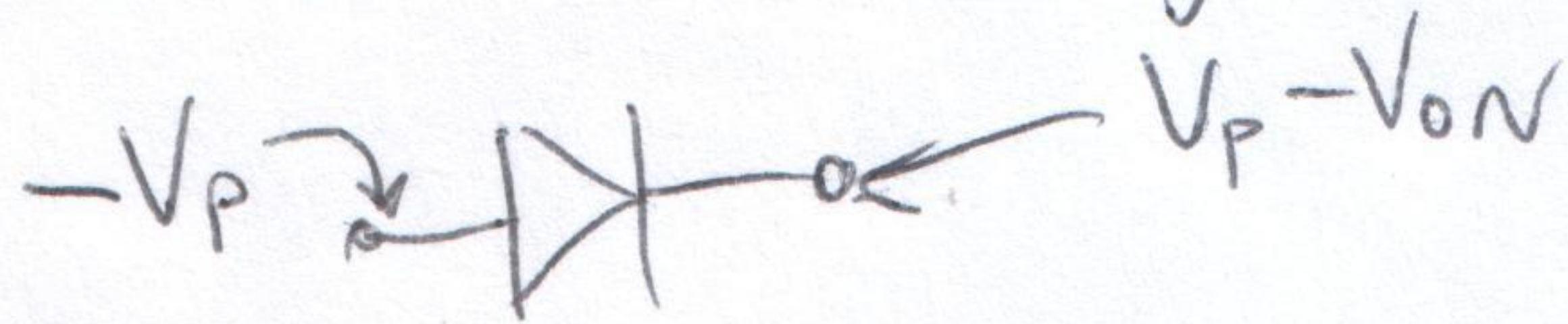

$$\underline{2V_p - V_{on}}$$

← make sure your diode is tougher than that!

In real designs:

Assuming the H.W.R. makes sense, you have some practical concerns:

- How much capacitance do you need? (RC)
- How much diode current must you support? (I SURGE)
- How much reverse bias will you face?
- How much power must the diode dissipate? (I · V)

Homework: Design a 5v power supply.

Specify:


- XFORMER in ratio from 120VAC to ??VAC
- A Rectifier (~~full wave or ha~~ ^{Half wave}) with C
- A zener diode _{regulator} to drop the voltage to 5v.

Report:

- Parts list
- Schematic
- V_{RIPPLE} at output.
- Max diode current, reverse bias

Due 12/7.
(Study problems to follow)

Analyzing ΔT

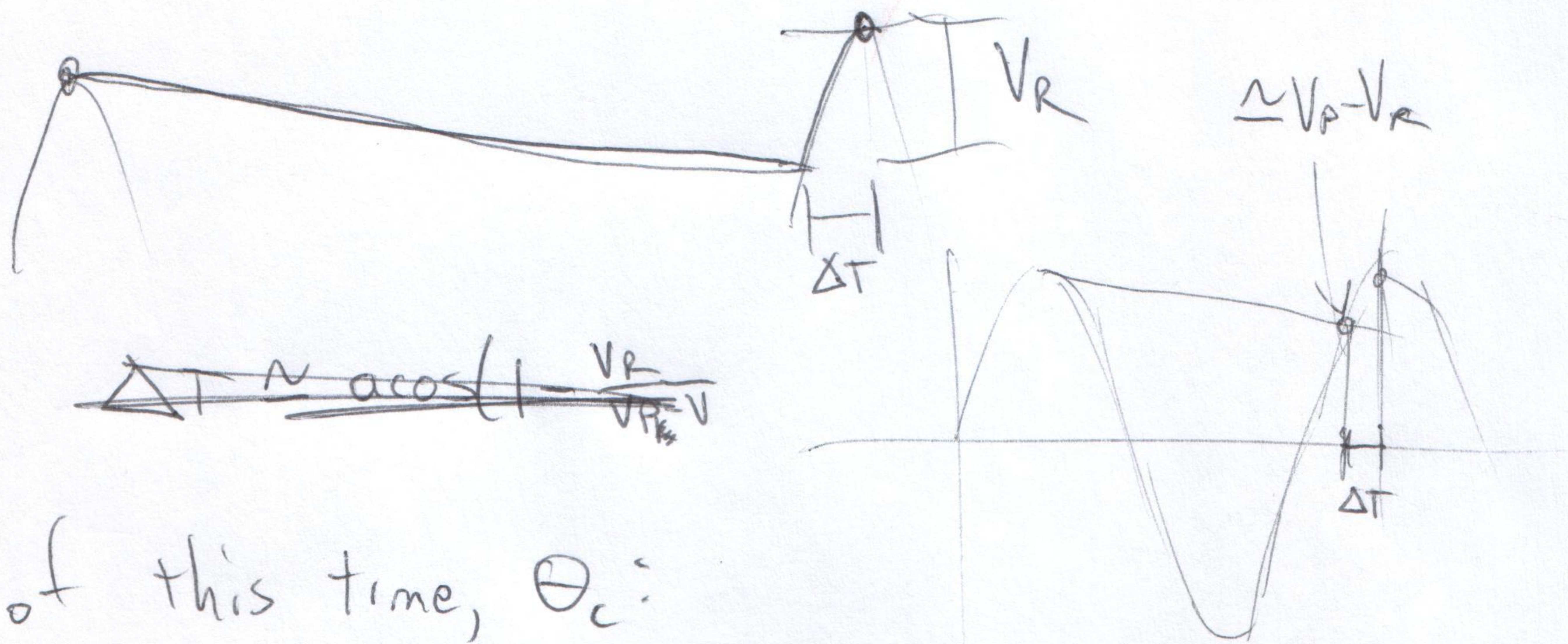

$$\Delta T \approx \frac{V_R}{V_P} \cos^{-1} \left(1 - \frac{V_R}{V_P} \right)$$

Angle of this time, Θ_c :


$$\cos \Theta_c = 1 - \frac{V_R}{V_P} \Rightarrow \cos \Theta_c \approx 1 - \frac{\Theta_c^2}{2}$$

$$= \frac{V_P - V_R}{V_P}$$

$$1 - \frac{\Theta_c^2}{2} \approx 1 - \frac{V_R}{V_P} \Rightarrow \Theta_c \approx \sqrt{\frac{2V_R}{V_P}}$$

$$\Delta T = \frac{\Theta_c}{\omega} = \frac{1}{\omega} \sqrt{\frac{2V_R}{V_P}}$$

Current:

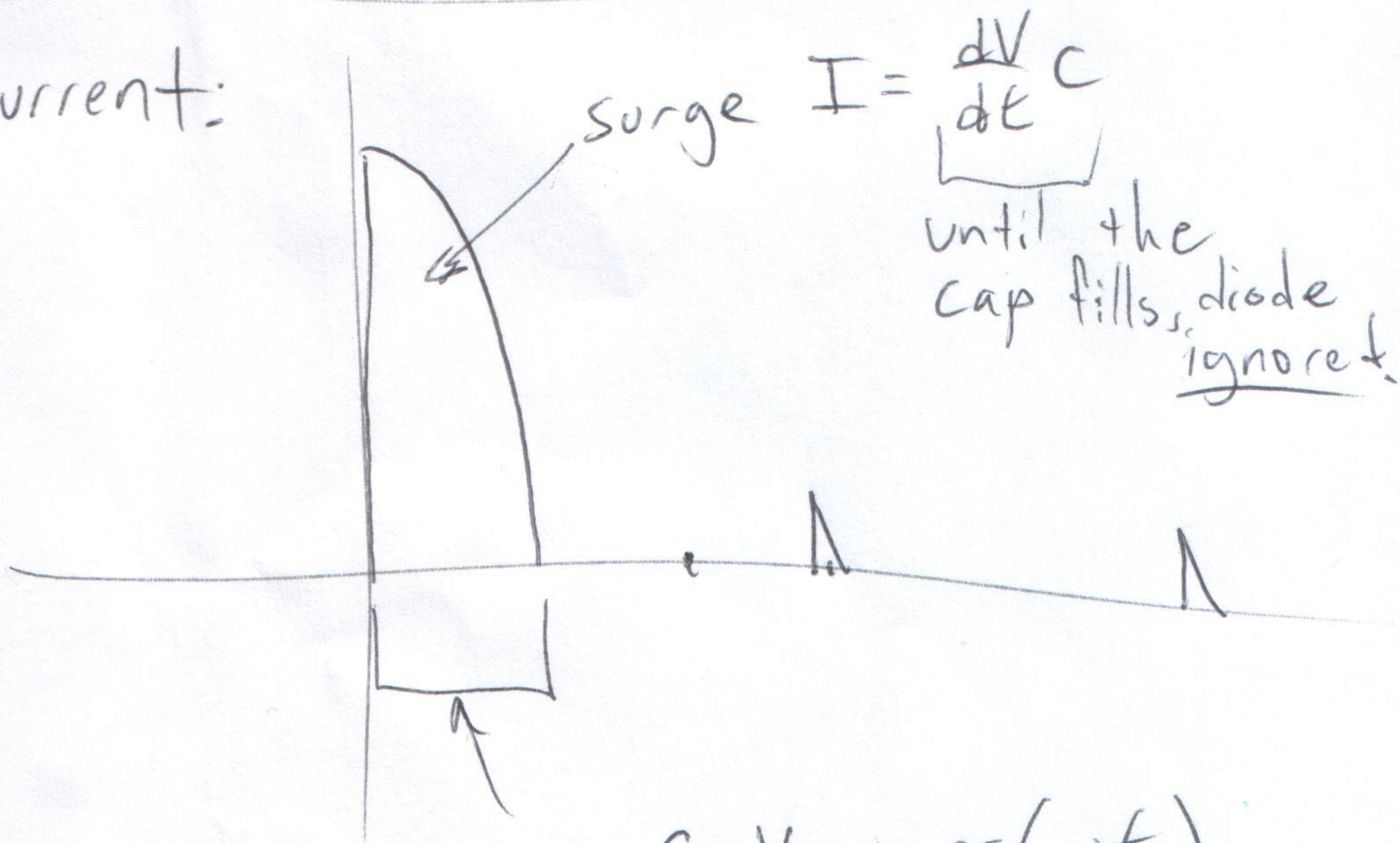

$$I = C \cdot V_P \omega \cos(\omega t)$$

$$\text{Initial surge} = \omega C V_P$$


Note: bigger for higher f , C , and V_P .

Spikes:




$$Q = I_{DC} \cdot T = I_{SPIKE} \frac{\Delta T}{2}$$

$$I_{SPIKE} = I_{DC} \frac{2T}{\Delta T}$$

$$= I_{DC}$$

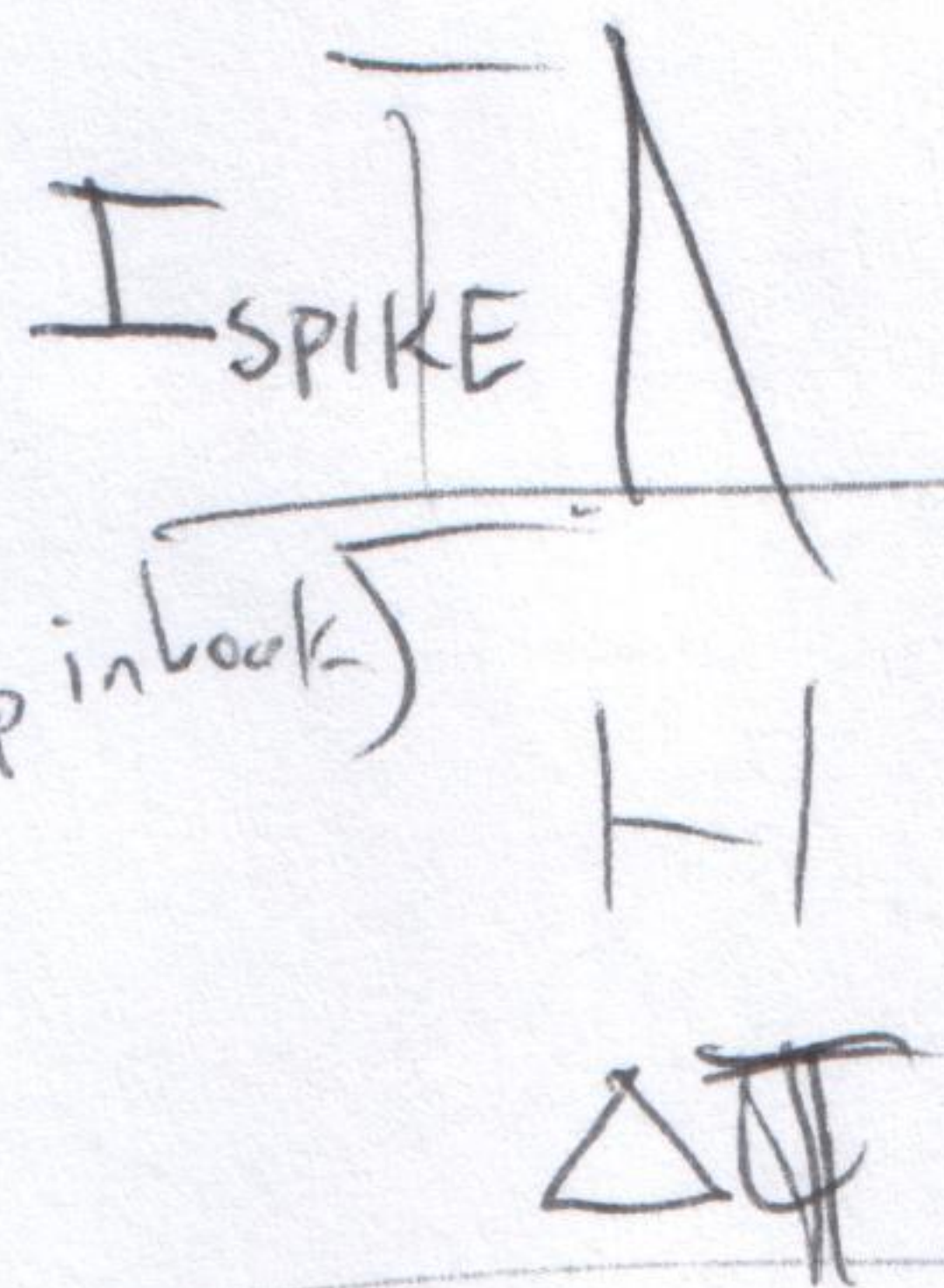

Going Full WAVE

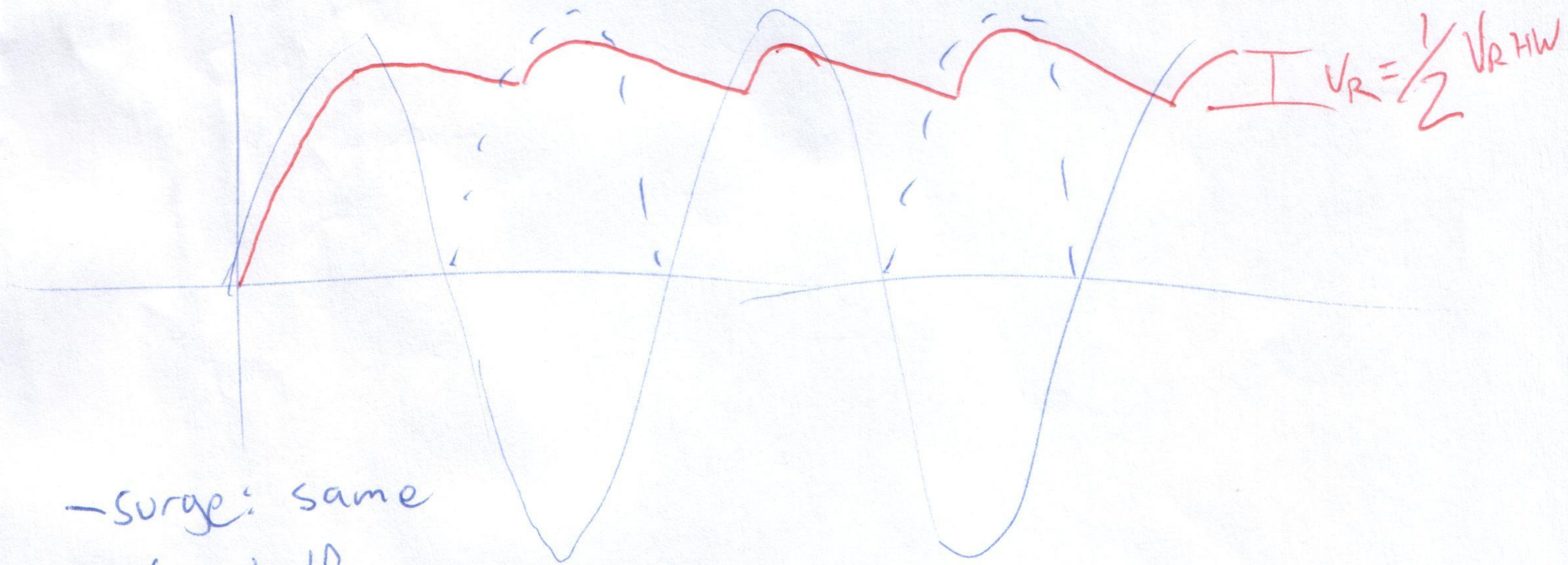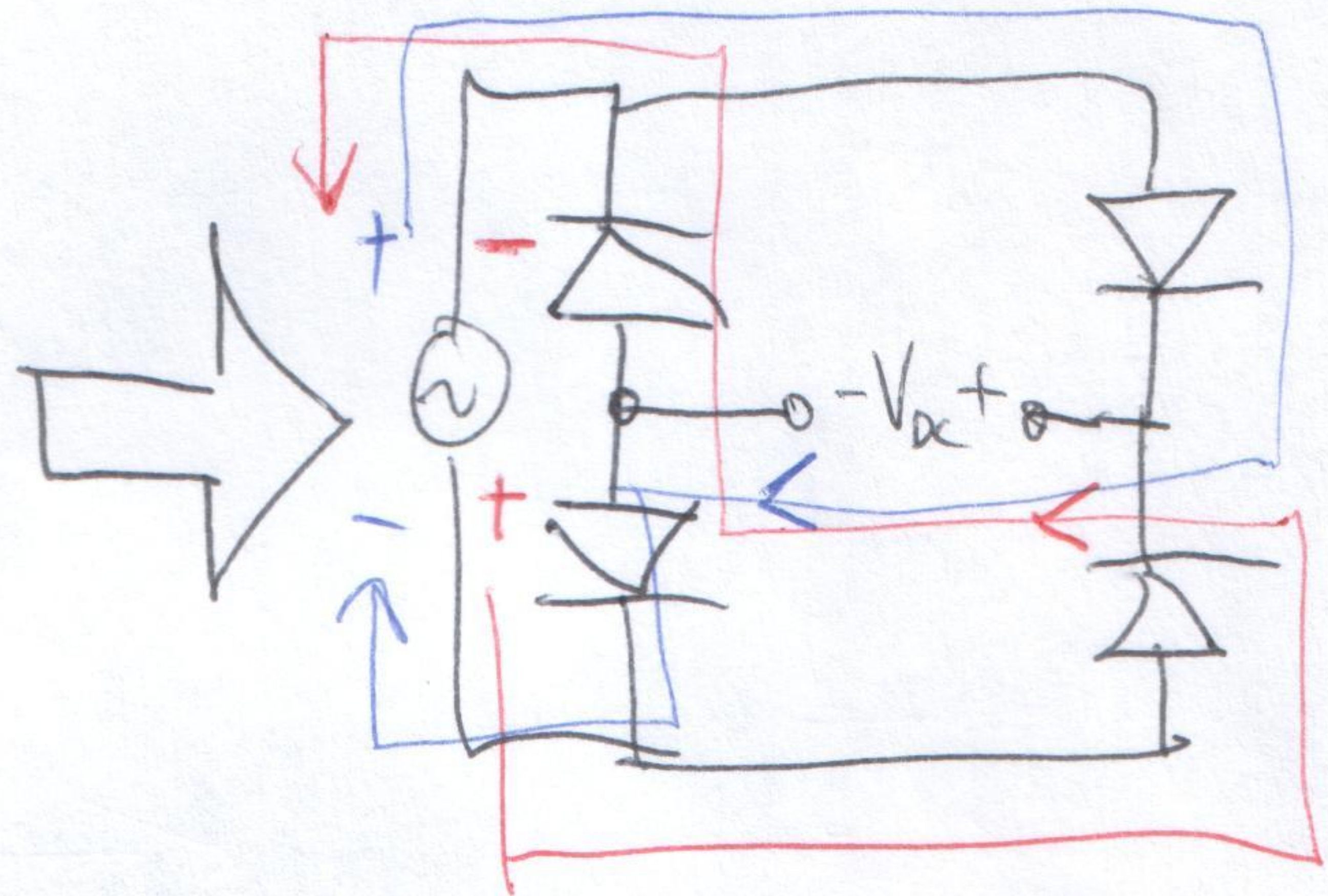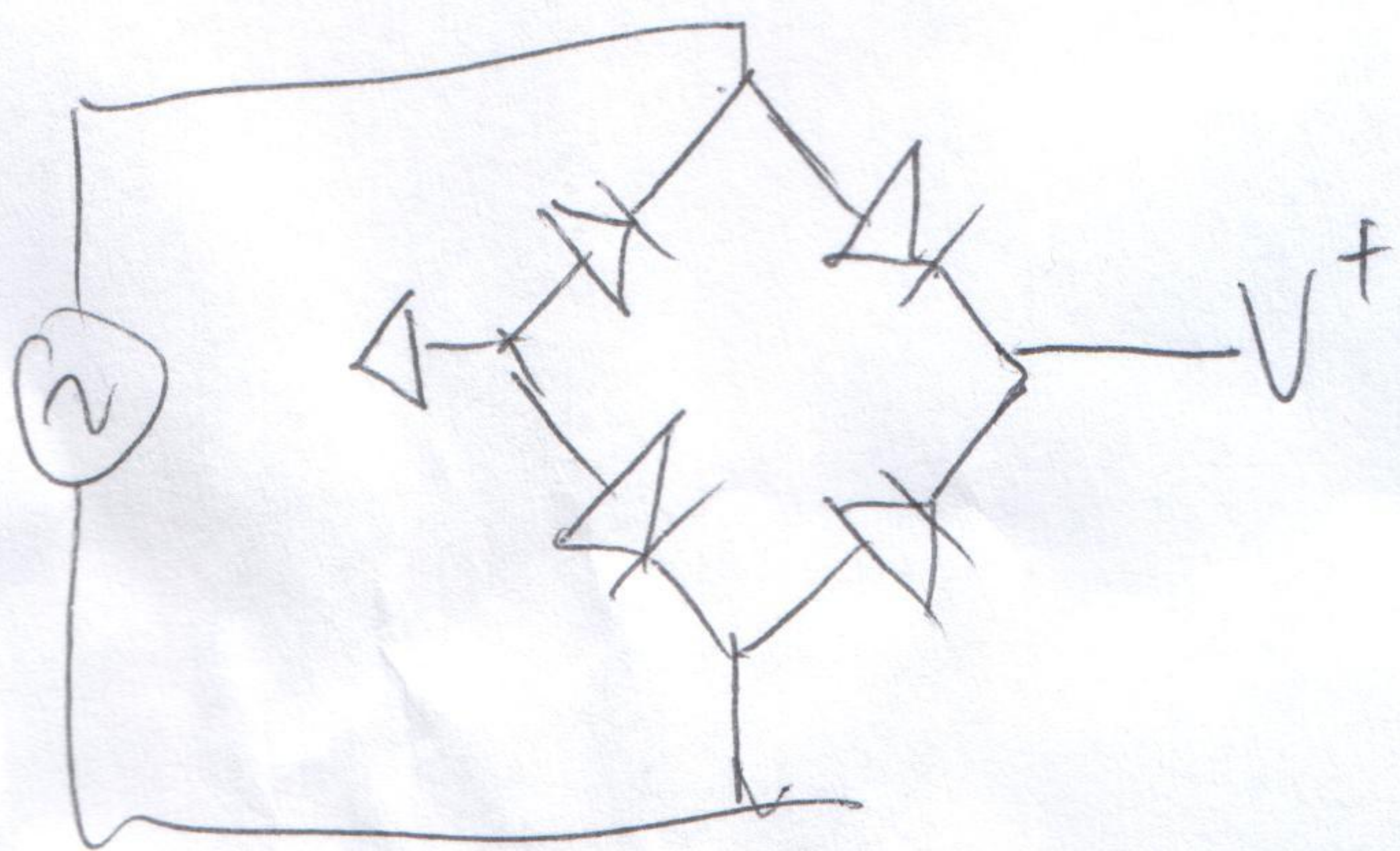

- surge: same

- V_R = half

- Peak I_{spike} = ~~half~~