

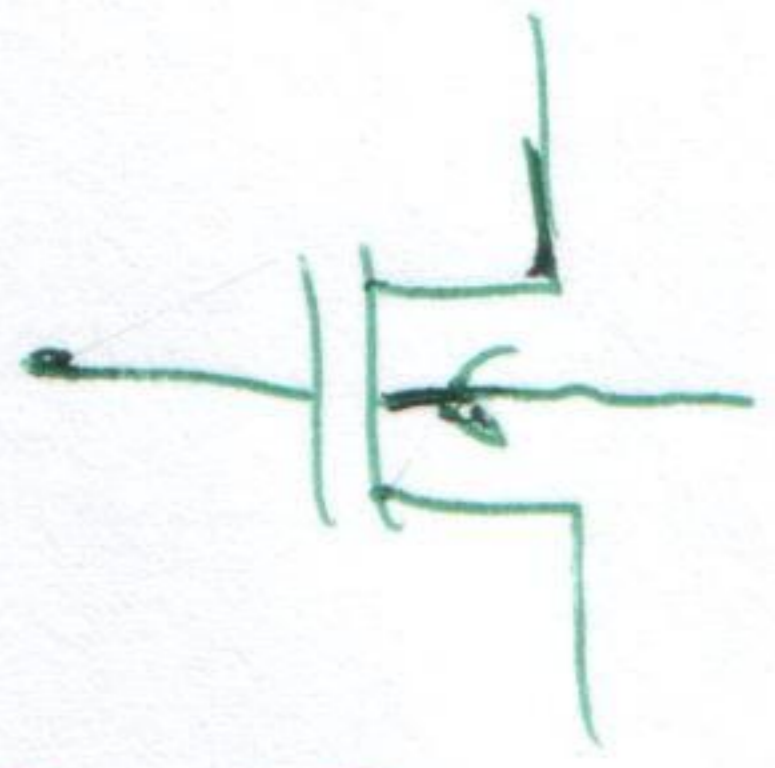


NMOS

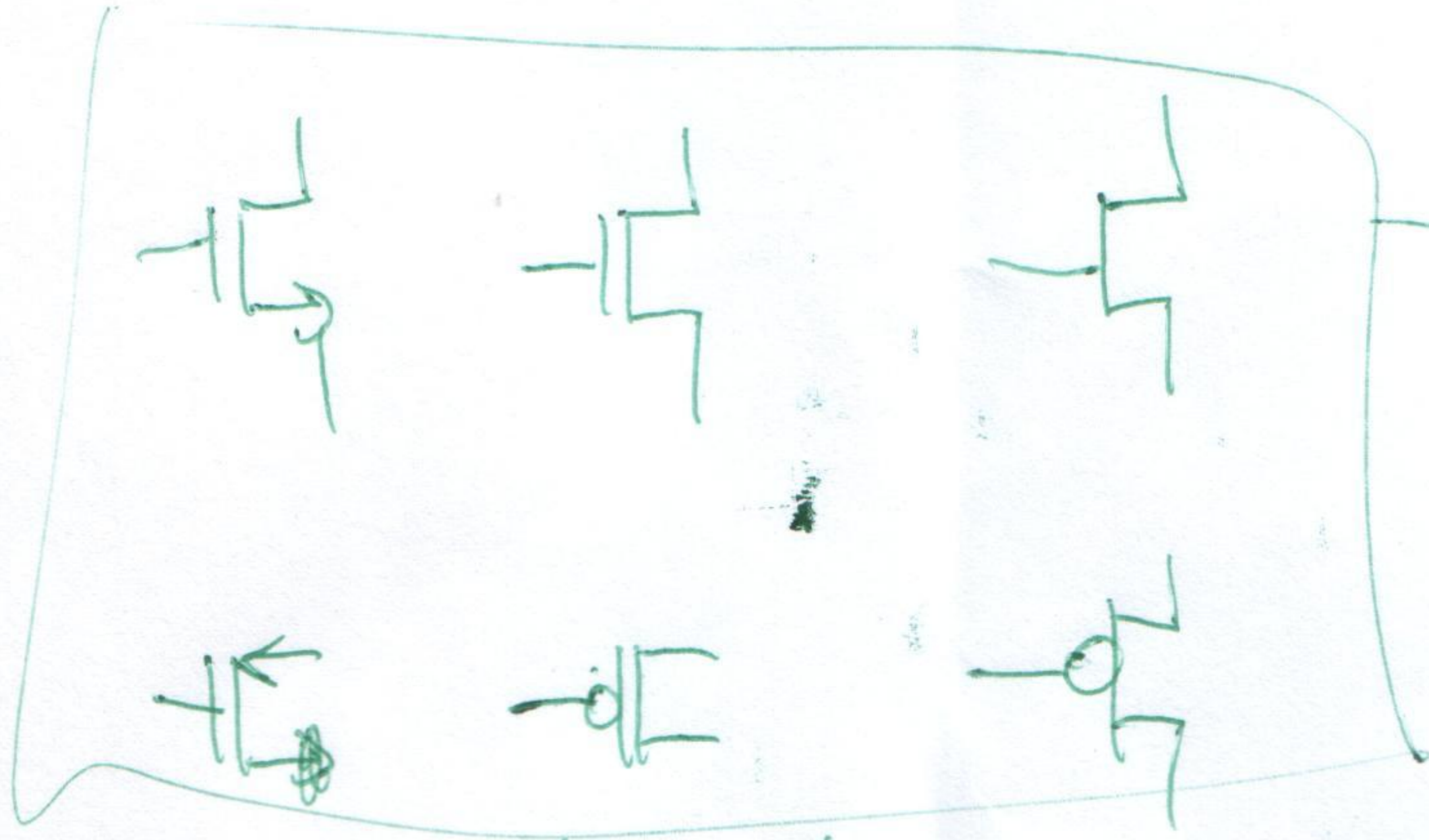



PMOS

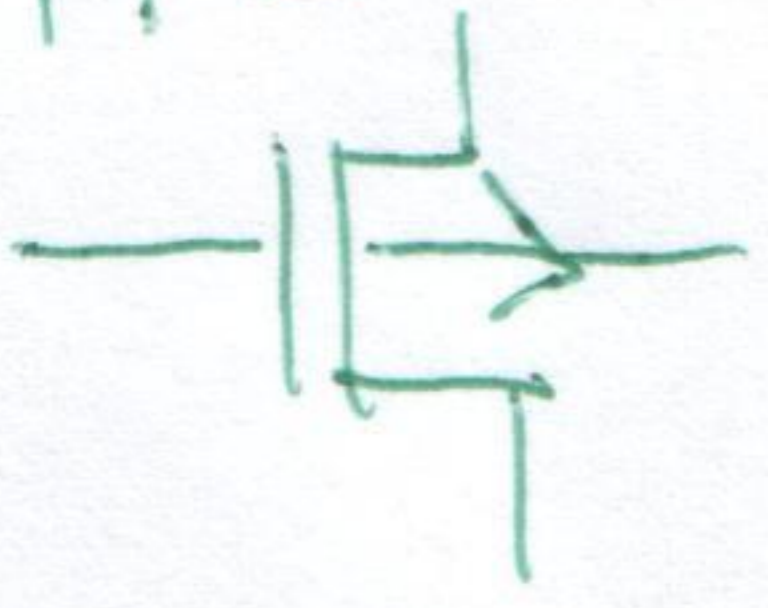

assume "something" done about bulk effect


Depletion Mode: Consult the apparently brilliant wizards that have you doing depletion mode devices.
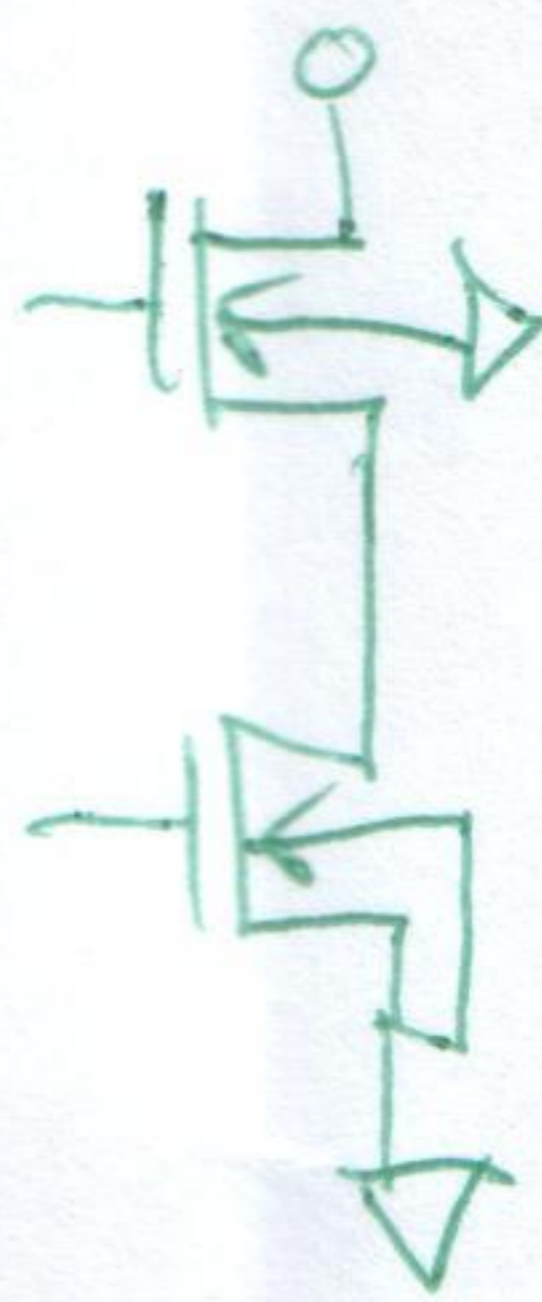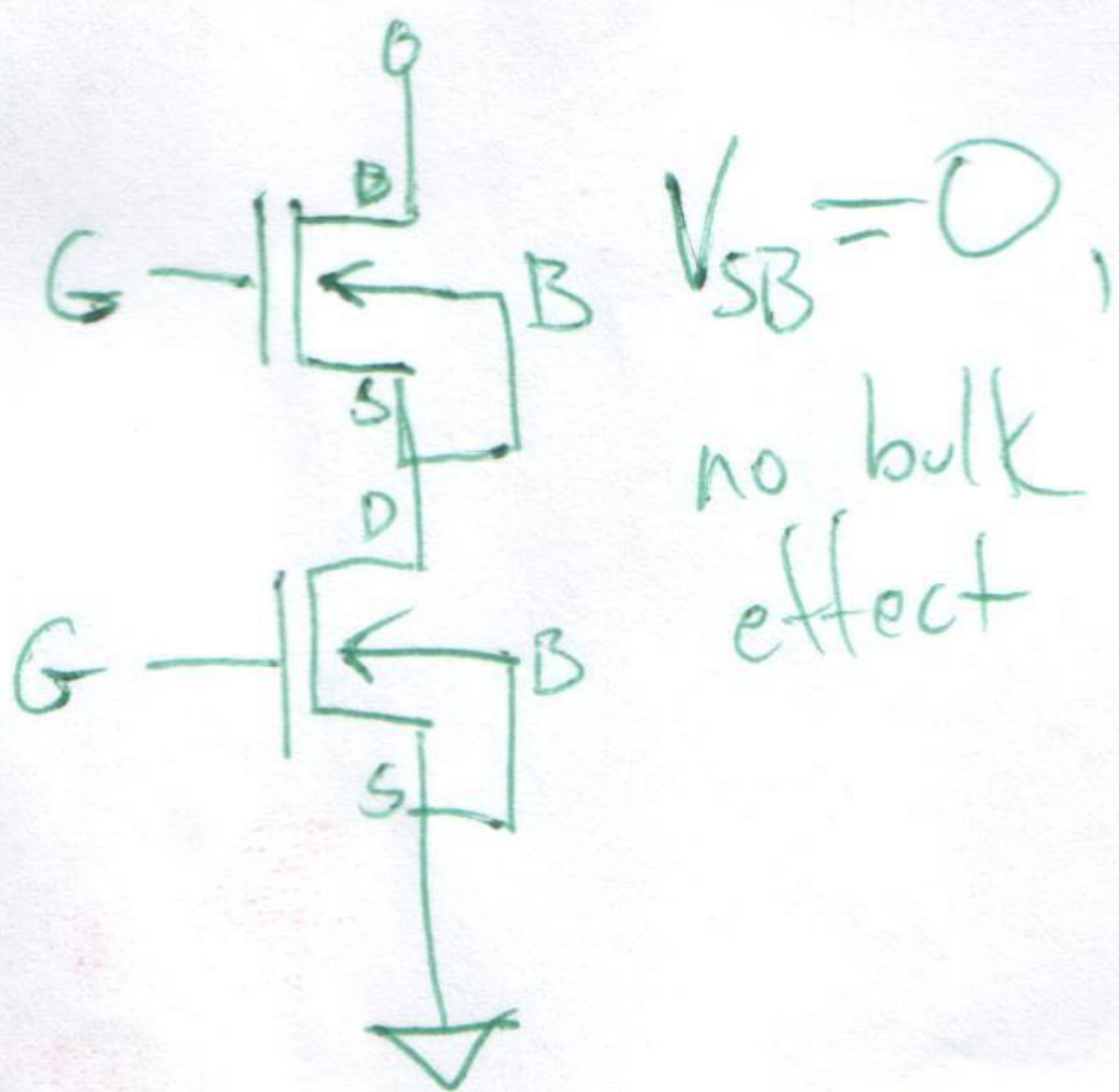
$$V_{TN} = \underbrace{V_{T0}}_{V_{TN} @ 0V V_{SB}} + \underbrace{\gamma}_{\text{Some constant}} \left(\underbrace{\sqrt{V_{SB} + 2\phi_F}}_{\text{Some other constant}} - \underbrace{\sqrt{2\phi_F}}_{\text{Some other constant}} \right) \leftarrow \text{?}$$



Cutoff Region	Current Equation	Condition
Cutoff	$i_D = 0$	$V_{GS} < V_{TN}$
Triode / Linear	$i_D = K_n' \frac{W}{L} \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$	$V_{GS} > V_{TN}$ $V_{GS} - V_{DS} \geq V_{TN}$
Saturation	$i_D = K_n' \frac{W}{L} \cdot \frac{1}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$ <small>↑ slope</small>	$V_{GS} > V_{TN}$ $V_{GS} - V_{DS} < V_{TN}$


what. → V_{DS}

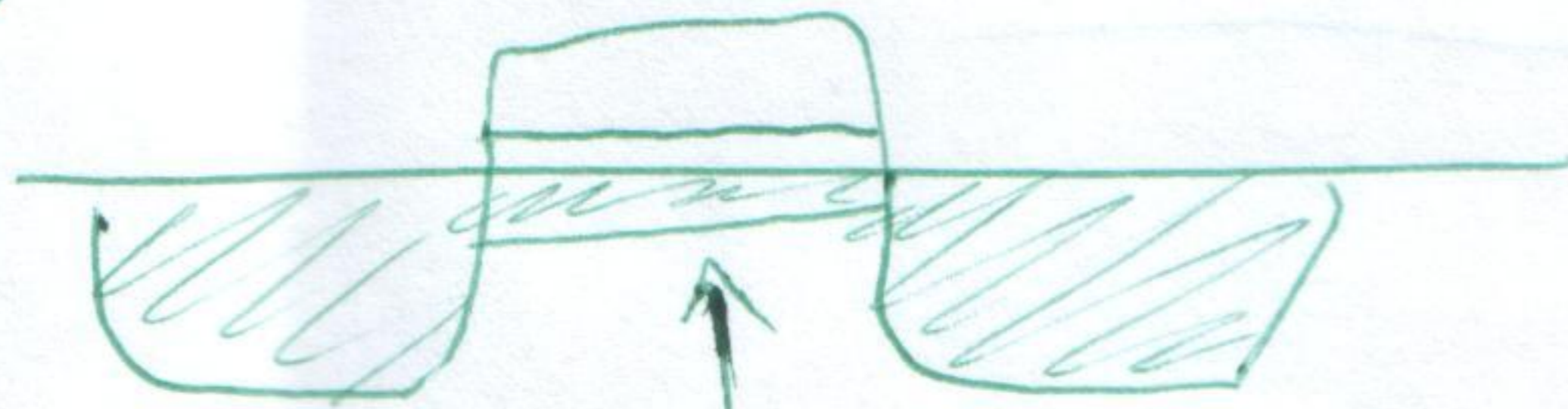



shape of region modeled as linear.

Idea: resistance increases as V_{DS} increases


Saturation

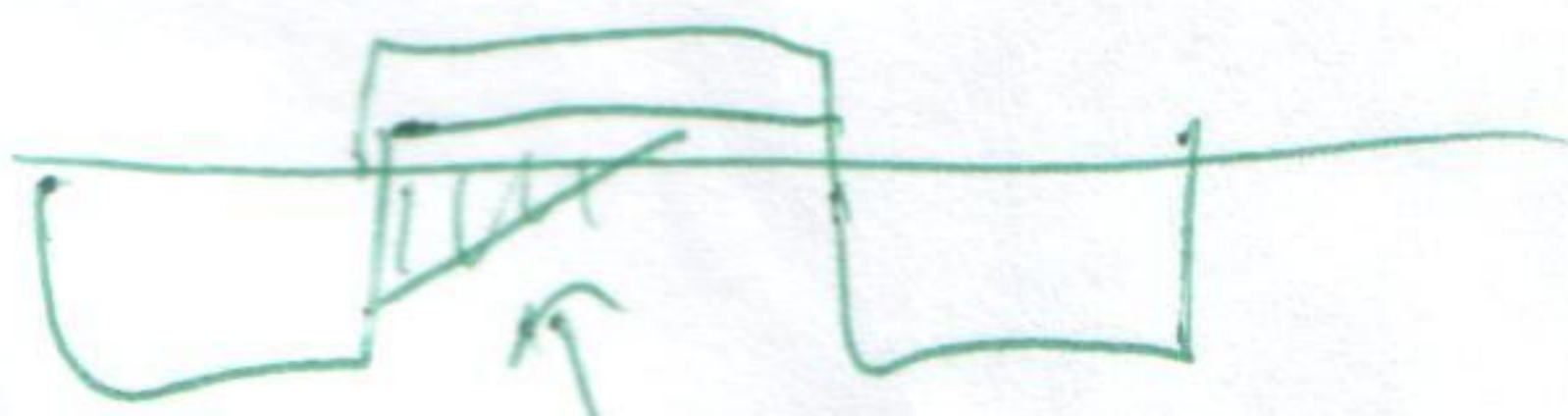

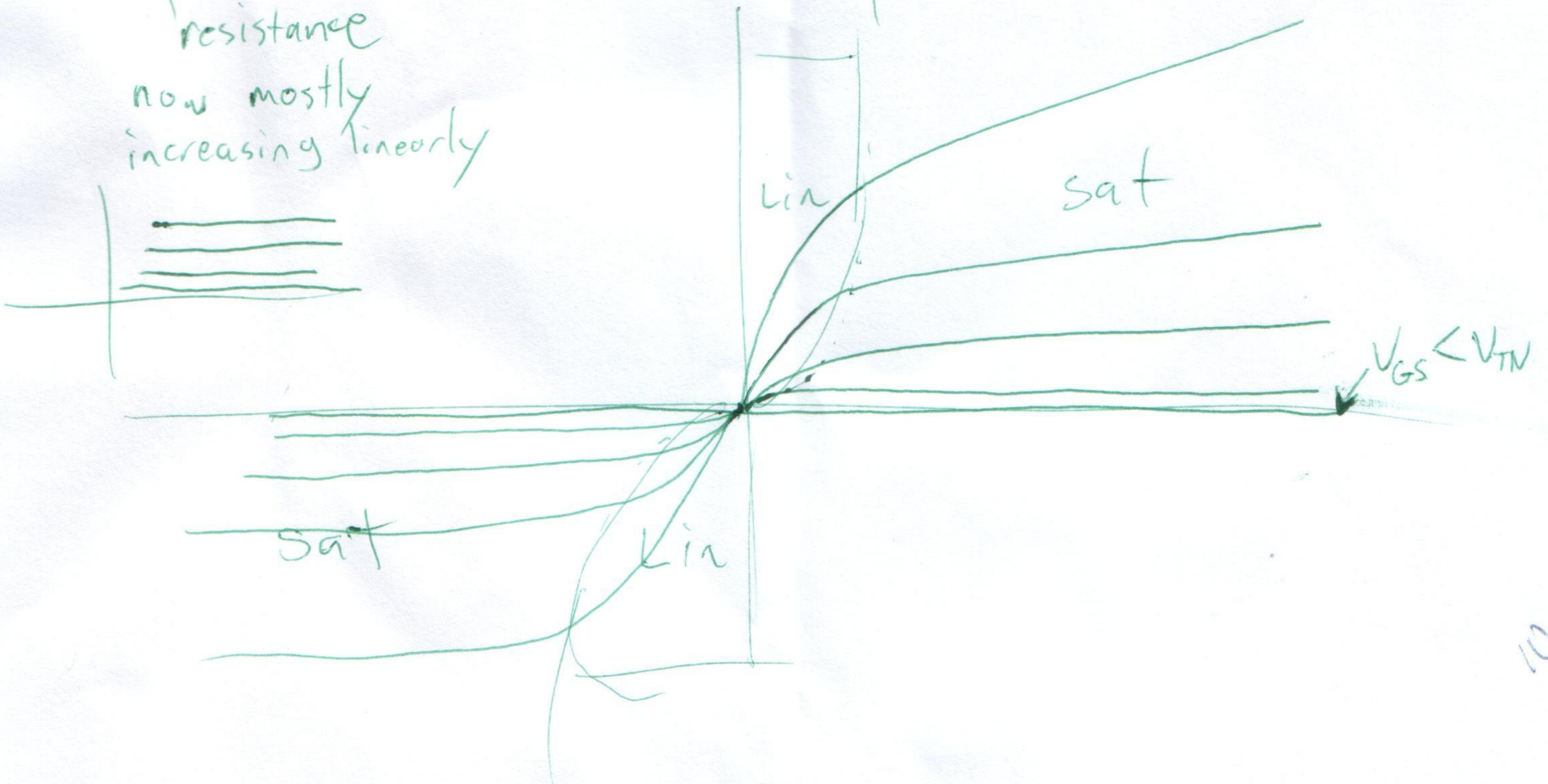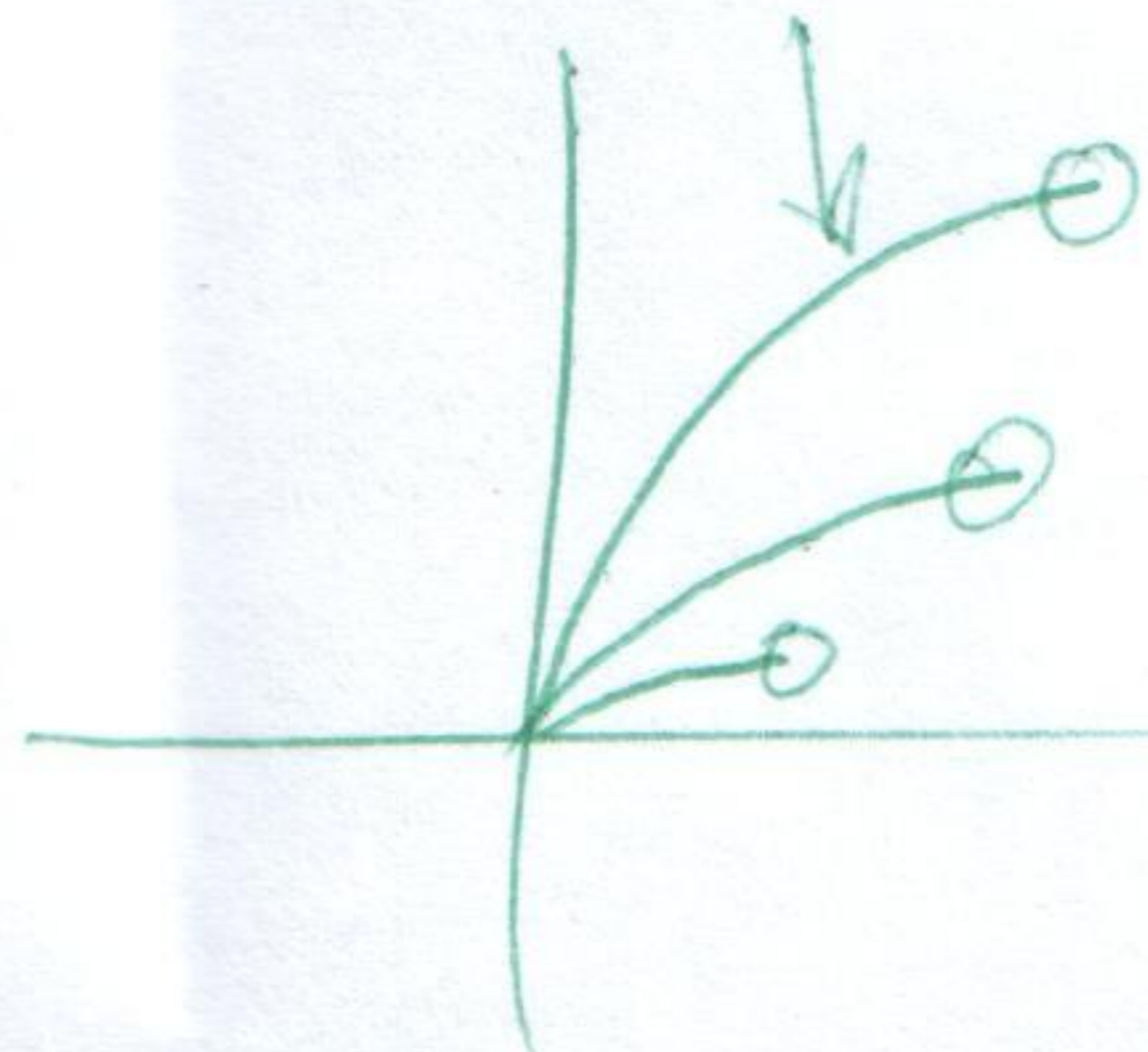resistance now mostly increasing linearly




$\frac{W}{L} \frac{K_n'}{2} V_{GS}^2$

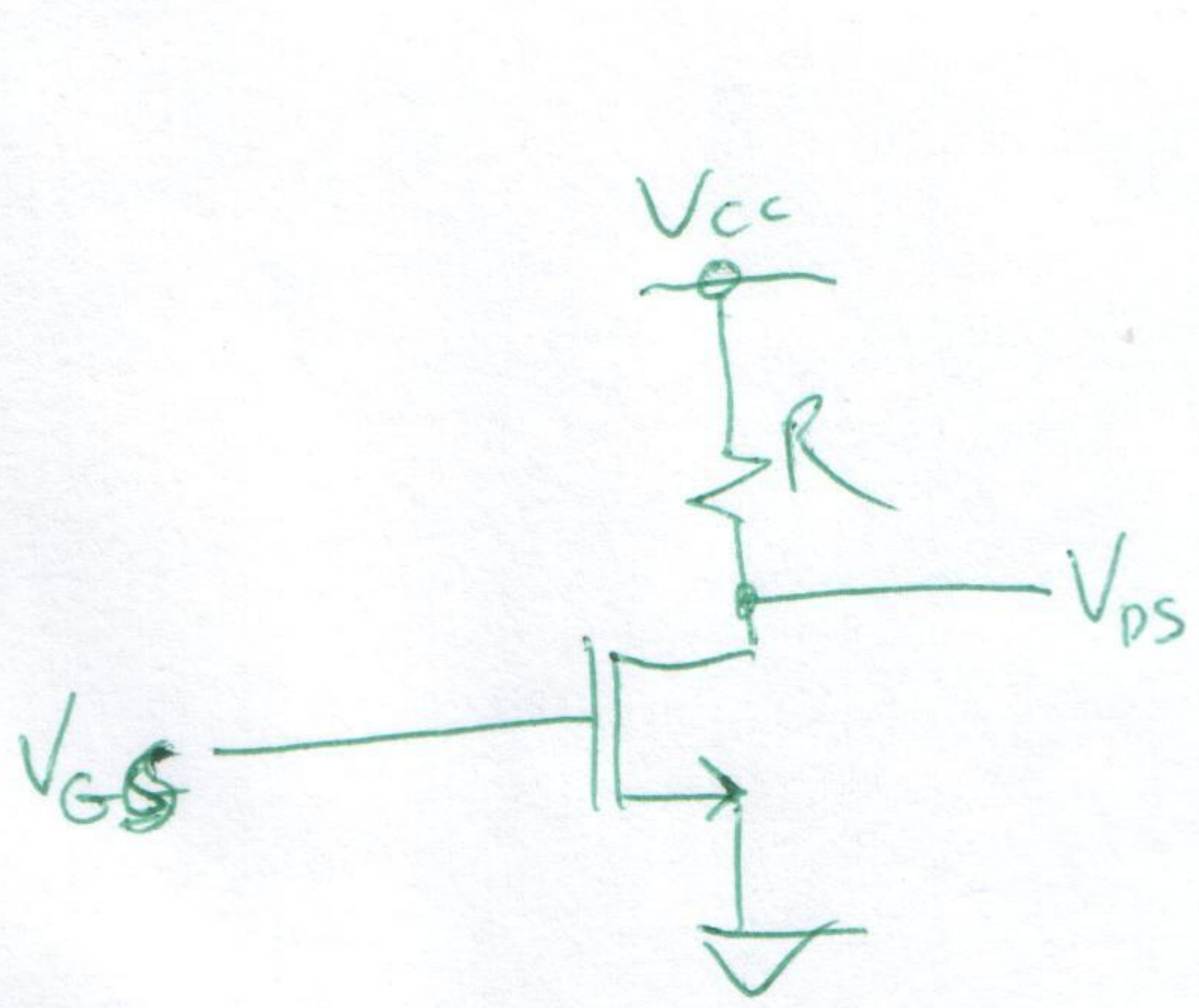

$K_n' = 25 \mu A/V^2$
 $V_{TN} = 1V$
 $\frac{W}{L} = 10$

$K_n = 250 \mu A/V^2$

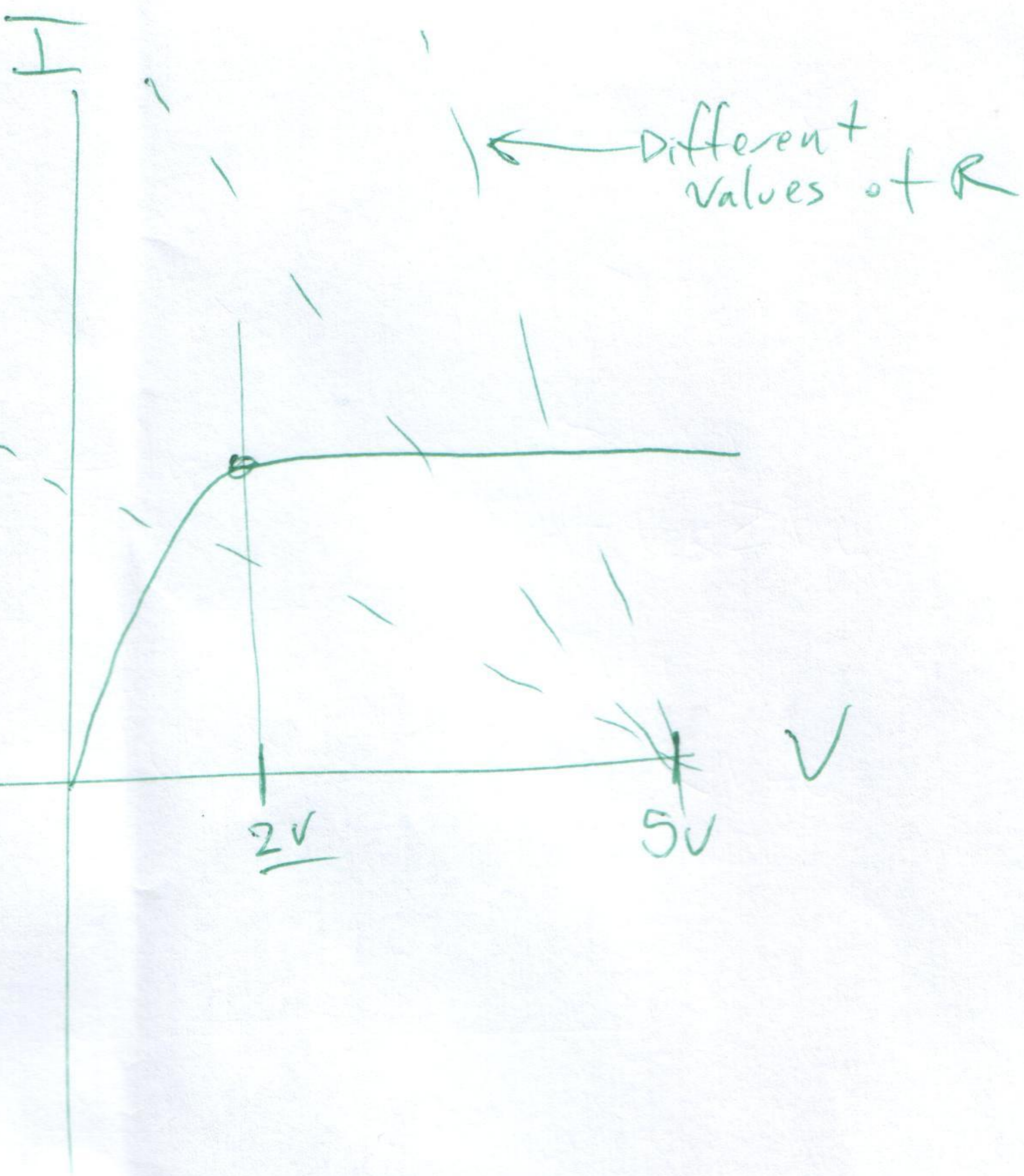

Problem: whether we're in sat. or lin. is dependent on I_D .

sat. current @ $V_{GS} = 3V$:



$I_D = 250 \mu A \cdot \frac{1}{2} \cdot (3-1)^2 = .5mA$

transition to lin-sat:


$V_{GS} - V_{DS} > V_{TN}$

$3 - V_{DS} > 1$

$V_{DS} < 2$

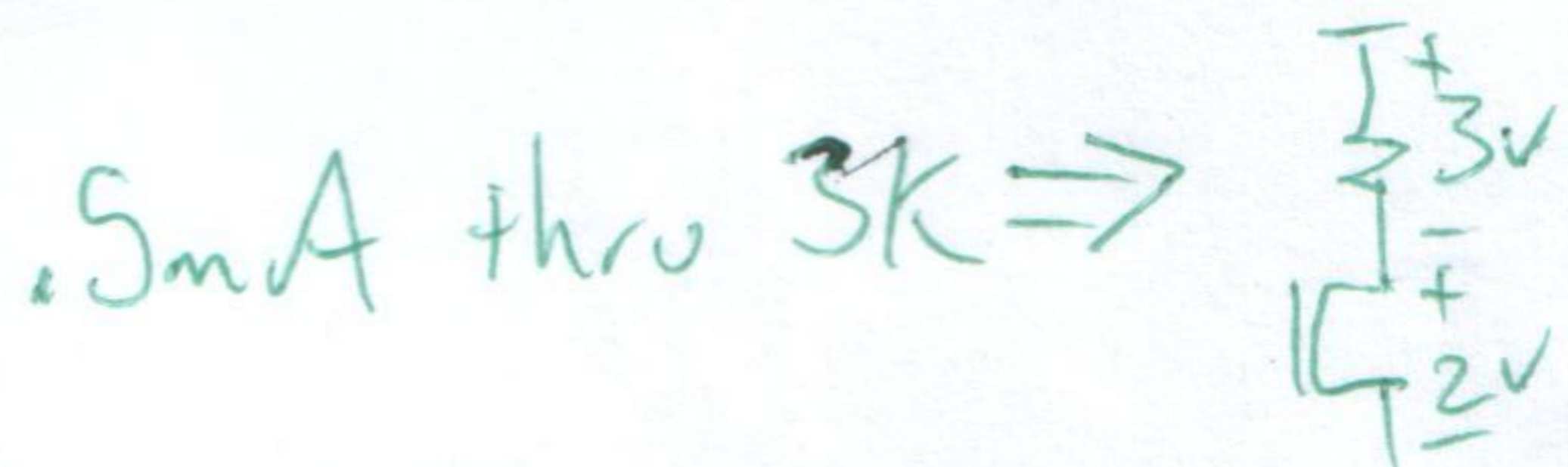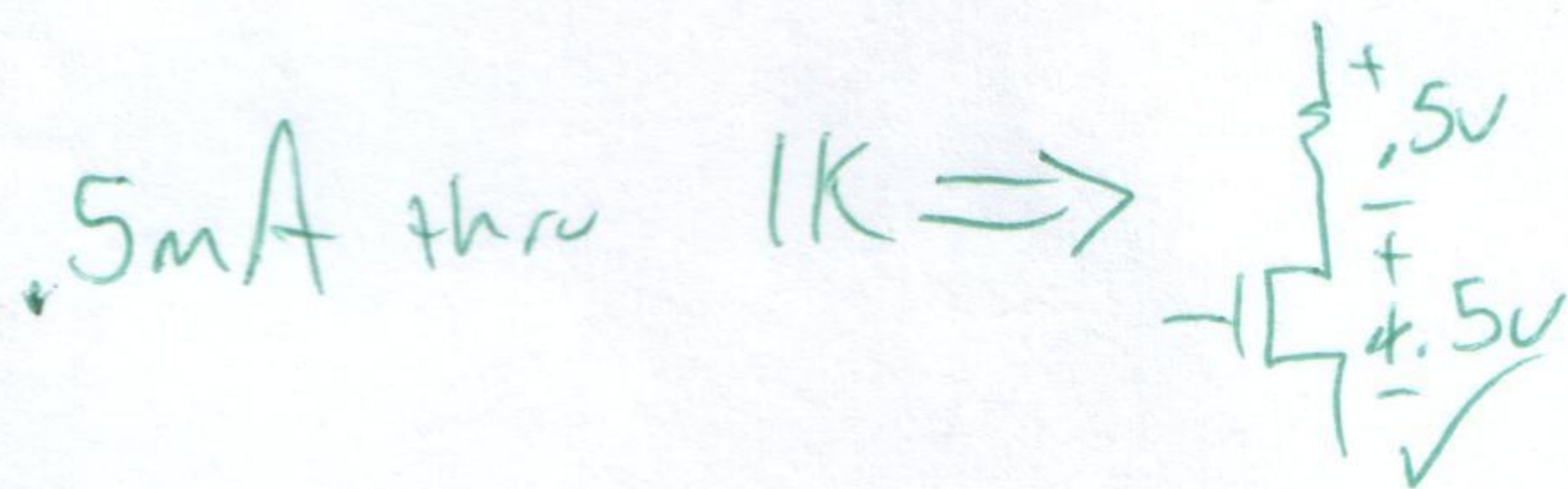

RIGHT ON THE EDGE

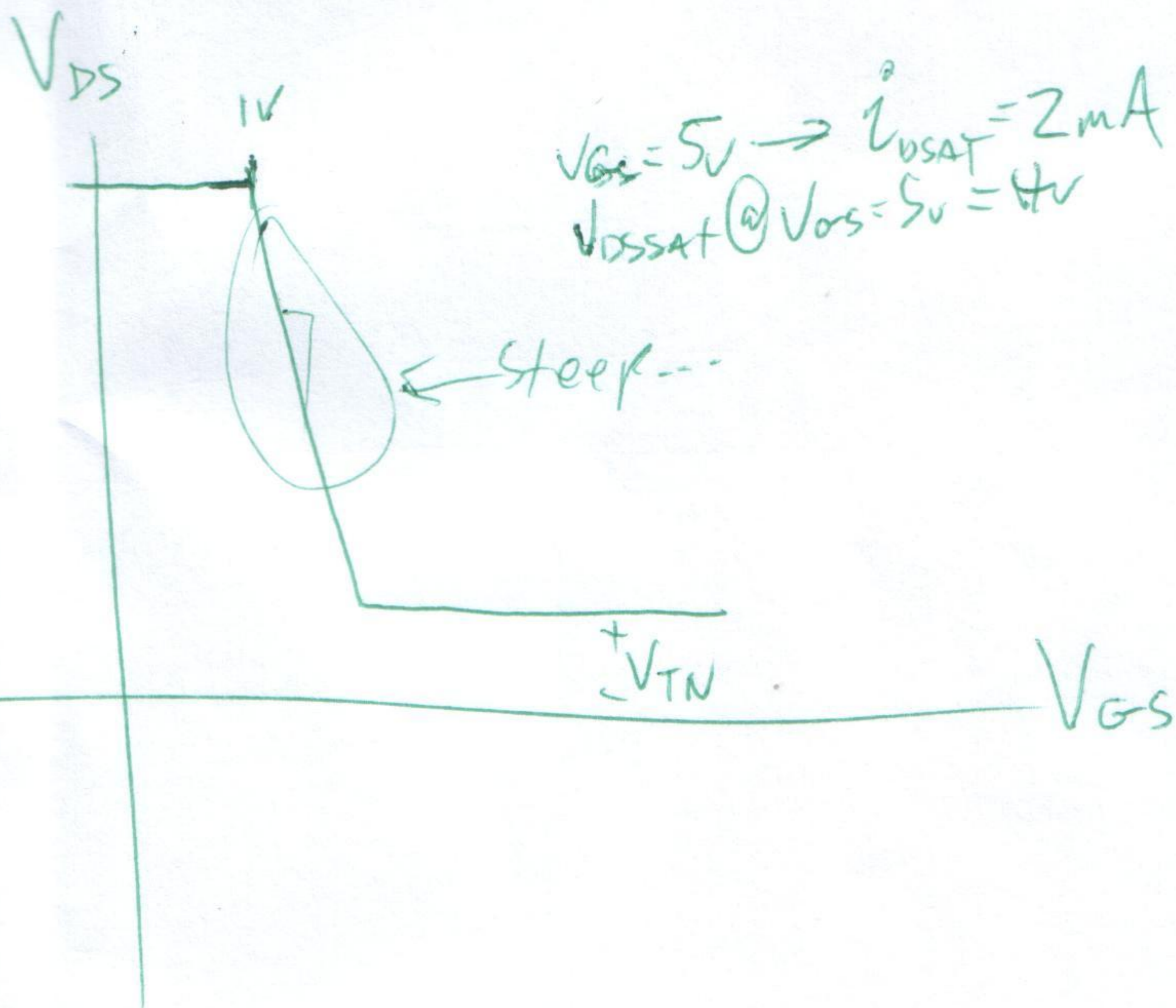



$$K'_n = 10 \mu\text{A}/\text{V}^2$$

$$w/L = 10$$

$$V_{TN} = 1\text{V}$$

$$R = \cancel{10\text{K}}$$



$$5\text{K}$$

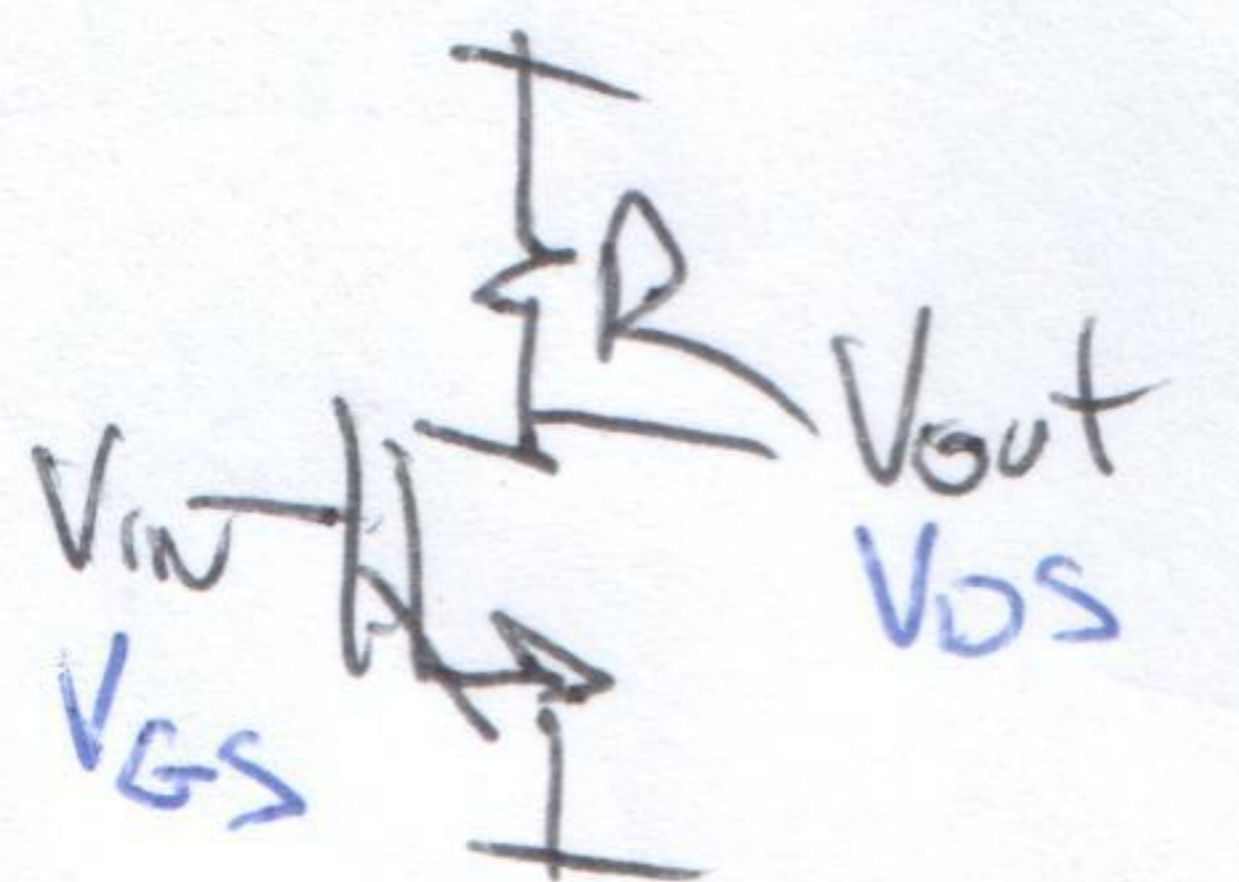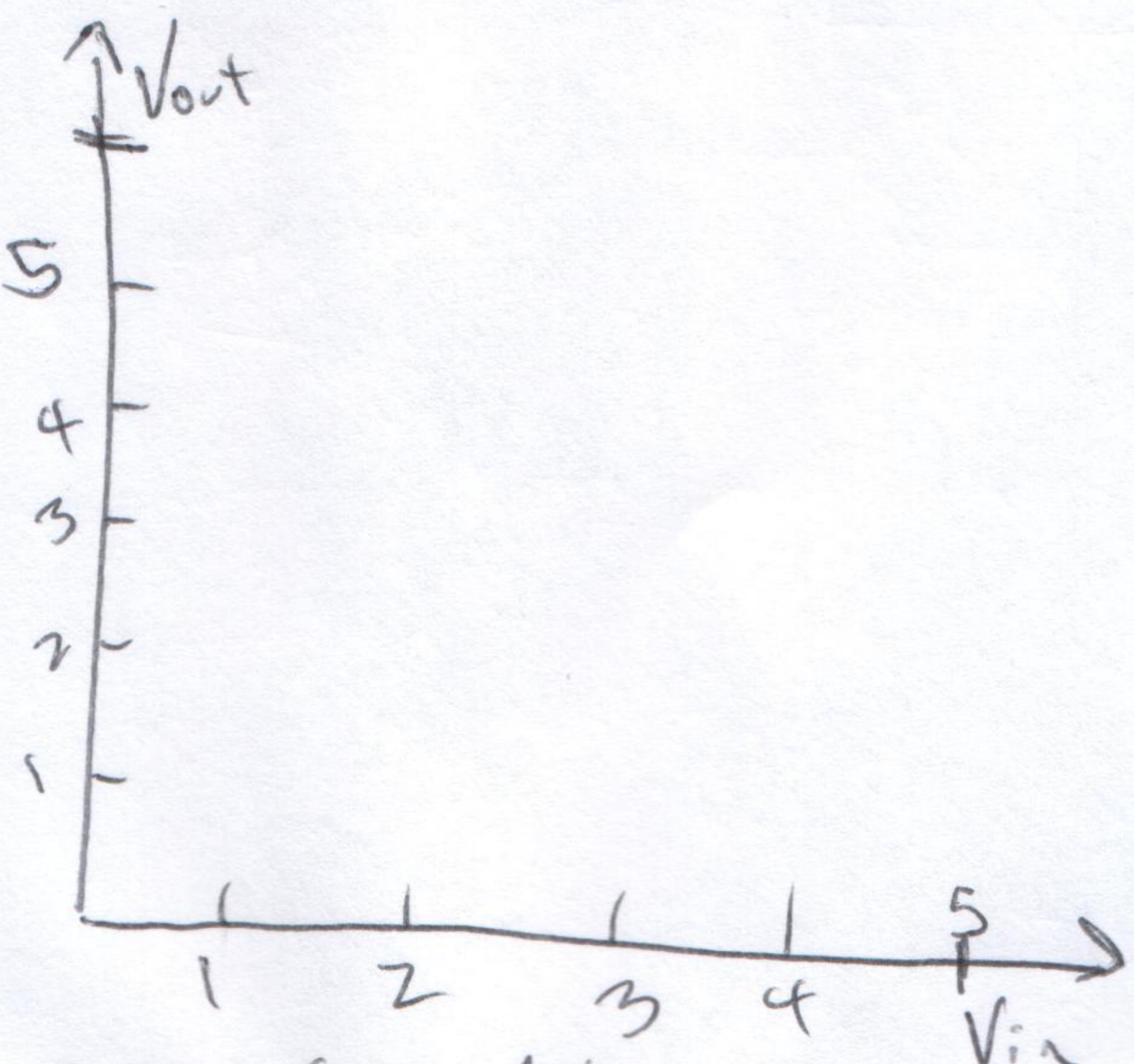


$$V_{GS} = V_{IN}$$

$$V_{DS} = V_{OUT}$$

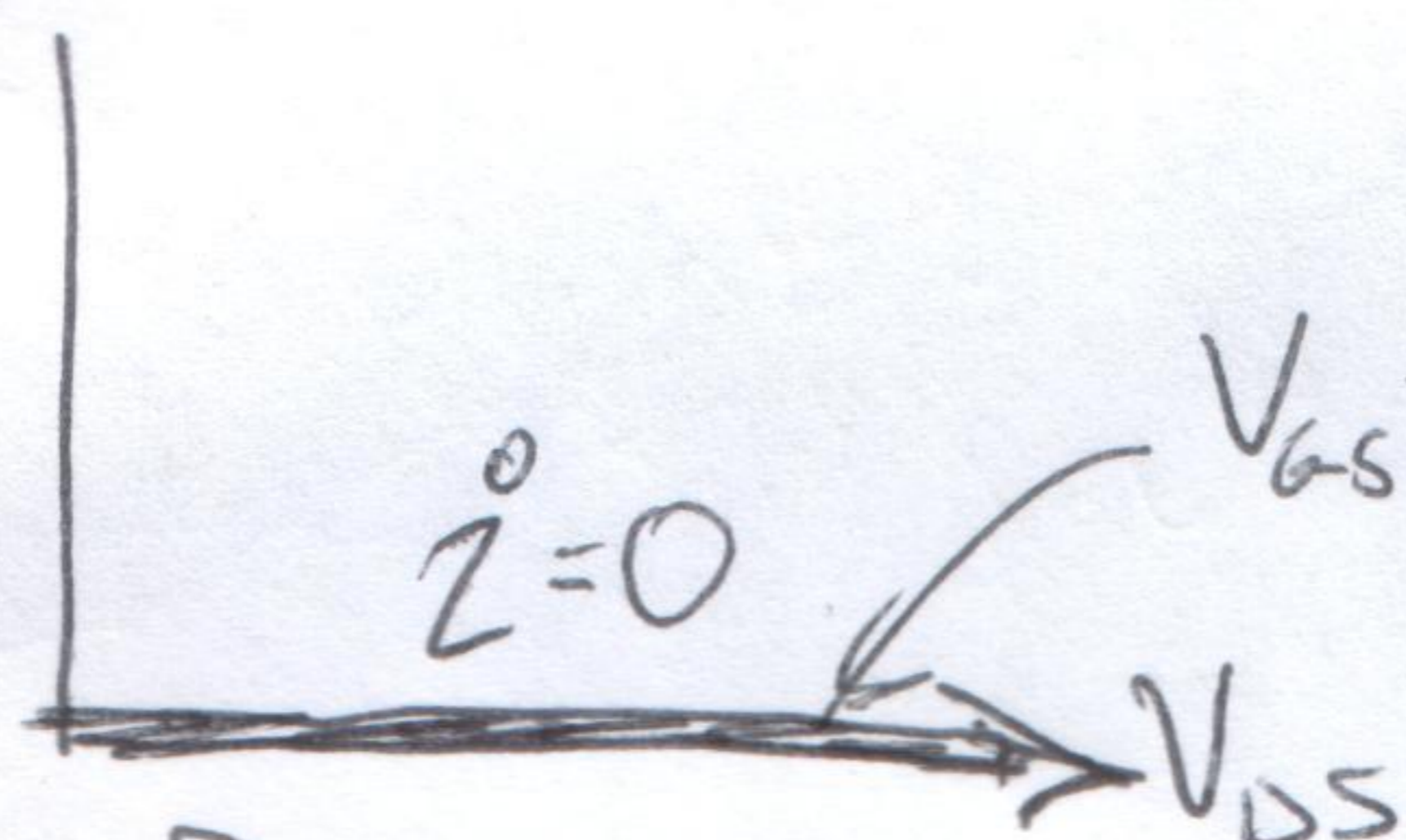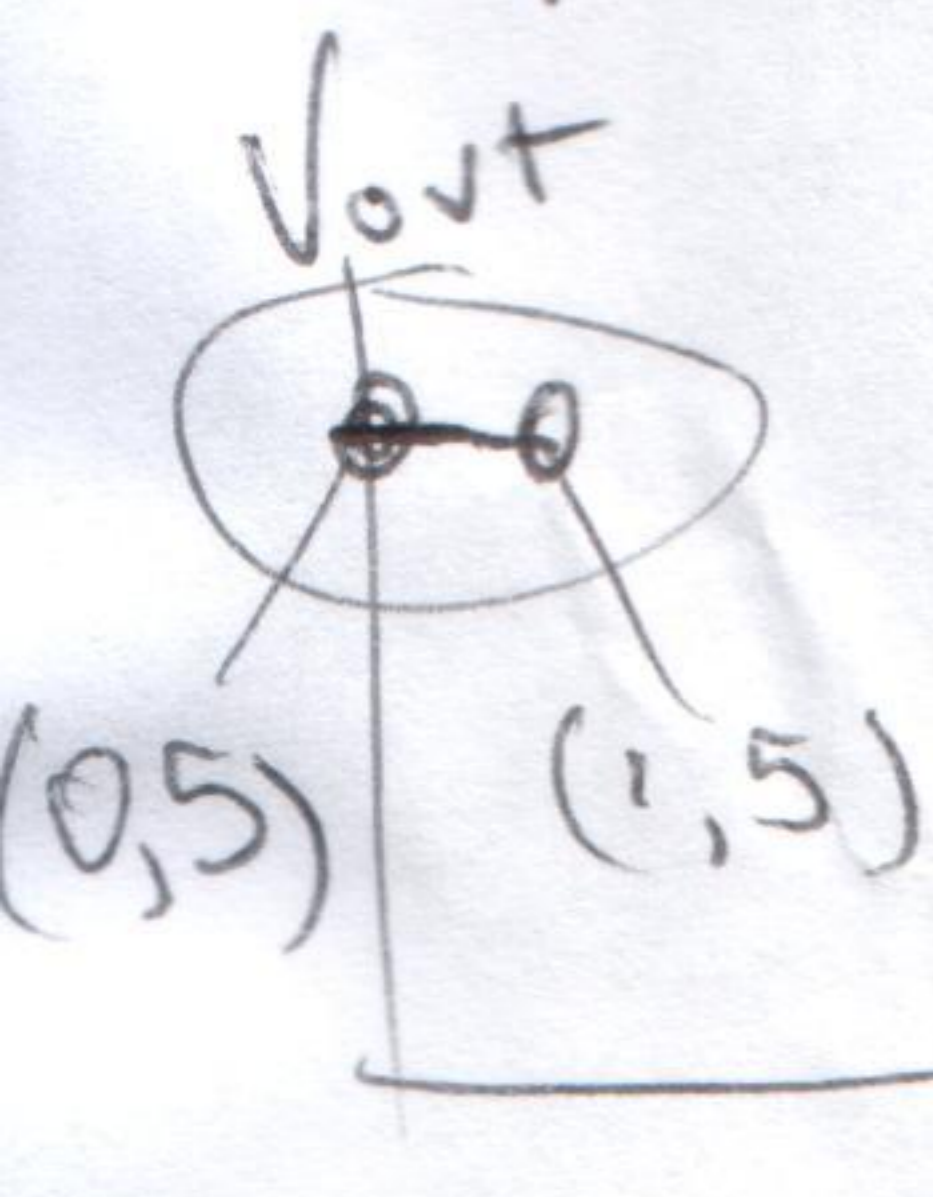Step 1: All $V_{GS} < V_{TN}$, $i = 0 \Rightarrow V_{DS} = 5\text{V}$



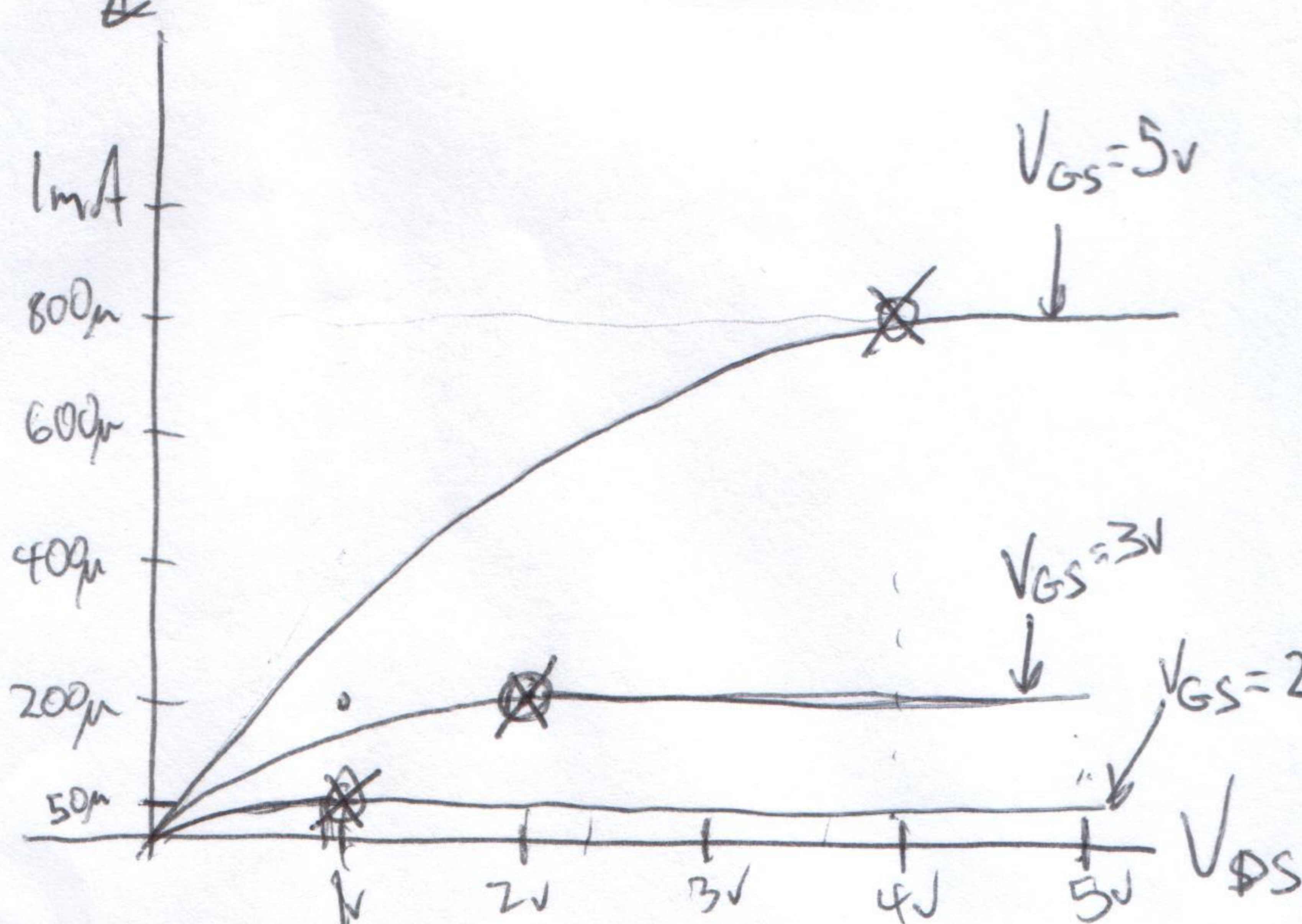Step 2: $V_{GS} = 2\text{V}, 3\text{V}, 5\text{V}$:



$V_{GS} = 0, V_{GS} = 1$

$i = 0$

$V_{GS} - V_{DS} > V_{TN} \quad [V_{DS} < 1\text{V}]$

$V_{GS} = 2\text{V}$: $i = 100 \mu\text{m} (V_{GS} - V_{TN} - \frac{V_{DS}}{2}) V_{DS}$

$i = 50 \mu\text{m} (V_{GS} - V_{TN})^2$ $[V_{GS} - V_{DS} < V_{TN} \quad [V_{DS} > 1\text{V}]]$

for $V_{GS} = 2\text{V}$, $V_{DS} = 1\text{V}$ @ sat. thresh. & $i = 50 \mu\text{A}$

$V_{GS} = 3\text{V}$: $i = 100 \mu\text{m} (V_{GS} - V_{TN} - \frac{V_{DS}}{2}) V_{DS}$

$i = 50 \mu\text{m} (V_{GS} - V_{TN})^2$ $[V_{GS} - V_{DS} < V_{TN} \quad [V_{DS} > 2\text{V}]]$


$V_{DS} = 2\text{V}$, sat. thresh. $i = 200 \mu\text{A}$

$V_{GS} = 5\text{V}$: $i = 100 \mu\text{m} (5 - 1 - \frac{V_{DS}}{2}) V_{DS}$

$i = 50 \mu\text{m} (5 - 1)^2$ $[V_{GS} - V_{DS} < V_{TN} \quad [V_{DS} > 4\text{V}]]$


Step 3:

Load-Line

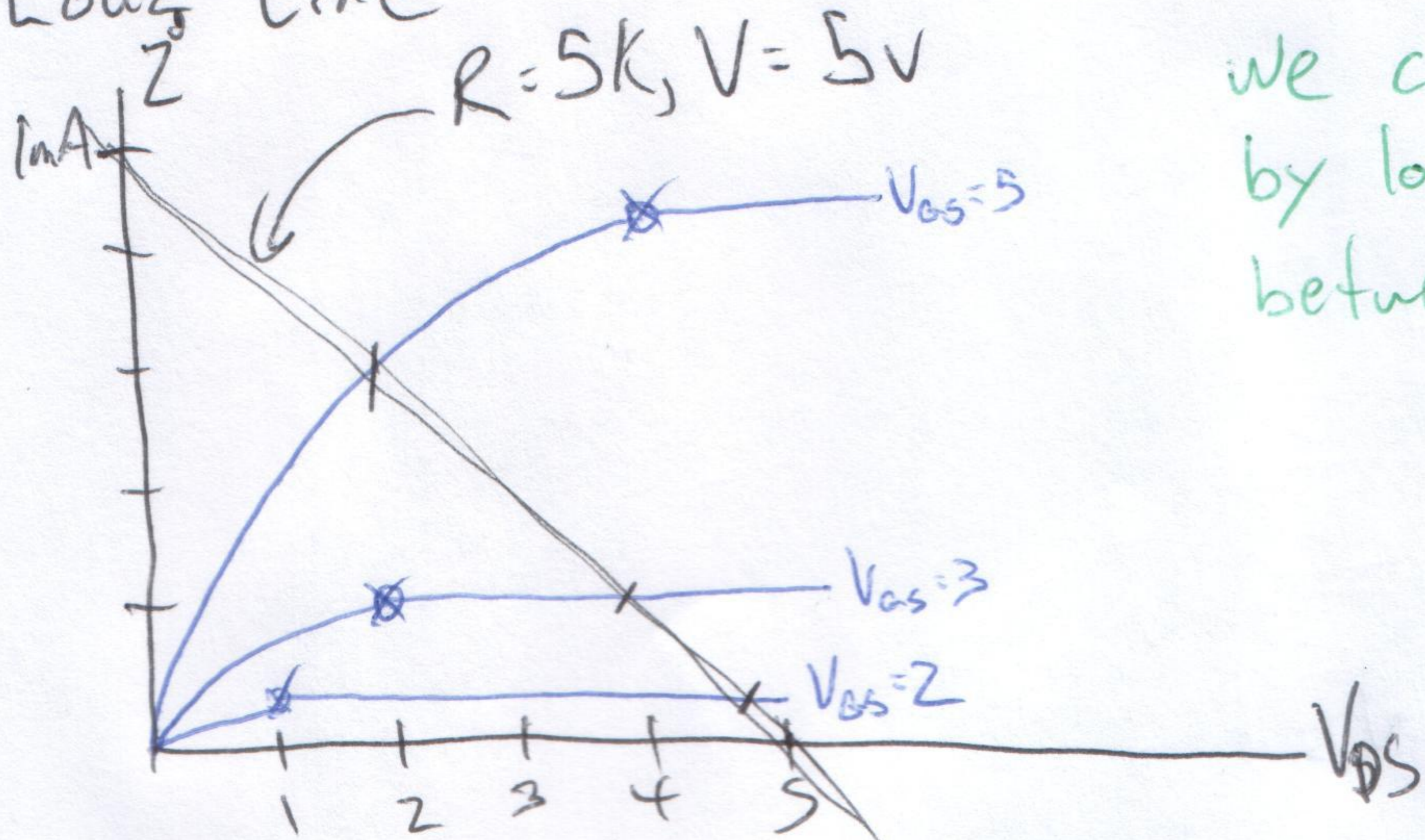

we can solve graphically by looking for crossing points between R and the Transistor.

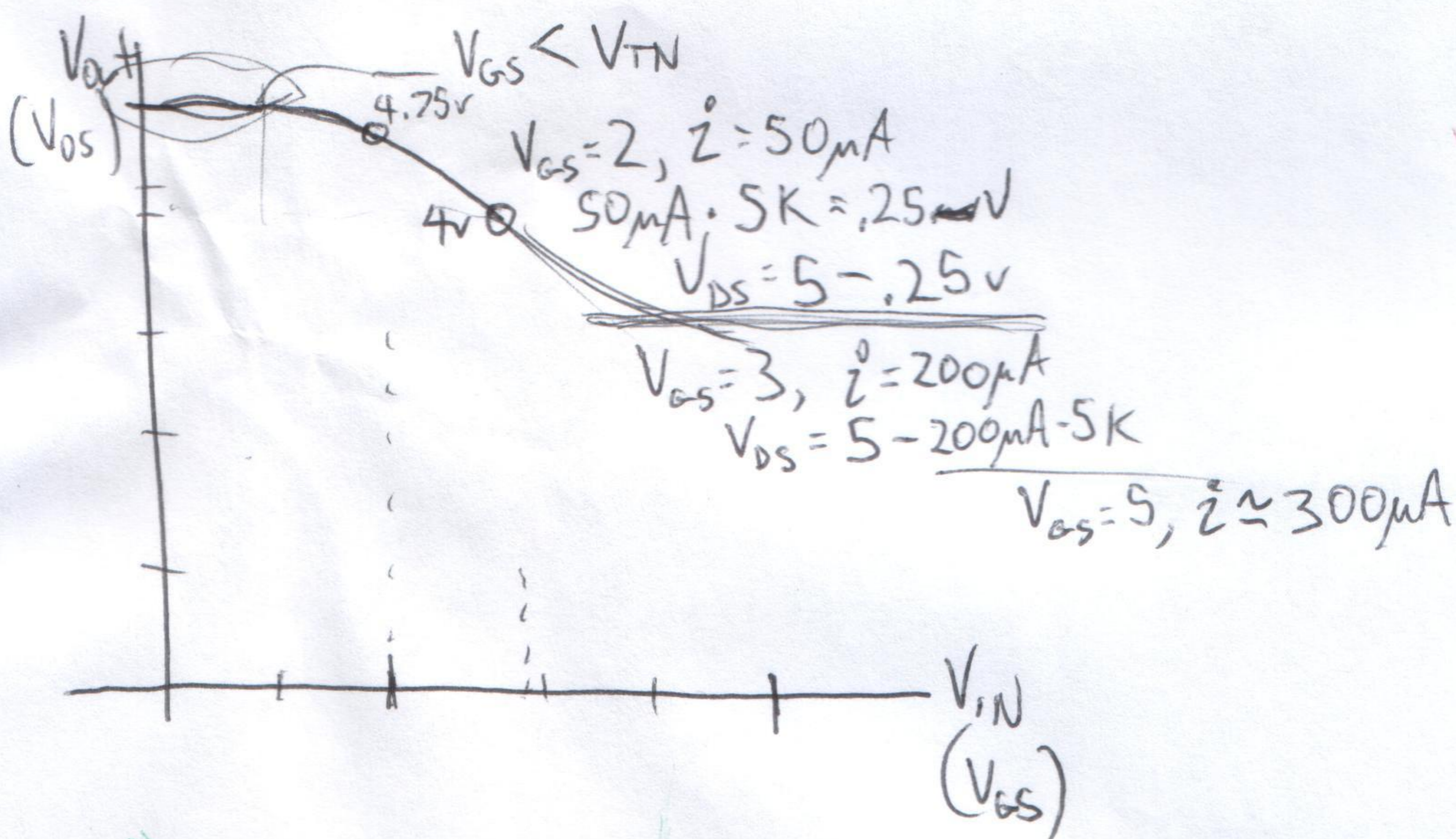
$V_{DS} \rightarrow V_{out}$ $V_{GS} \rightarrow V_{in}$



Wow, this is terrible! needs to be much bigger!


$R \rightarrow$

$R \rightarrow 20k\Omega$

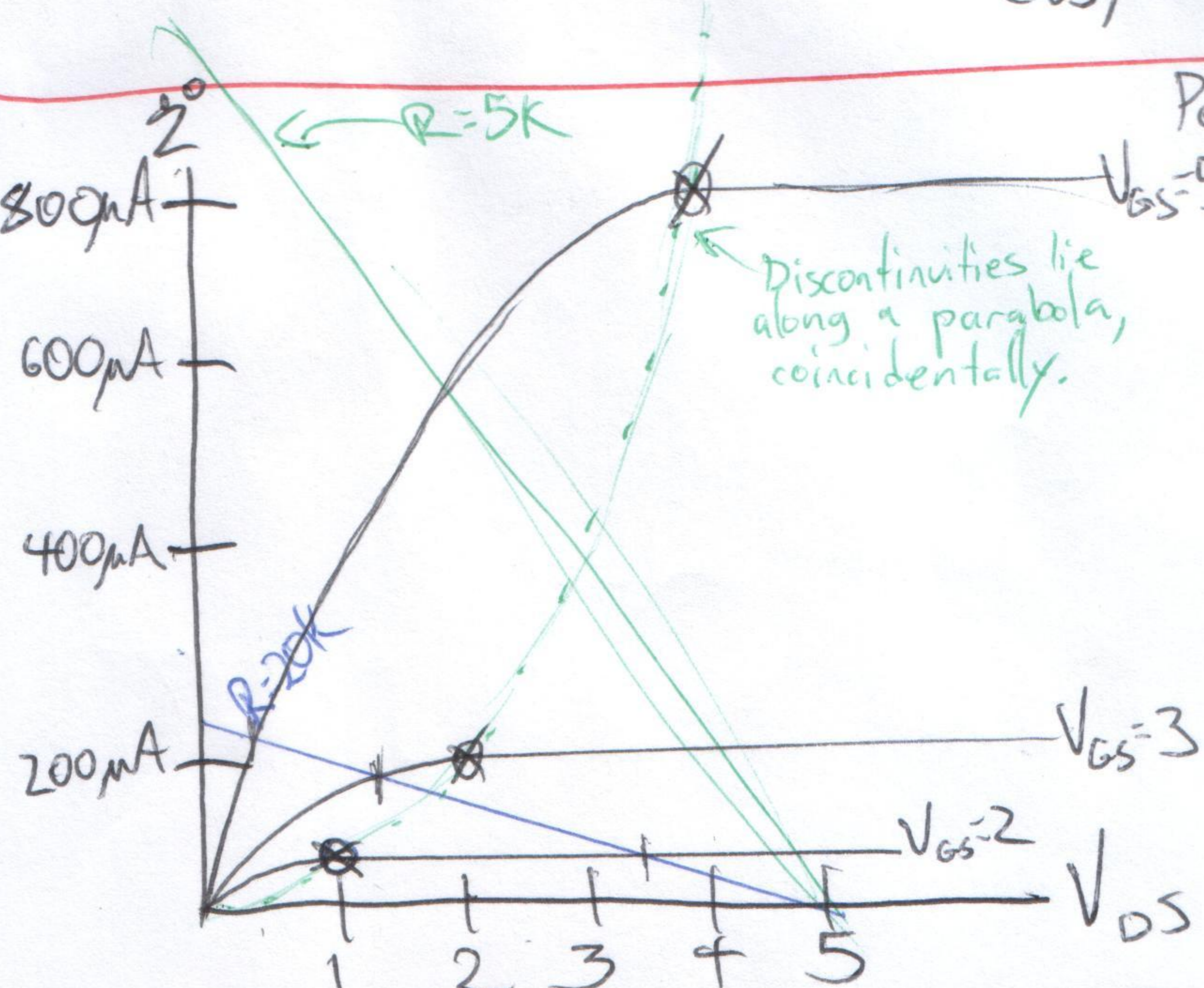


Point 1, Device current is all THE SAME. I_D is only from V_{GS} & V_{DS}

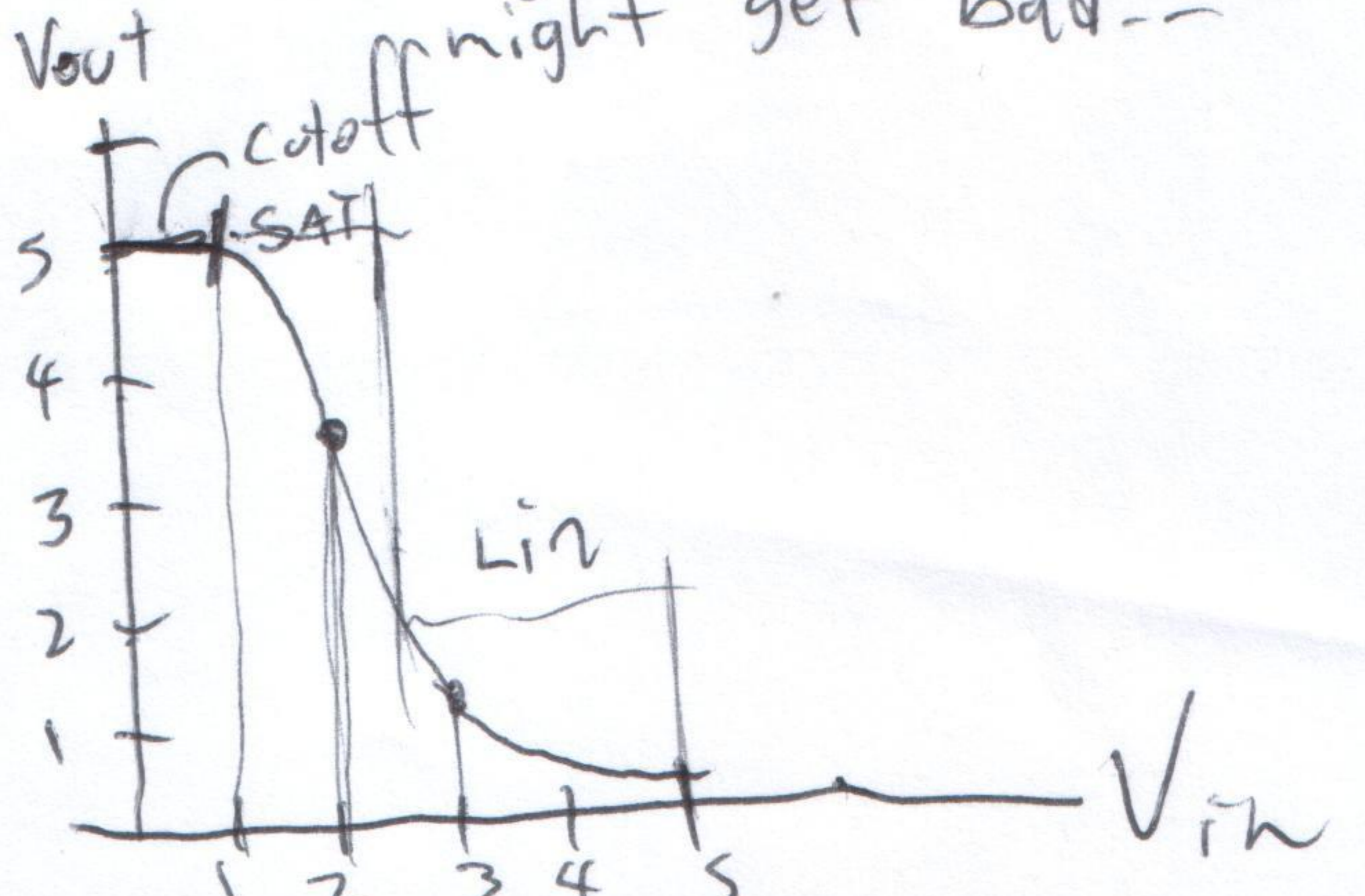Point 2, at high R , RC time const. might get bad--




Transient Behavior:

RC vs Harsh Reality

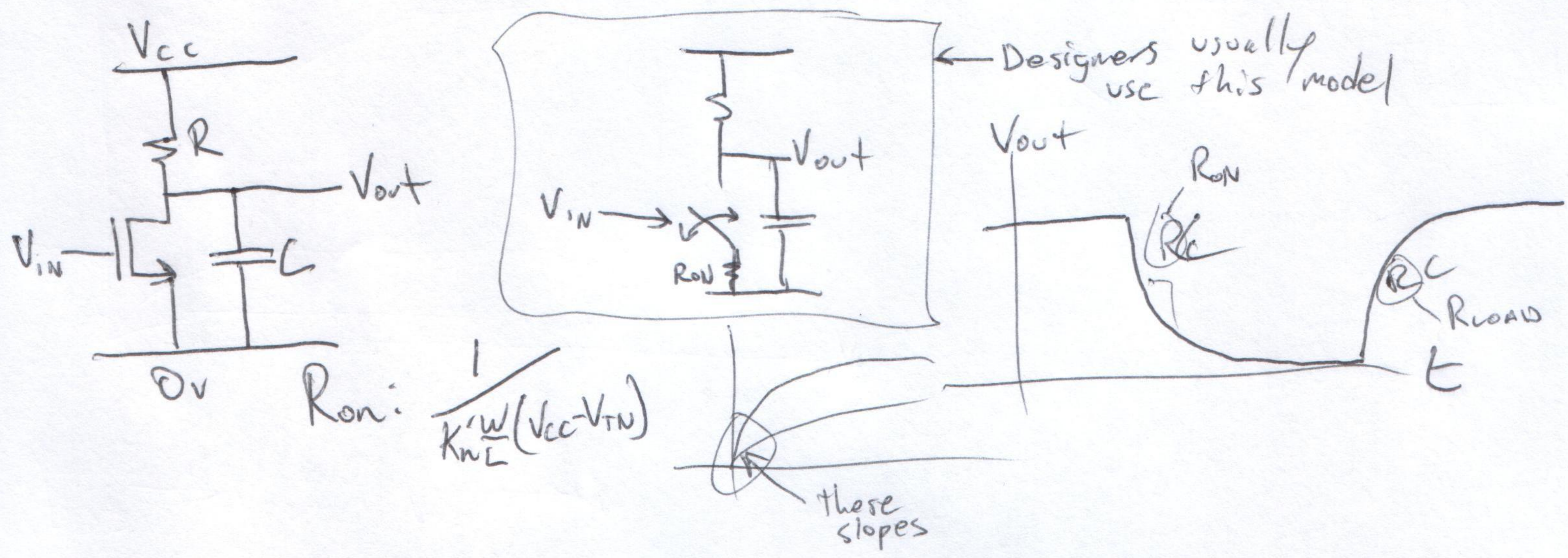

Cold, harsh reality:

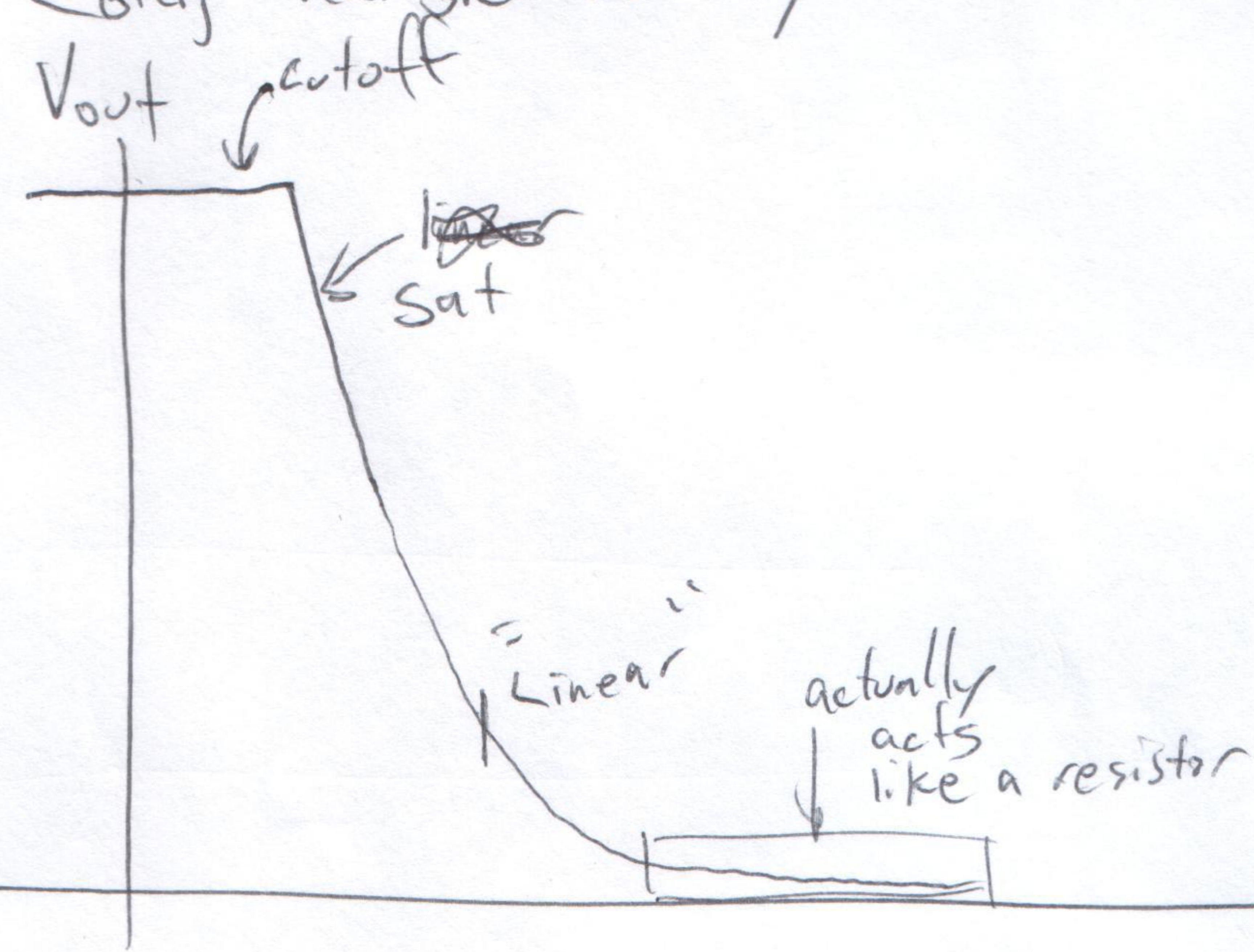

Your Homework: simulate this!


- calculate: rough RC time constant calculation
 - set $\Delta t \ll RC$ and compute the actual curve for ~~of~~ this system.
- (This isn't as terrible as it sounds, just find V_{DS} over and over for new amounts of i pulled off C)

So Chapter 6 is kinda busted.

V_L, V_H : The "ideal" high/low

V_{OH}, V_{OL} : Output levels } defined by slope = 1 points

V_{IH}, V_{IL} : Input levels }

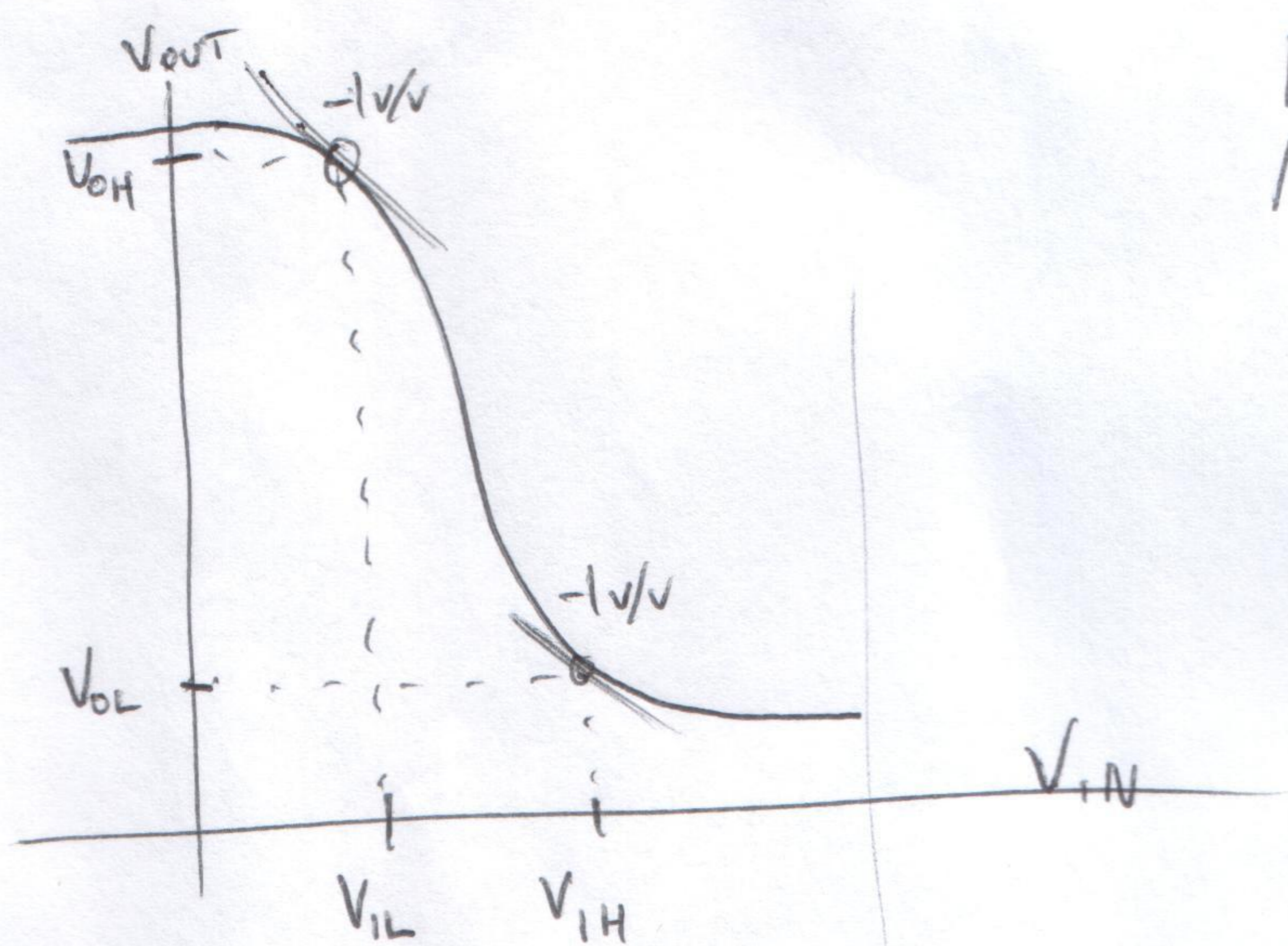

$NM_H = V_{OH} - V_{IH}$
 $NM_L = V_{OL} - V_{OL}$ } somewhat blurry idea of "safety"

Rise, Fall times:

