
 


Ron & Gates:

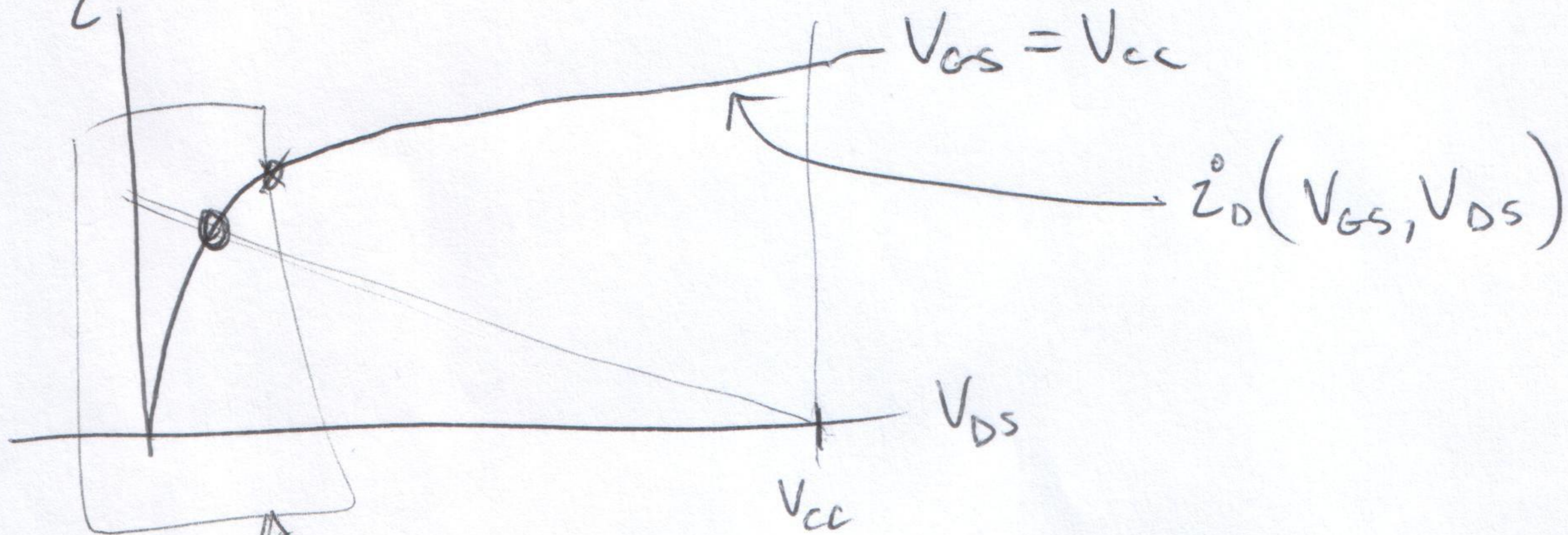

i_D Picking w/L



for a good inverter, i_D in linear range

R:

$$i_D \cdot R = V_{CC} - V_{DS}$$

M_n :

$$i_D = K_n' \frac{W}{L} \left(V_{CC} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$$




* Pick a value of V_{DS} [$V_{DS} = V_L$]

* set $\frac{V_{CC} - V_{DS}}{R} = K_n' \frac{W}{L} \left(V_{CC} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$


$$\left[\frac{W}{L} \right] \cdot [R] = \frac{V_{CC} - V_{DS}}{K_n' \left(V_{CC} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}}$$

for a chosen value of V_{CC}/V_{DS} , $\frac{W}{L}$ or R determine each other.



The Warmup.

 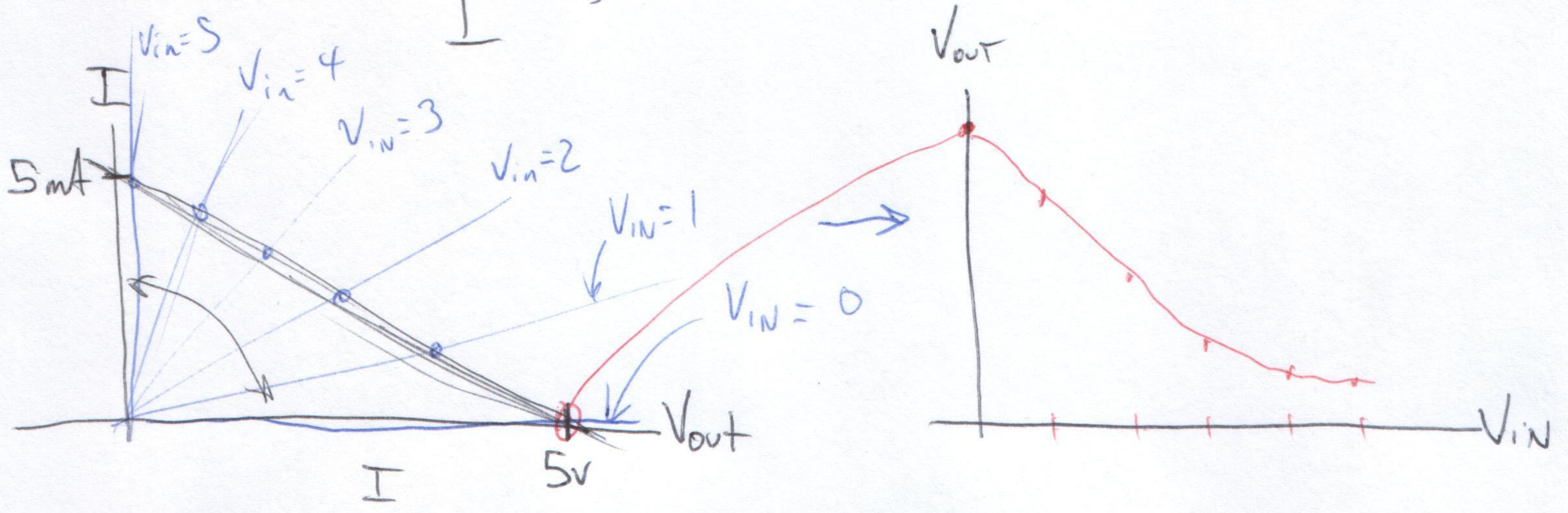 



What we did yesterday:

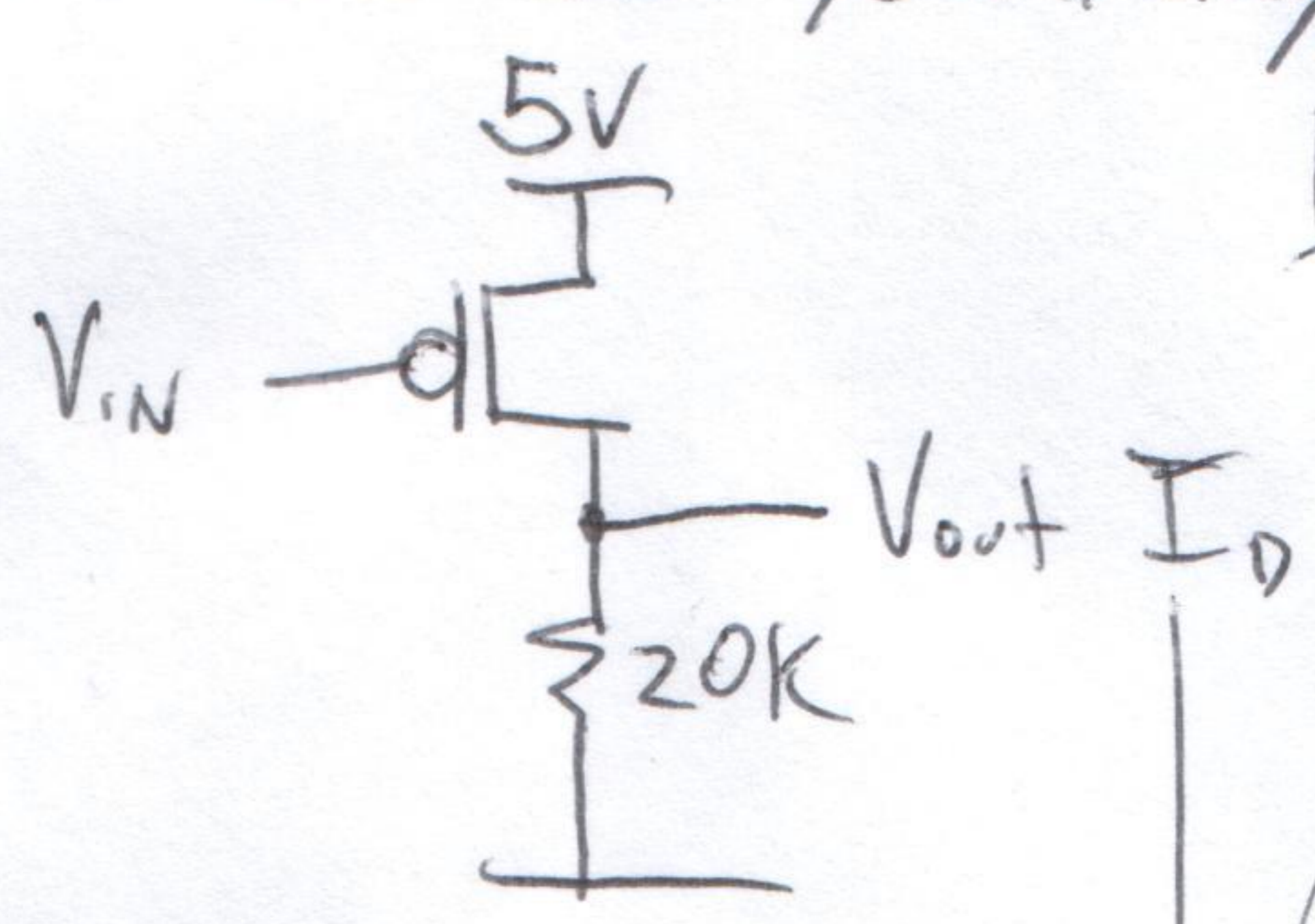




 
 
$K_p' = 10 \mu A/V^2$
 $\frac{W}{L} = 10$
 $K_p' = 5 \mu A/V^2$
 $\frac{W}{L} = 20, V_{TP} = 1V$
 ← same $K_p \cdot \frac{W}{L}$ as last NMOS inv.



CMOS:

  


NMOS FIRST

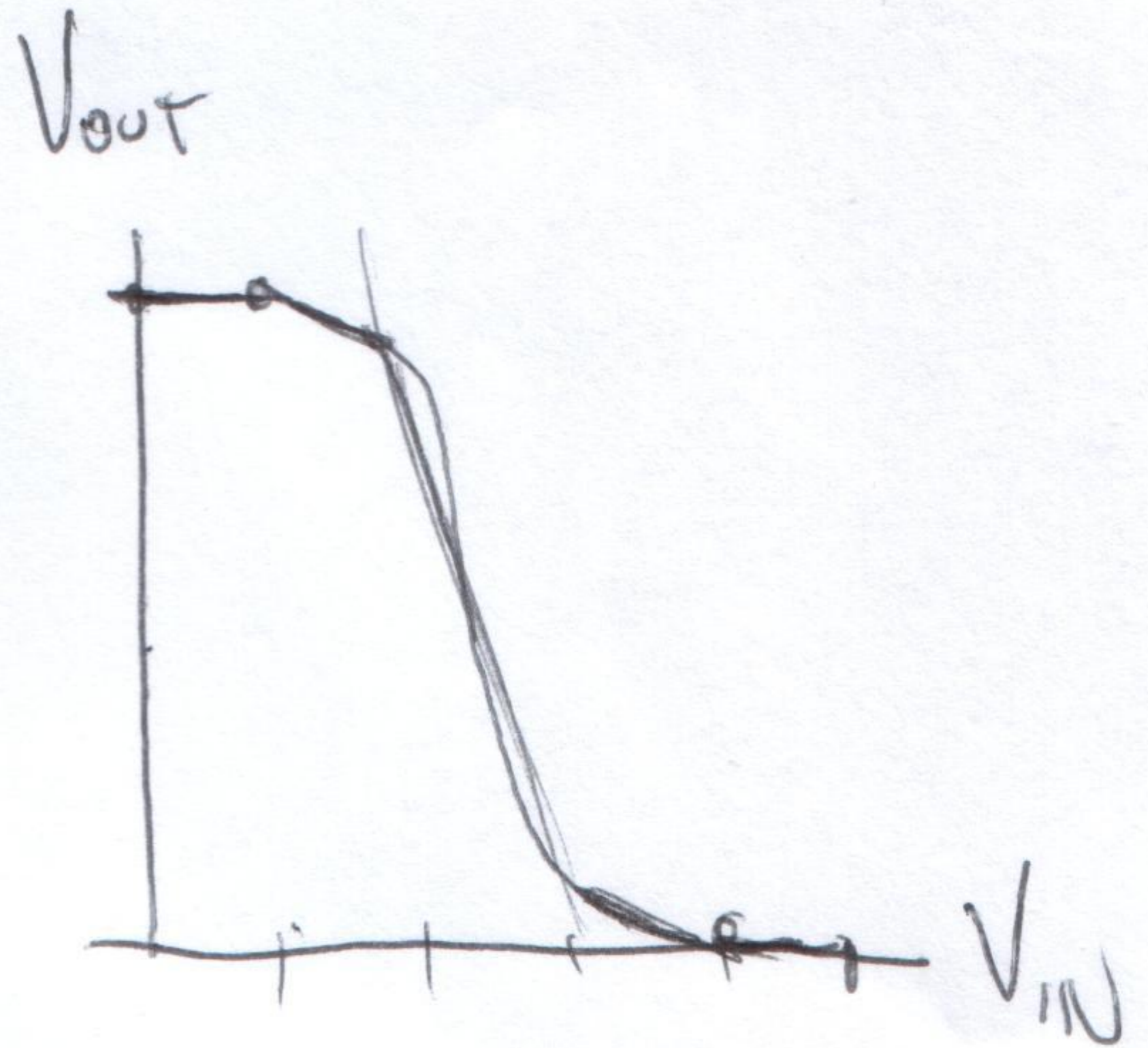 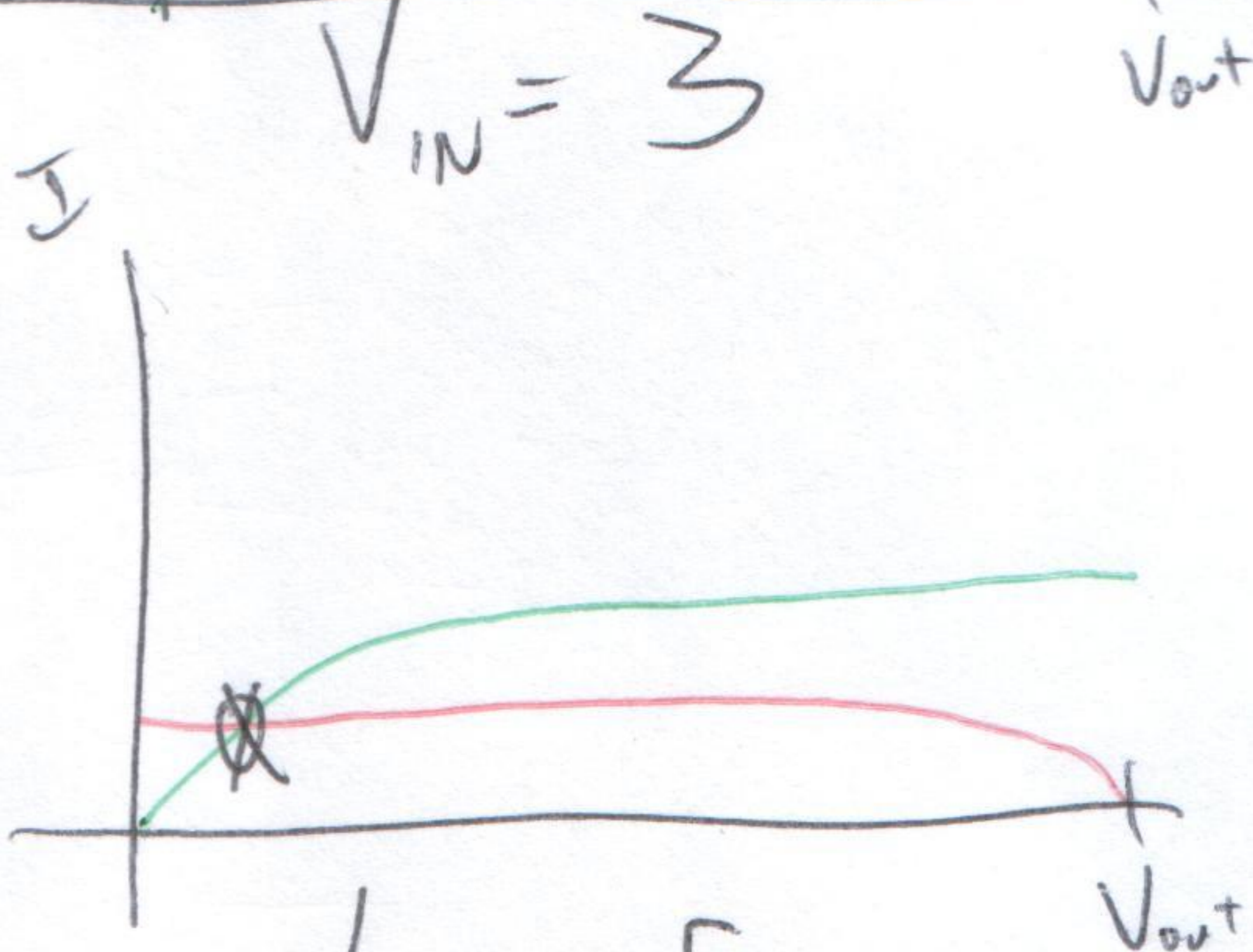 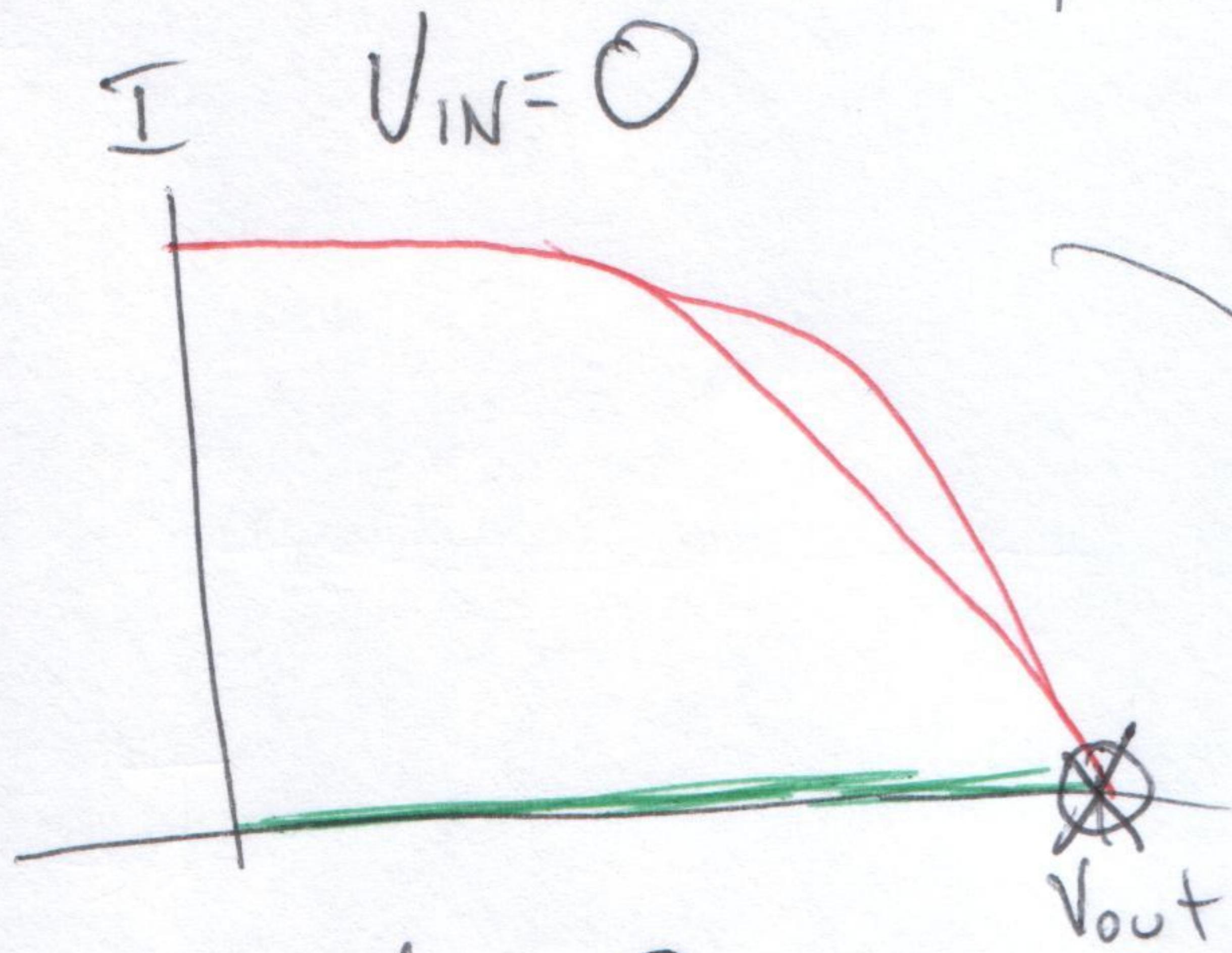

Note: I am aware this is revolting.

This is the analysis you do to get details about something you will usually lock in a box and try very hard to forget.

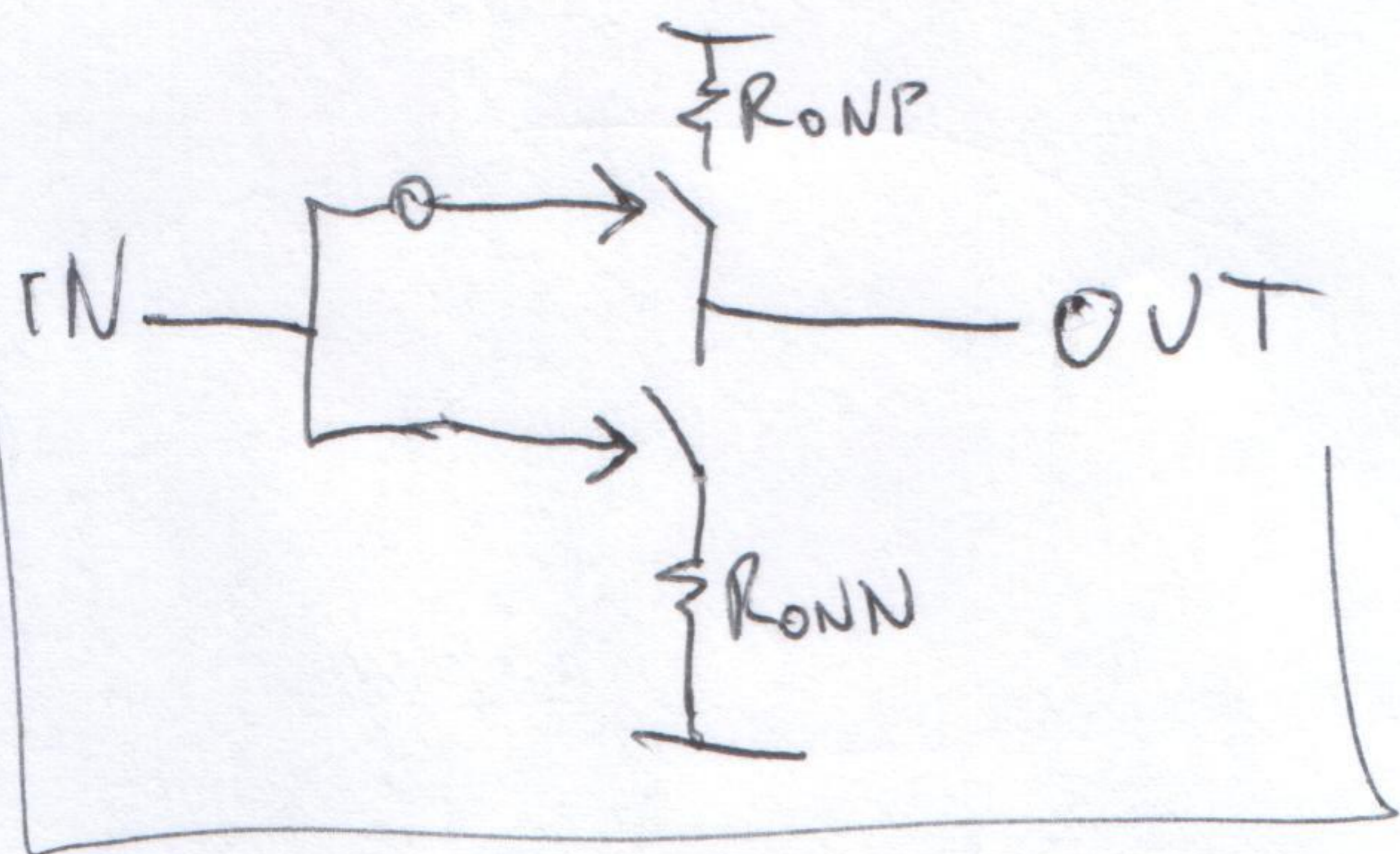
CMOS, as you will think of it from here out:




$$R_{ONP} \propto K'_P \frac{W_P}{L_P}$$


$$R_{ONN} \propto K'_N \frac{W_N}{L_N}$$

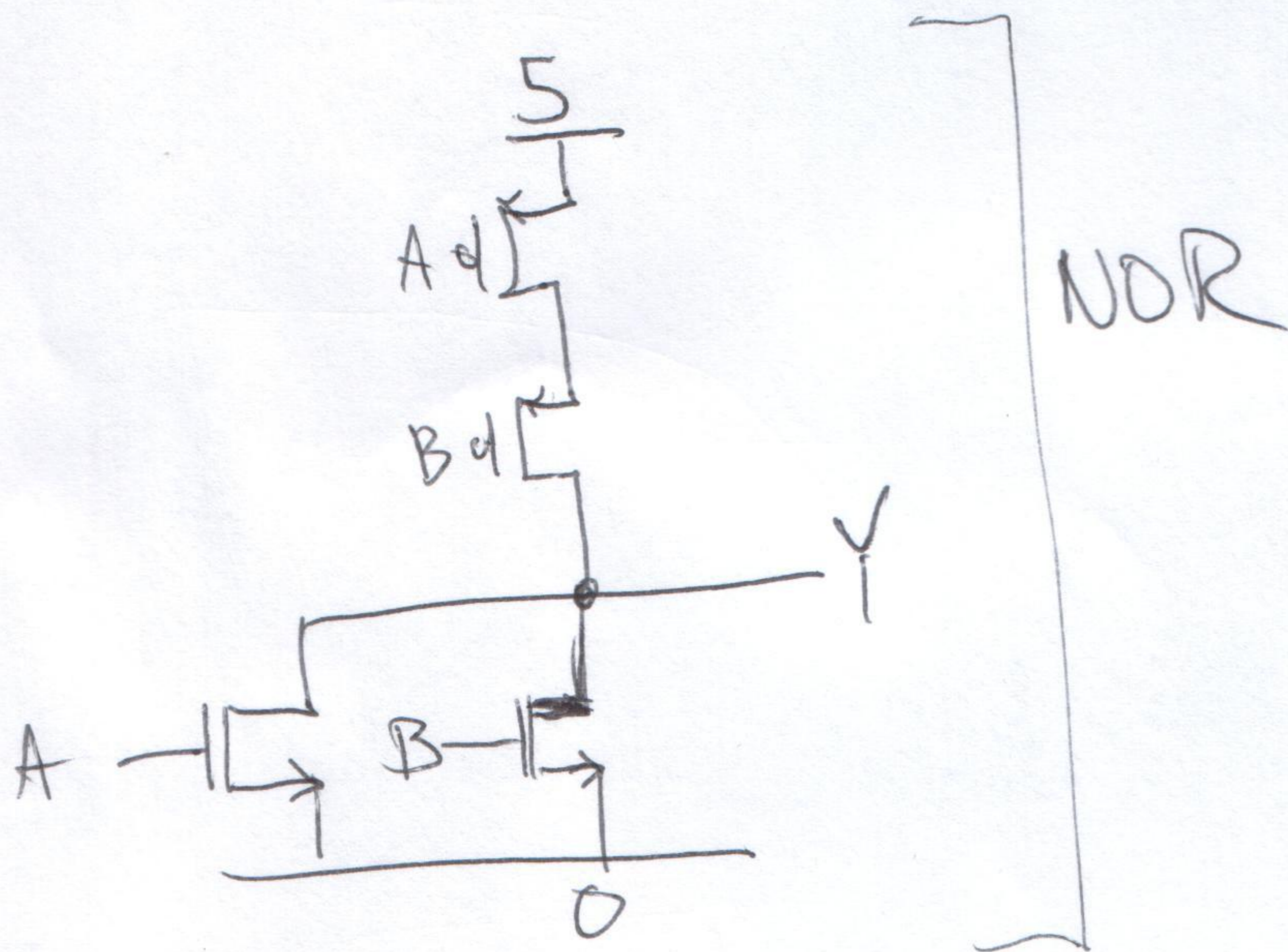except for special cases where you will need an expert.




 

Logic:


 


NOR
Not-OR

 



NAND
Not-And

Delay design:

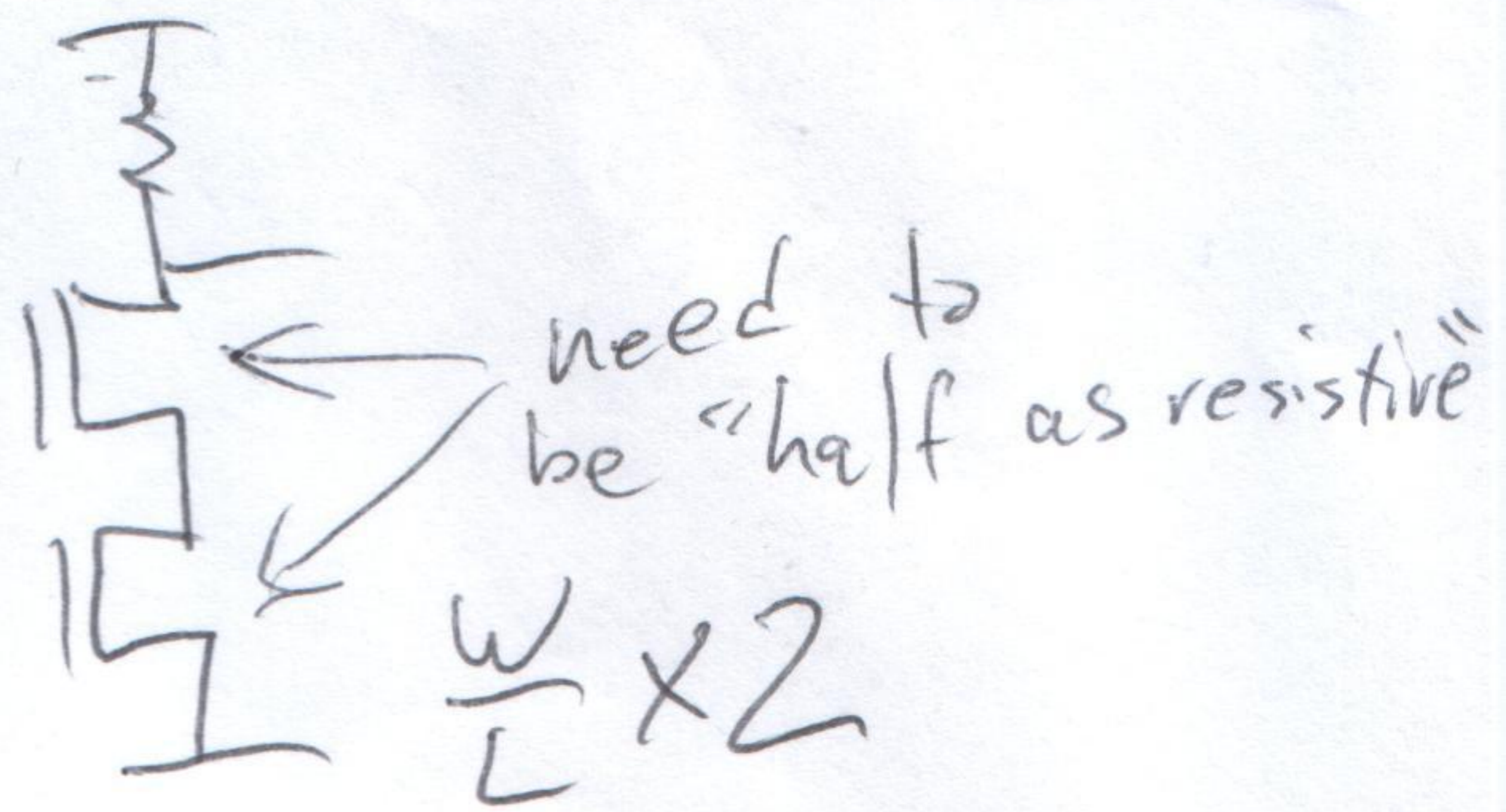 


System Resources:


 
 
literally anything that conceivably is needed
by more than one thing




I don't want
to draw this

 

CMOS:

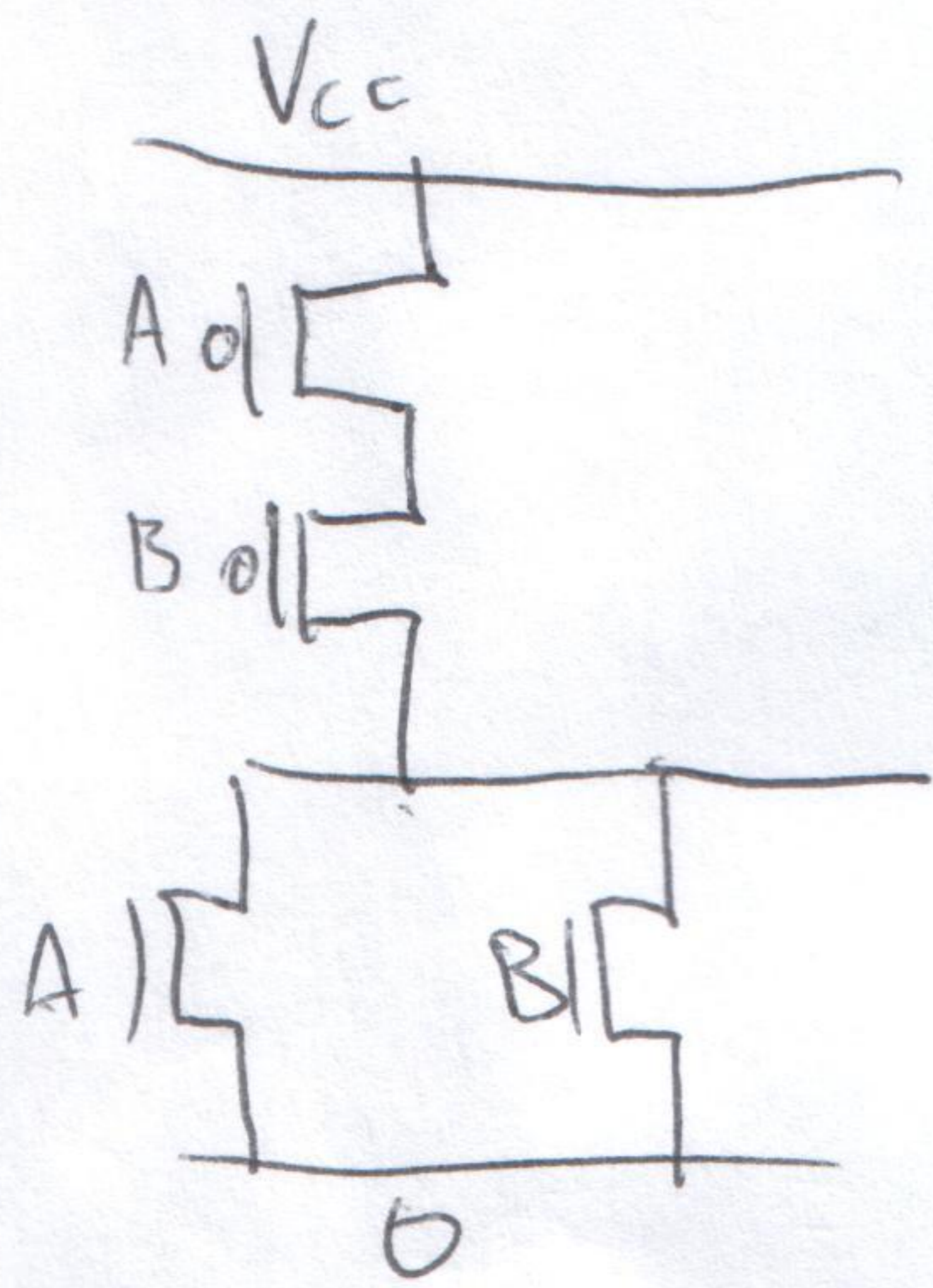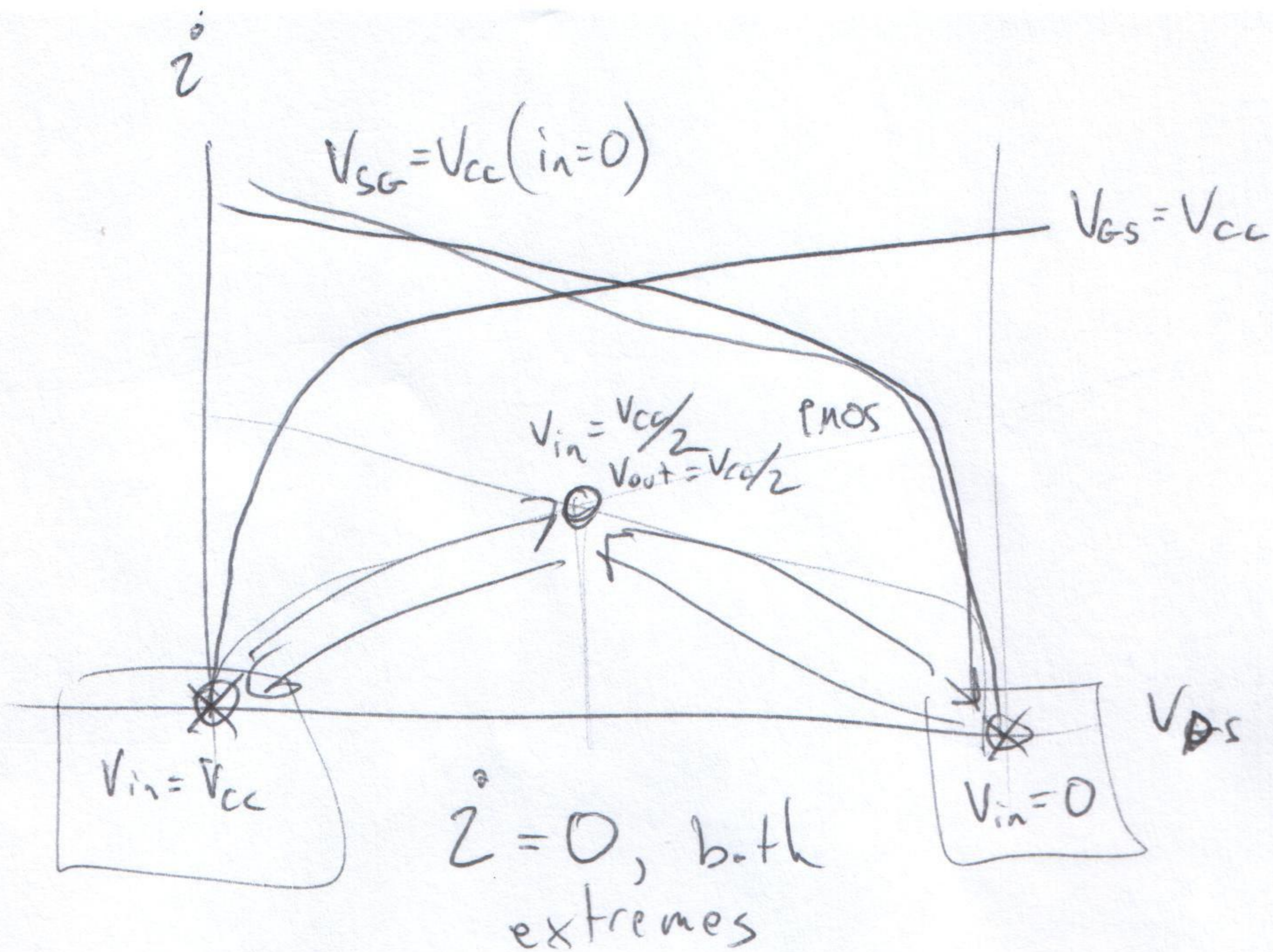 


NOR

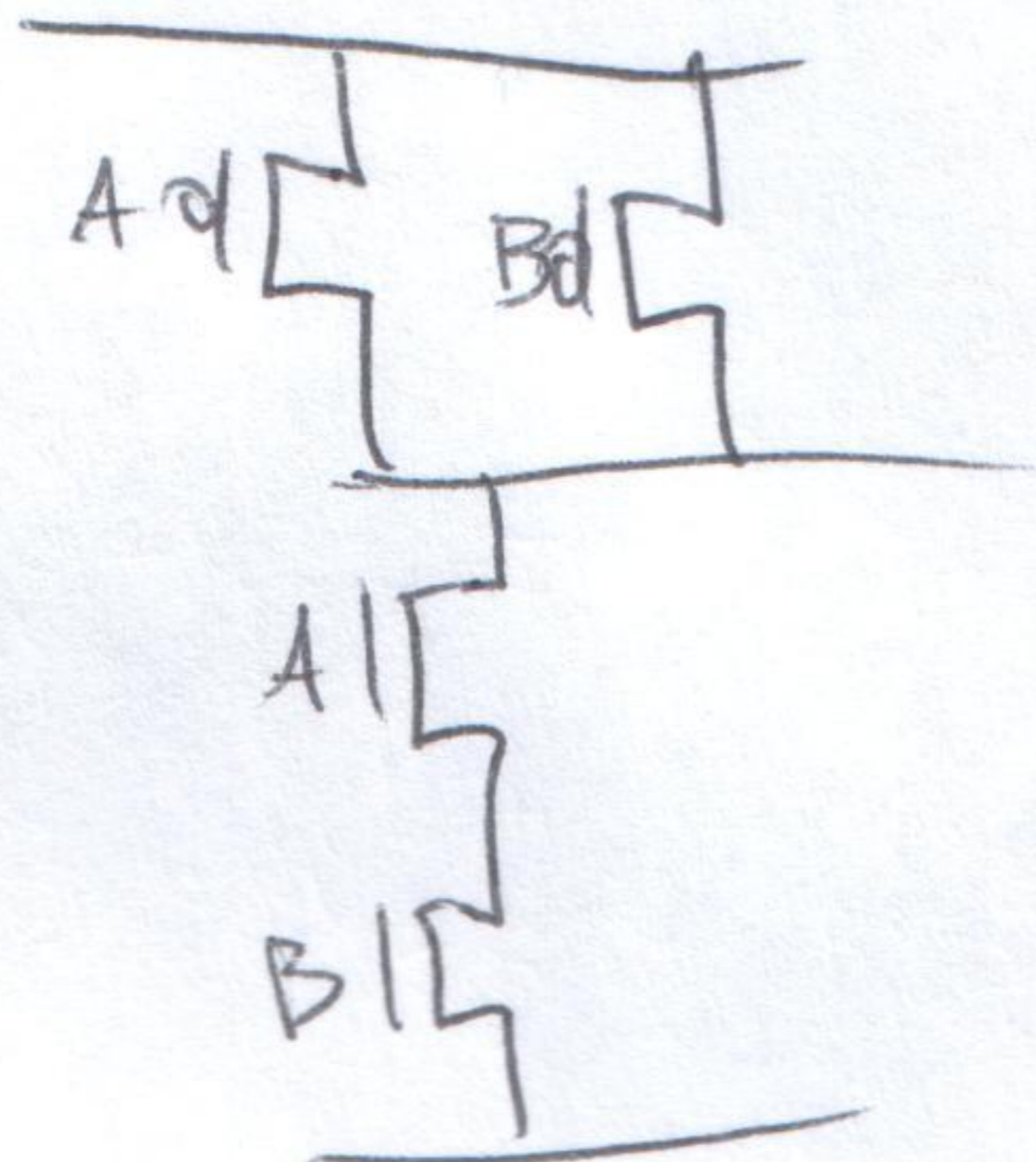


NAND



Why not do this?

 



"PMOS Buffer"

 

Pass 0

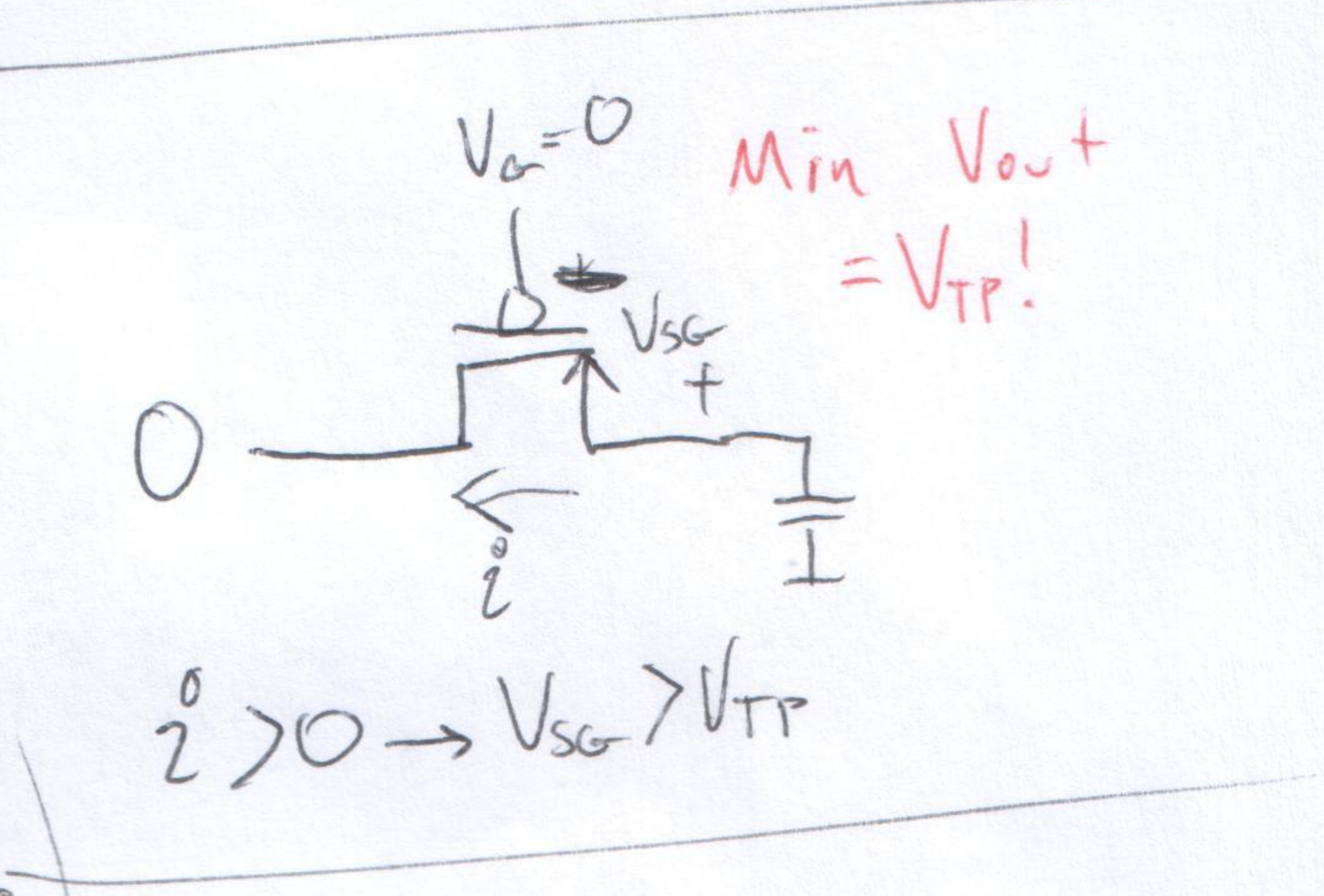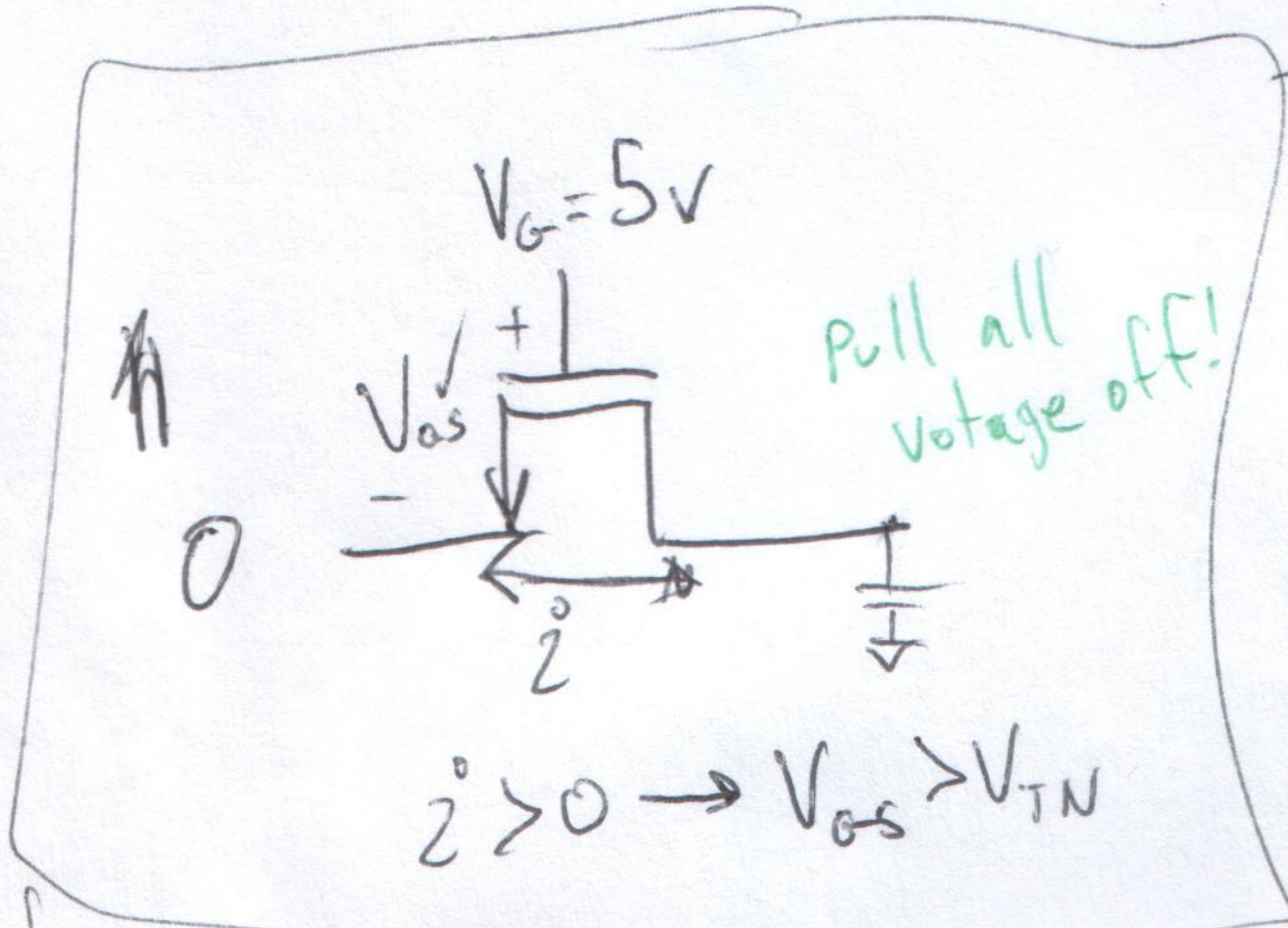

Pass 1

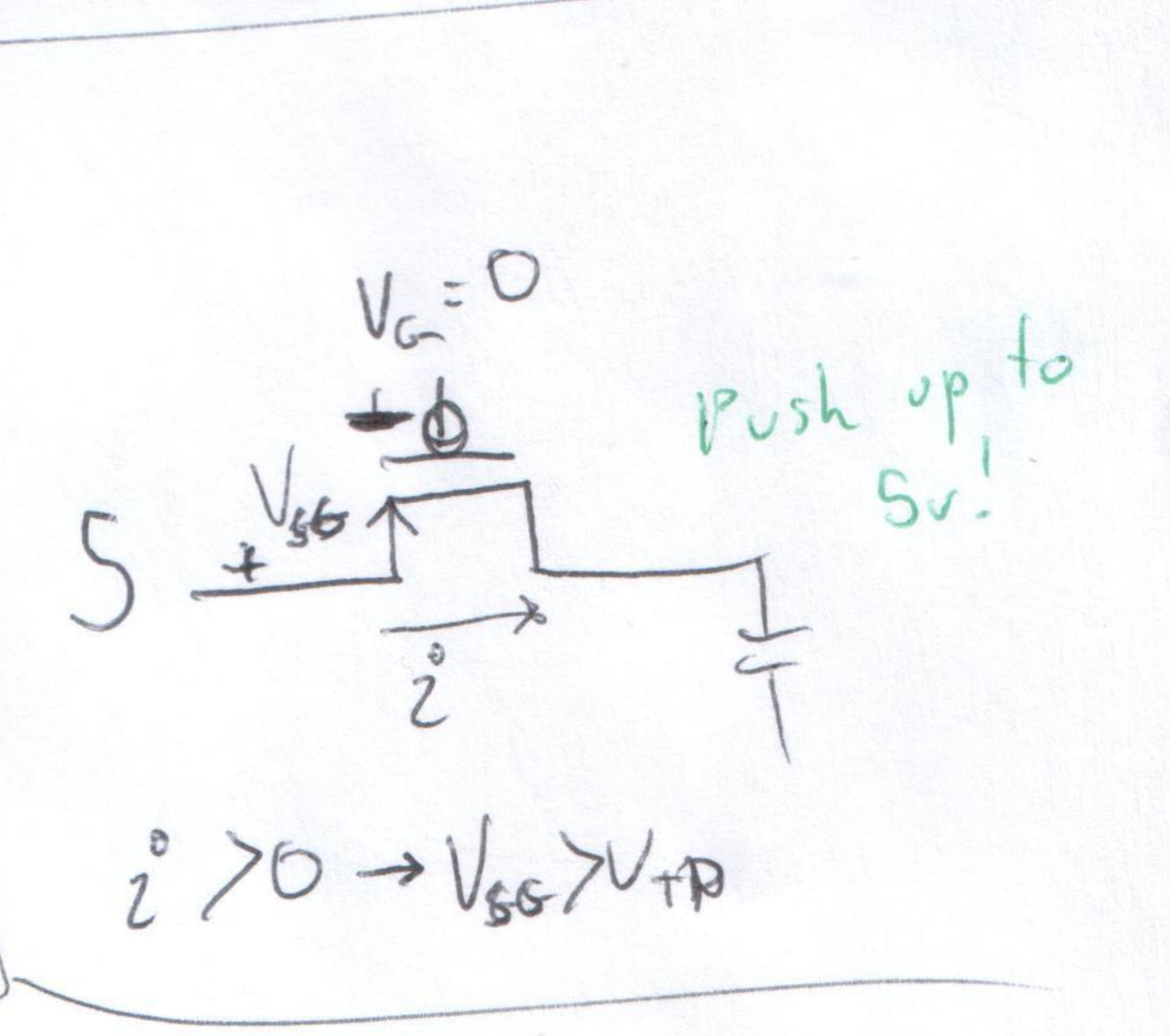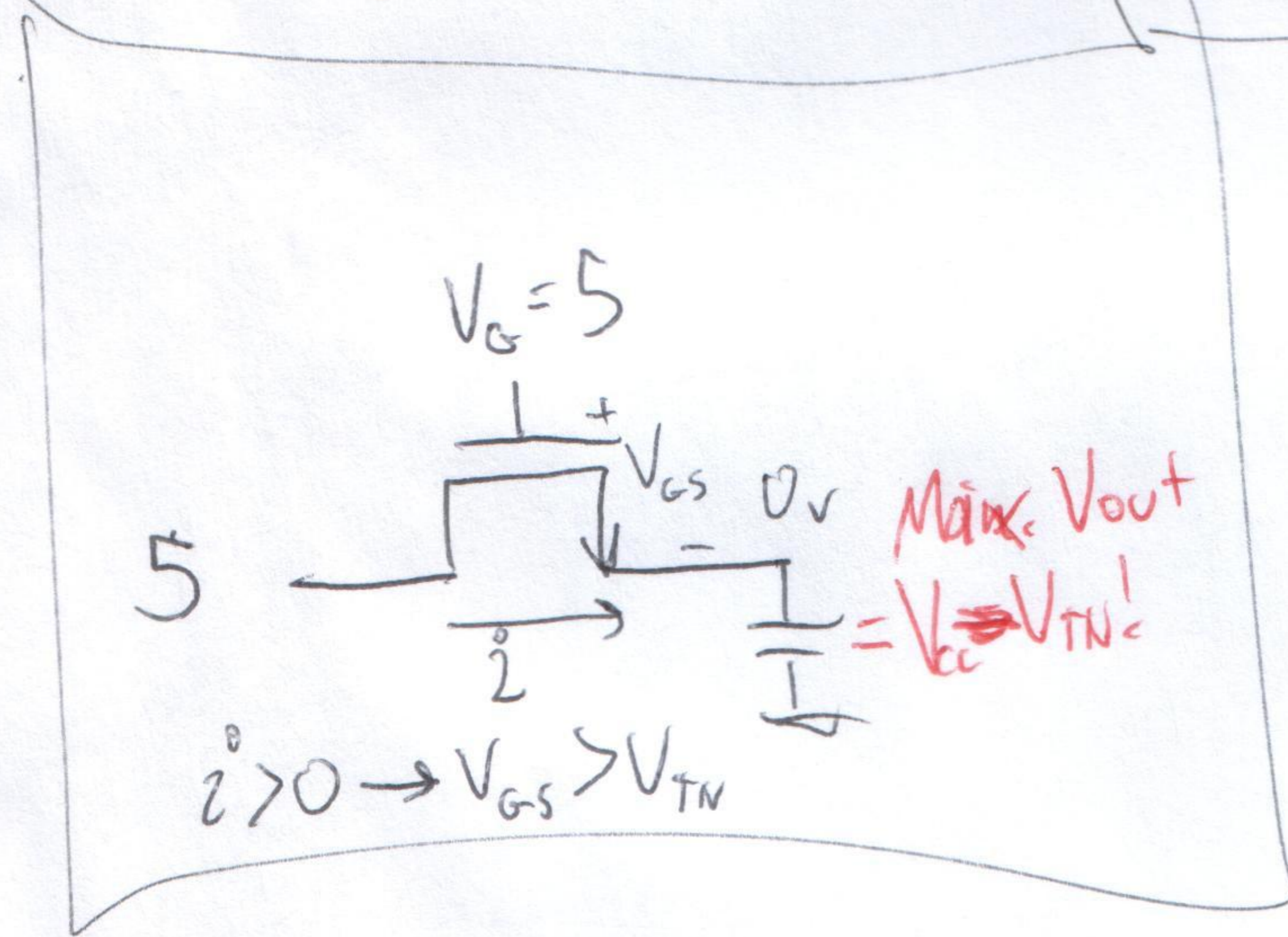

NMOS

PMOS

Implies design of T-Gate:

